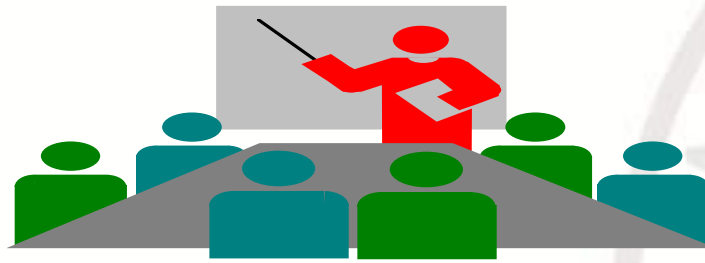




浙江大学
ZHEJIANG UNIVERSITY



数字逻辑设计

LOGIC and Computer Design Fundamentals

CHAPTER 6

Register & Register Transfers

Registers, Microoperations & Implementations (part I)

施青松

Asso. Prof. Shi Qingsong

College of Computer Science and Technology, Zhejiang University

zjsqs@zju.edu.cn


❑ Part 1-Registers, Microoperations and Implementations

- Registers and load enable
- Register transfer operations
- Microoperations - arithmetic, logic, and shift
- Microoperations on a single register
 - ❑ Multiplexer-based transfers
 - ❑ Shift registers

❑ Part 2 - Counters, Register Cells, Buses, & Serial Operations

❑ Part 3 – Control of Register Transfers

Course Outline

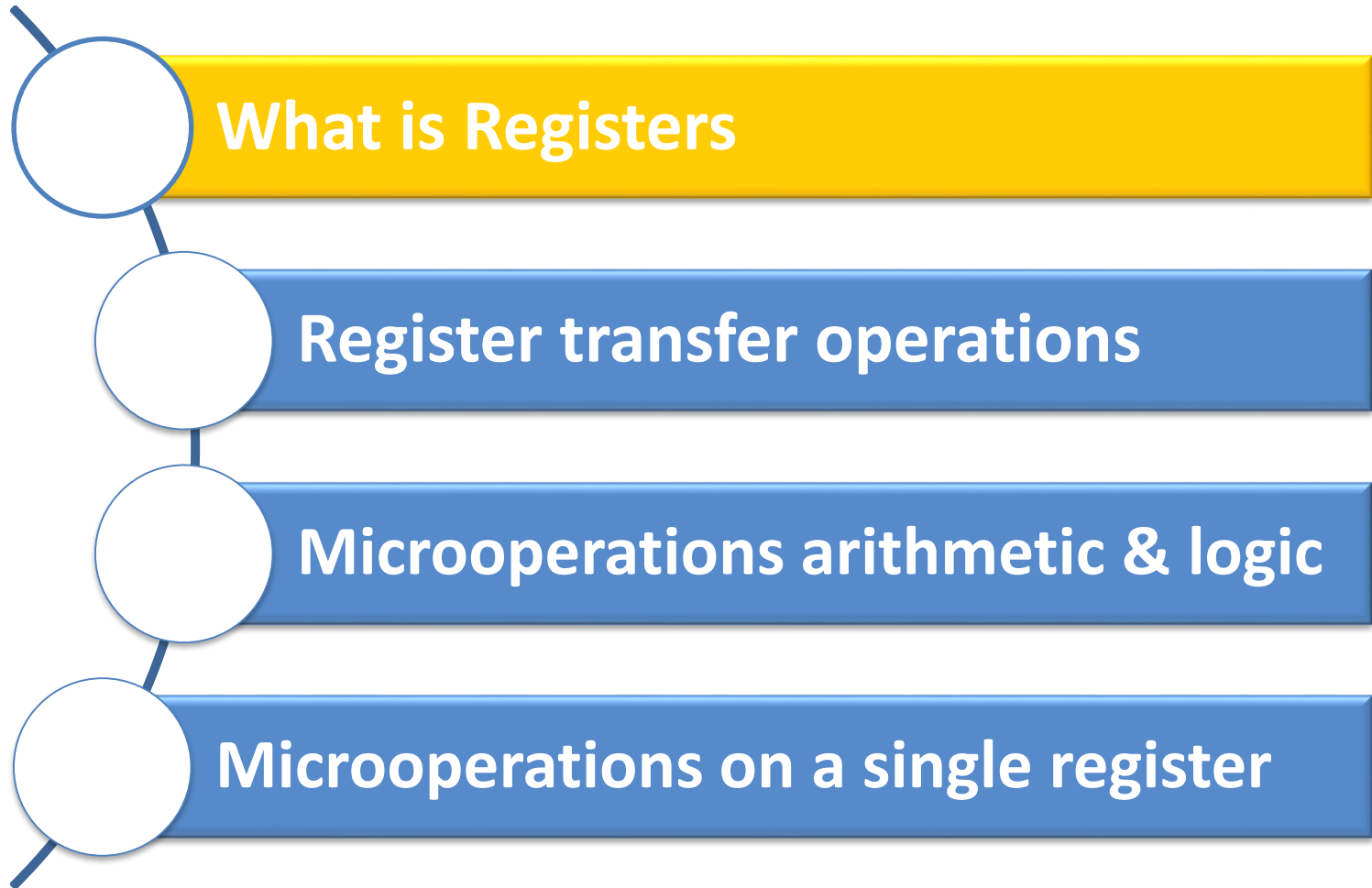



What is Registers

□ Register


- a **collection** of binary storage elements
- In theory, a register is sequential logic which can be defined by a state table
- More often, think of a register as storing a vector of binary values

□ Operating

- Frequently used to **perform simple data storage and data movement and processing operations**

 Example: 2-bit Register

- How many **states** are there?
- How many **input** combinations?
Output combinations?
- What is the *output function*?
- What is the *next state function*?
- Moore or Mealy?



State Table:

Current State A1 A0	Next State A1(t+1) A0(t+1) For In1 In0 =				Output (=A1 A0)	
	00	01	10	11	Y1	Y0
	00	01	10	11	0	0
0 0	00	01	10	11	0	0
0 1	00	01	10	11	0	1
1 0	00	01	10	11	1	0
1 1	00	01	10	11	1	1

- What are the **quantities** above for an n -bit register?



Register Design Models

- ❑ Due to the **large numbers** of **states** and **input** combinations as n becomes large, the state diagram/state table model is **not feasible!**
- ❑ What are methods we can use to design registers?
 - Add predefined combinational circuits to registers
 - ❑ Example: To count up, connect the register flip-flops to an **incrementer**
 - Design **individual cells** using the state diagram/state table model and combine them into a register
 - ❑ A 1-bit cell has just two states
 - ❑ Output is usually the state variable



Register Storage

□ Expectations:

- A register can store information for multiple clock cycles
- To “store” or “load” information should be controlled by a signal

□ Reality:

- A D flip-flop register loads information on every clock cycle

□ Realizing expectations:

- Use a signal to *block* the clock to the register,
- Use a signal to control *feedback* of the output of the register back to its inputs, or
- Use other SR or JK flip-flops, that for (0,0) applied, store their state

□ Load is a frequent name for the signal that controls register storage and loading


- Load = 1: **Load** the values on the data inputs
- Load = 0: **Store** the values in the register

Clock Skew :

Registers with Clock Gating



 - The ***Load*** signal **enables** the **clock signal** to pass through if 1 and prevents the clock signal from passing through if 0.
- Example: For Positive Edge-Triggered or Negative Pulse Master-Slave Flip-flop:



- What logic is needed for gating?

- **What is the problem?**

$$\text{Gated Clock} = \text{Clock} + \text{Load}$$

Clock **Skew** of gated clocks with respect to clock or each other

Registers with Load-Controlled Feedback




- ❑ A more reliable way to selectively load a register:
 - Run the clock continuously, and
 - Selectively use a load control to change the register contents.

- ❑ Example: 2-bit register with Load Control:


- ❑ For Load = 0, loads register contents (hold current values)

- ❑ For Load = 1, loads input values (load new values)

 - ❑ Hardware more complex than clock gating, but free of timing problems




Course Outline

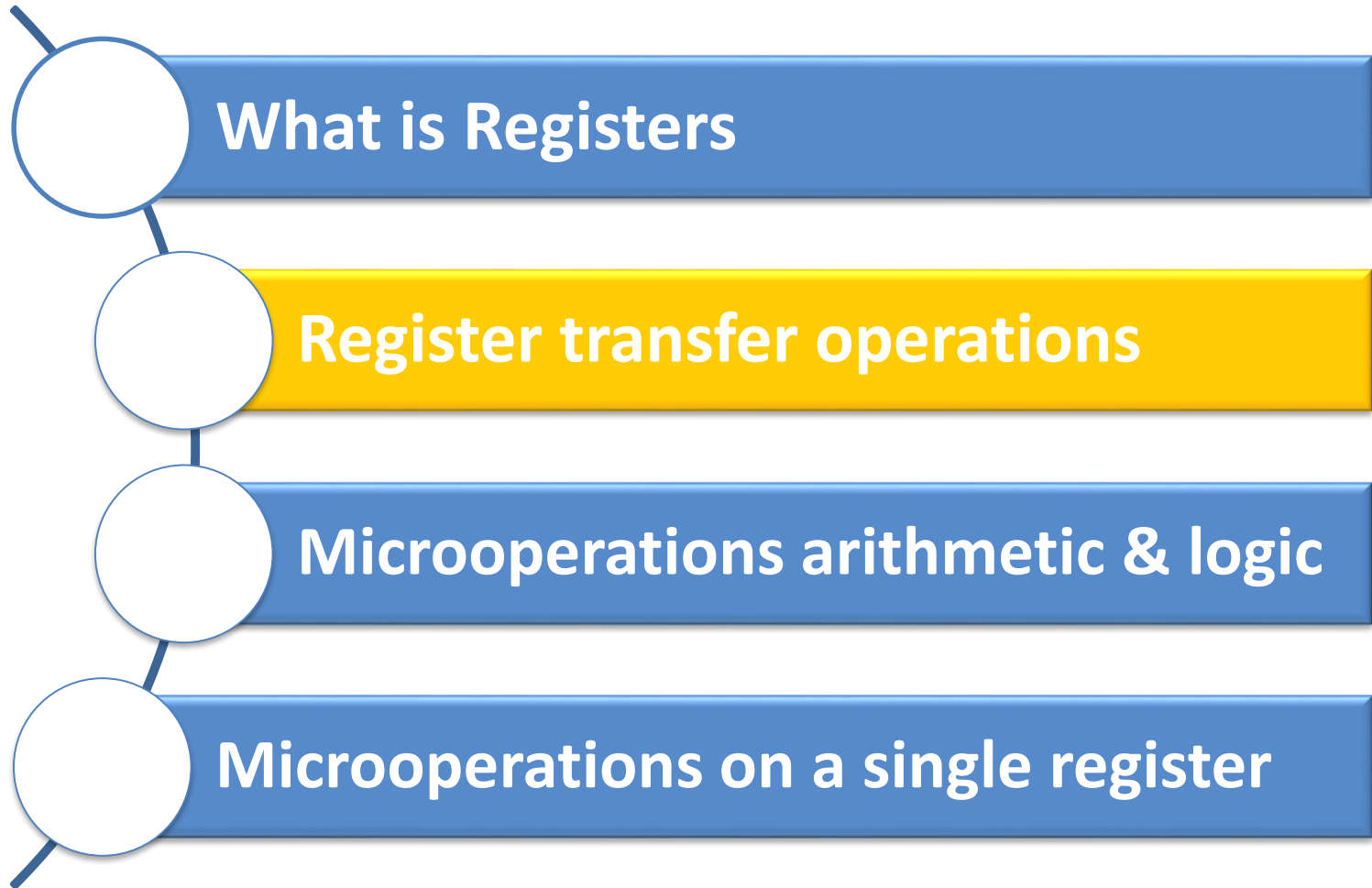

Register Transfer Operations

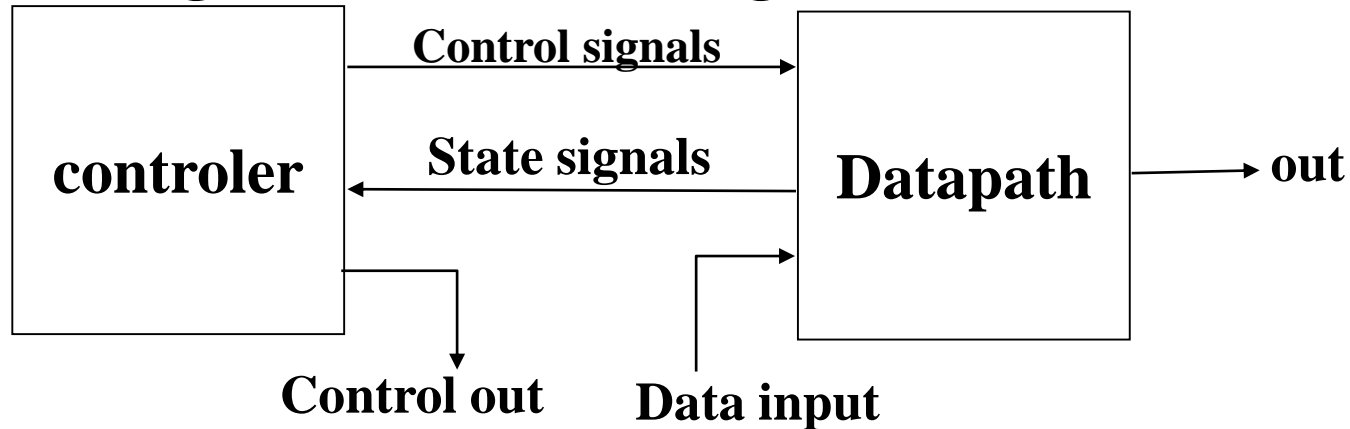
- **Register Transfer Operations** – The movement and processing of data stored in registers



- **Three basic components:**
 - Set of registers
 - Operations
 - control of operations
- **Elementary Operations** -load, count, shift, add, bitwise "OR", etc.
 - Elementary operations called *microoperations*



Register Notation

 


- ❑ Letters and numbers – denotes a register (ex. R2, PC, IR)
- ❑ Parentheses () – denotes a range of register bits
 - ex. R1(1), PC(7:0), PC(L)
- ❑ Arrow (\leftarrow) – denotes data transfer
 - ex. $R1 \leftarrow R2$, $PC(L) \leftarrow R0$
- ❑ Comma – separates parallel operations
- ❑ Brackets [] – Specifies a memory address
 - ex. $R0 \leftarrow M[AR]$, $R3 \leftarrow M[PC]$

Conditional Transfer

- If ($K1 = 1$) then ($R2 \leftarrow R1$) is shortened to

$K1: (R2 \leftarrow R1)$

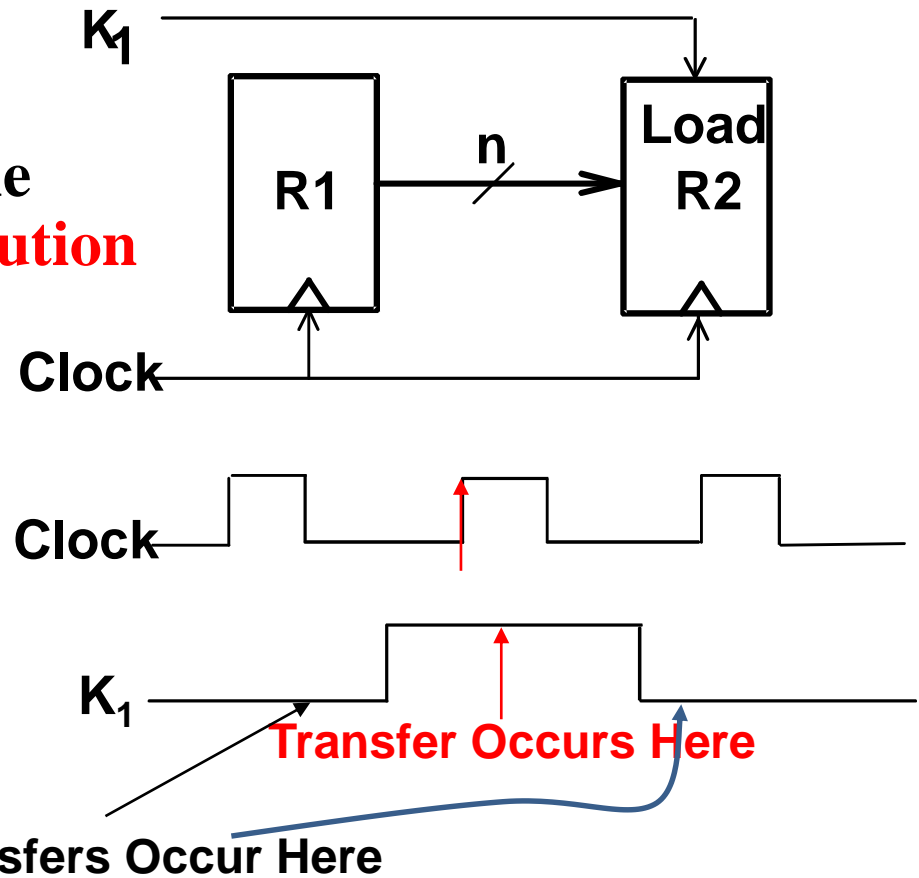where **$K1$** is a control variable specifying a **conditional execution** of the microoperation.



□ Logical Groupings:

- Transfer - move data from one register to another
- Arithmetic - perform arithmetic on data in registers
- Logic - manipulate data or use bitwise logical operations
- Shift - shift data in registers

Arithmetic operations

+ Addition
– Subtraction
* Multiplication
/ Division

Logical operations

✓ Logical OR
^ Logical AND
⊕ Logical Exclusive OR
– Not



Example Microoperations

- Add the content of R1 to the content of R2 and place the result in R1.

$$R1 \leftarrow R1 + R2$$

- Multiply the content of R1 by the content of R6 and place the result in PC.

$$PC \leftarrow R1 * R6$$

- Exclusive OR the content of R1 with the content of R2 and place the result in R1.

$$R1 \leftarrow R1 \oplus R2$$

Example Microoperations (Continued)



- Take the 1's Complement of the contents of R2 and place it in the PC.

$$PC \leftarrow \overline{R2}$$

- On condition K1 **OR** K2, the content of R1 is **Logic bitwise OR** with the content of R3 and the result placed in R1.

$$(K1 + K2): R1 \leftarrow R1 \vee R3$$

NOTE


- "+" (as in $K_1 + K_2$) means "OR"
- In $R1 \leftarrow R1 + R3$, + means "plus."



Control Expressions

- The **control expression** for an operation appears to the left of the operation and is separated from it by a colon
 - Control expressions specify the **logical condition** for the operation to occur
 - Control expression values of:
 - Logic "1" -- the operation occurs.
 - Logic "0" -- the operation is does not occur.
- Example:
 $\overline{X} \text{ K1} : R1 \leftarrow R1 + R2$
 $X \text{ K1} : R1 \leftarrow R1 + \overline{R2} + 1$
 - Variable K1 enables the add or subtract operation.
 - If $X = 0$, then $\overline{X} = 1$ so $\overline{X} \text{ K1} = 1$, activating the addition of R1 and R2.
 - If $X = 1$, then $X \text{ K1} = 1$, activating the addition of R1 and the two's complement of R2 (subtract).

Course Outline

 



Arithmetic Microoperations

□ From
Table
7-3:

Symbolic Designation	Description
$R0 \leftarrow R1 + R2$	Addition
$R0 \leftarrow \overline{R1}$	Ones Complement
$R0 \leftarrow \overline{R1} + 1$	Two's Complement
$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1 (2's Comp)
$R1 \leftarrow R1 + 1$	Increment (count up)
$R1 \leftarrow R1 - 1$	Decrement (count down)

- Note that any register may be specified **for source 1, source 2, or destination.**
- These simple microoperations operate on the whole word



Logical Microoperations

□ From Table 7-4:

Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (sets bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \oplus R2$	Bitwise EXOR (complements bits)

Logical Microoperations (continued)



- Let $R1 = 10101010$, and $R2 = 11110000$
- Then after the operation, $R0$ becomes:

R0	Operation
01010101	$R0 \leftarrow \overline{R1}$
11111010	$R0 \leftarrow R1 \vee R2$
10100000	$R0 \leftarrow R1 \wedge R2$
01011010	$R0 \leftarrow R1 \oplus R2$



Shift Microoperations

- From Table 7-5:
- Let $R2 = 11001001$
- Then after the operation, $R1$ becomes:

Symbolic Designation	Description
$R1 \leftarrow sl R2$	Shift Left
$R1 \leftarrow sr R2$	Shift Right

R1	Operation
10010010	$R1 \leftarrow sl R2$
01100100	$R1 \leftarrow sr R2$

- Note: These shifts "zero fill". Sometimes a separate flip-flop is used to provide the data shifted in, or to "catch" the data shifted out.
- Other shifts are possible (rotates, arithmetic) (see Chapter 10).



Transfers and Assigning

□ assign(流描述)

assign r0 = {0, r0[15:1]}; //Right Shift

□ always(过程描述语句)

- 对于复杂的电路行为，用assign赋值无法描述
- always可以用来描述复杂的信号传输过程
- 赋值必须是reg变量，但结果由电路综合决定，不一定是reg

Always @ (触发表达式)begin

//过程赋值

//条件语句

.....

end


■ timing

- 非阻塞赋值: **\leq** , 触发边沿同时赋值(并行)
- 阻塞赋值: **$=$** , 先赋值再同步, 较难把握(组合电路, assign)

□ 触发事件表达式有:

- 组全电路使用变量:
(a)、(a or b), 可用“*”代替
- 时序电路用时钟边沿:
(posedge clk) //上升沿
(negedge clk) //下降沿
(posedge clk or negedge res) //上下边沿

Course Outline

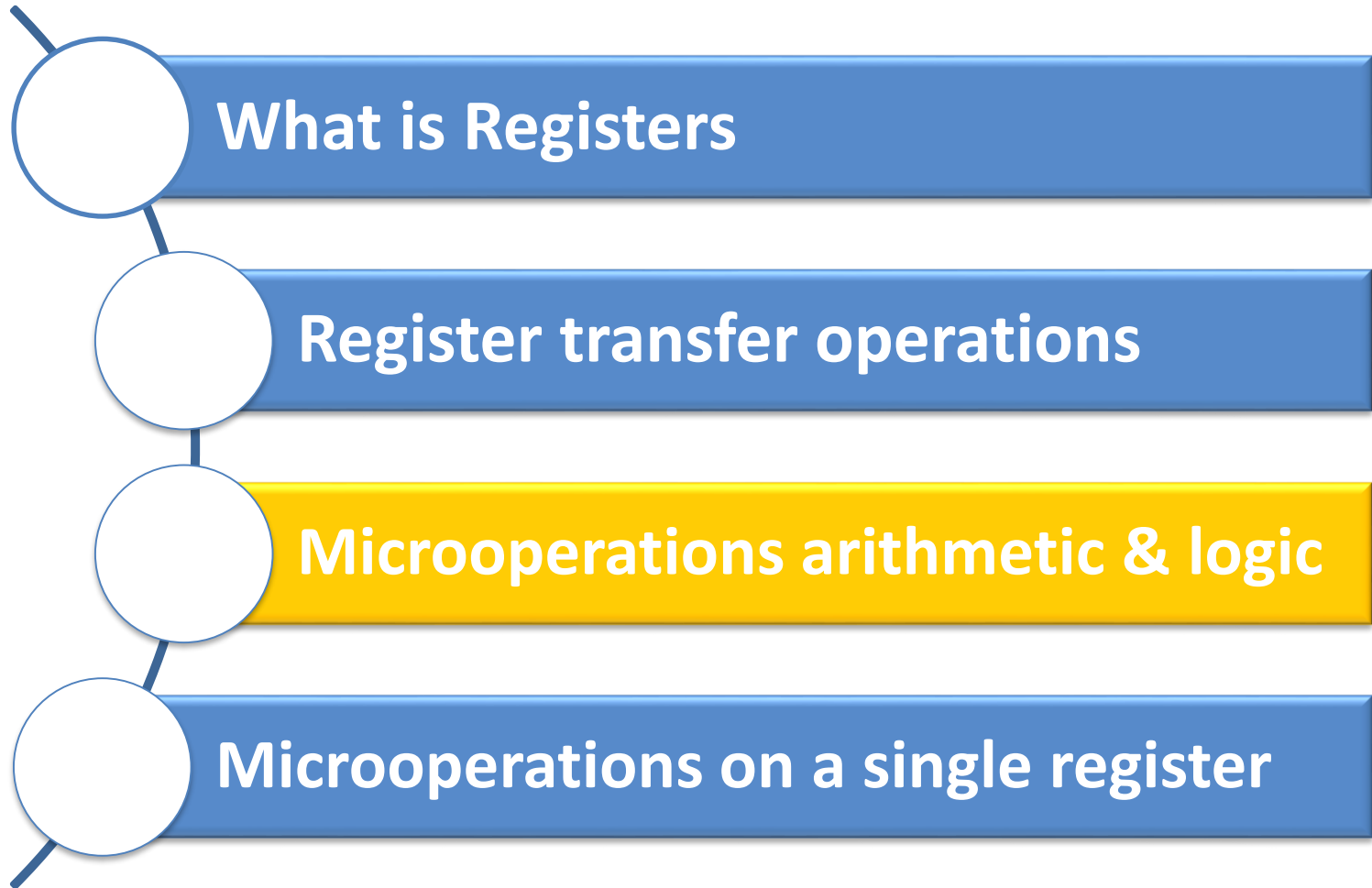



Register Transfer Structures


- ❑ **Multiplexer-Based Transfers** - Multiple inputs are selected by a multiplexer dedicated to the register
- ❑ **Bus-Based Transfers** - Multiple inputs are selected by a shared multiplexer driving a bus that feeds inputs to multiple registers
- ❑ **Three-State Bus** - Multiple inputs are selected by 3-state drivers with outputs connected to a bus that feeds multiple registers
- ❑ **Other Transfer Structures** - Use multiple multiplexers, multiple buses, and combinations of all the above

Multiplexer-Based Transfers

- ❑ Multiplexers **connected to register inputs** produce flexible transfer structures (Note: Clocks are omitted for clarity)
- ❑ The transfers are:


K1: $R0 \leftarrow R1$

K2 $\overline{K1}$: $R0 \leftarrow R2$

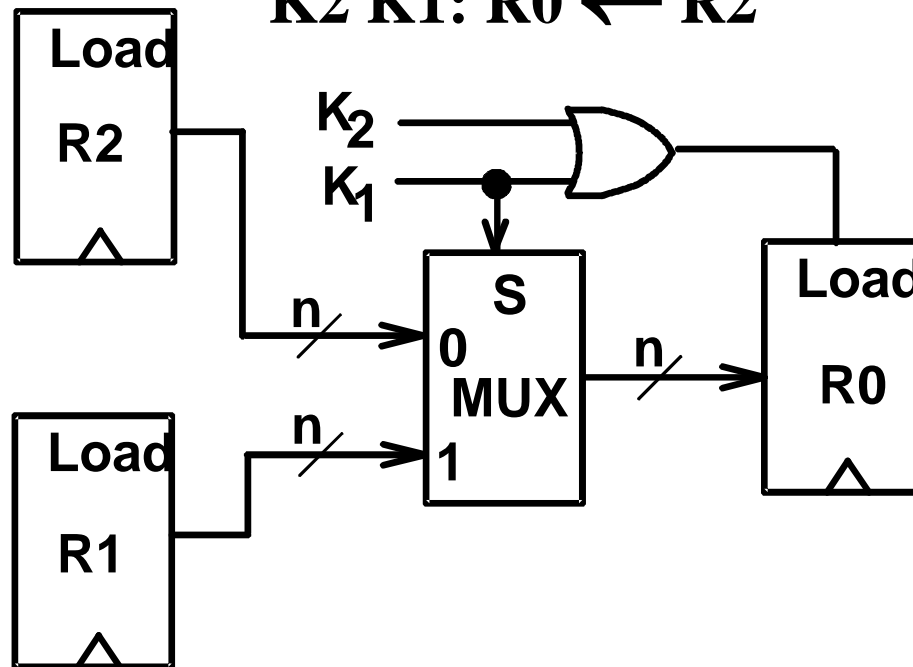

Shift Registers

 
- Shift Registers move data laterally within the register toward its MSB or LSB position
- In the simplest case, the shift register is simply a set of D flip-flops connected in a row like this:



- Data input, In, is called a *serial input* or the *shift right input*.
- Data output, Out, is often called the *serial output*.
- The vector (A, B, C, Out) is called the *parallel output*.

Shift Registers Running

 
- The behavior of the serial shift register is given in the listing on the lower right
- T0 is the register state just before the first clock pulse occurs
- T1 is after the first pulse and before the second.
- Initially unknown states are denoted by “?”
- Complete the last three rows of the table



CP	In	A	B	C	Out
T0	0	?	?	?	?
T1	1	0	?	?	?
T2	1	1	0	?	?
T3	0	1	1	0	?
T4	1				
T5	1				
T6	1				

Parallel Load Shift Registers

 - By adding a mux between each shift register stage, data can be shifted or loaded
- If SHIFT is low, A and B are replaced by the data on D_A and D_B lines, else data shifts right on each clock.
- By adding more bits, we can make n -bit parallel load shift registers.
- A parallel load shift register with an added “hold” operation that stores data unchanged is given in Figure 7-10 of the text.




Shift Registers with Additional Functions




- By placing a 4-input multiplexer in front of each D flip-flop in a shift register, we can implement a circuit with **shifts right, shifts left, parallel load, hold**.
- Shift registers can also be designed to shift more than a single bit position right or left
- Shift registers can be designed to shift a variable number of bit positions specified by a variable called a ***shift amount***.

Application of the shift register

 

通过P2S模块输出:

$P_Data[63:0] = SEGMENT[63:0]$

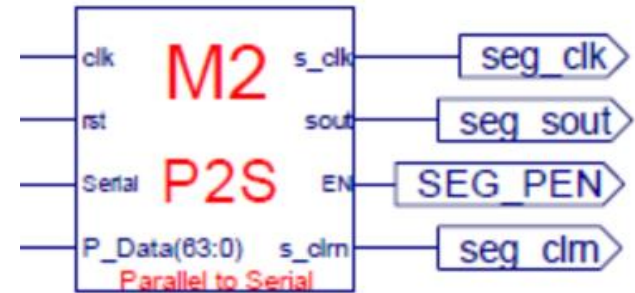

Synchronous serial transmission: Parallel-serial Converter




◎ Parallel-serial Converter

Ⓔ 没有启动命令时: 移位输入 “1”

Start=0

S/L=0

 



移位寄存器应用：P2S模块设计

```
1  module          P2S(input wire clk,                //parallel to serial
2                  input wire rst,
3                  input wire Start,
4                  input wire[DATA_BITS-1:0] PData,
5                  output wire s_clk,
6                  output wire s_clrn,
7                  output wire sout,
8                  output reg  EN
9                  );
10
11  parameter
12      DATA_BITS = 16,                // data length
13      DATA_COUNT_BITS = 4,          // data shift bits
14      DIR = 0;                       // Shift direction =0左移
15
16  wire S1,S0,SL,SR;
17  wire [DATA_BITS:0] D,Q;
18  reg [1:0]Go = 00, S = 00;
19
20      assign {SR,SL} = 2'b11;         //左移右移初值=1，用于传输标志
21      assign {S1,S0} = DIR ? {S[0],S[1]} : S; //调整移位方向
22      assign D       = DIR ? {1'b0,PData} : {PData,1'b0}; //置移位末端标志"0"
23      wire finish     = DIR ? &Q[DATA_BITS:1] : &Q[DATA_BITS-1:0]; //移位传输结束：全"1"
24      assign sout      = DIR ? Q[0] : Q[DATA_BITS]; //串行输出：右移输出Q[0]
25
```



```
26  SHIFT64  #(.DATA_BITS(DATA_BITS)) [参数传入] //调用移位寄存器，宽度=DATA_BITS
27          PTOS(.clk(clk),
28              .SR(SR), .SL(SL),
29              .S1(S1), .S0(S0),
30              .D(D), .Q(Q)
31          );
32
33  always @(posedge clk ) //采样Start上升沿
34      Go <= {Go[0],Start};
35  assign shift  =(Go==2'b01)? 1:0; //移位启动采样
36
37  always @(posedge clk or posedge rst)begin //启动传输结束控制块
38      if(rst) begin EN = 1; S = 2'b11; end
39      else begin
40          if(shift) begin EN = 0; S = 2'b11; end //并行置入
41          else begin
42              if(!finish)begin EN = 0; S = 2'b10; end //启动移位传输
43              else begin EN = 1; S = 2'b00; end //结束移位
44          end
45      end
46  end
47  assign s_clk = finish | clk; //禁止74LS164时钟
48  assign s_clrn = 1;
49
50 endmodule
```

仅供参考



```
1 module SHIFT64(input clk,
2               input SR,SL,
3               input S1,S0,
4               input [DATA_BITS:0]D,
5               output reg[DATA_BITS:0]Q
6               );
7 parameter
8     DATA_BITS = 16,           // data length
9     DATA_COUNT_BITS = 4;      // data shift bits
10
11
12     always @(posedge clk )begin
13         case({S1,S0})
14             2'b00: Q <= Q;           //S1S0=00 保持
15             2'b01: Q <= {SR,Q[DATA_BITS:1]}; //S1S0=01 右移DIR=1
16             2'b10: Q <= {Q[DATA_BITS-1:0],SL}; //S1S0=10 左移DIR=0
17             2'b11: Q <= D;           //S1S0=11 并入
18         endcase
19     end
20
21 endmodule
22
```



第六章作业 一

Ch6-1

page391-392:

6-1, 6-2, 6-5

With Registers, It is More easy!

Thank you!

