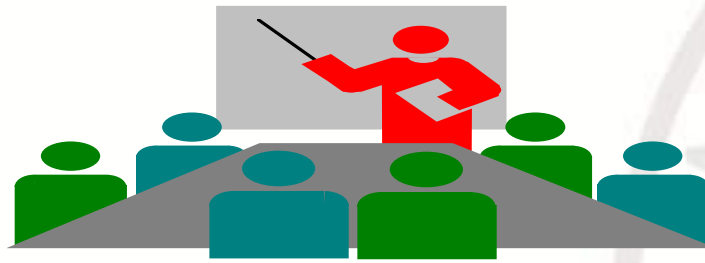




浙江大学
ZHEJIANG UNIVERSITY



数字逻辑设计

LOGIC and Computer Design Fundamentals

CHAPTER 6

Register & Register Transfers

Counters, Register Cells, Buses, & Serial Operations (part II)

施青松

Asso. Prof. Shi Qingsong

College of Computer Science and Technology, Zhejiang University


zjsqs@zju.edu.cn



Overview

- Part 1 – Registers, Microoperations and Implementations
- **Part 2 – Counters, register cells, buses, & serial operations**
 - Microoperations on single register (continued)
 - Counters
 - Register cell design
 - Multiplexer and bus-based transfers for multiple registers
 - Serial transfers and microoperations
- Part 3 – Control of Register Transfers

Course Outline


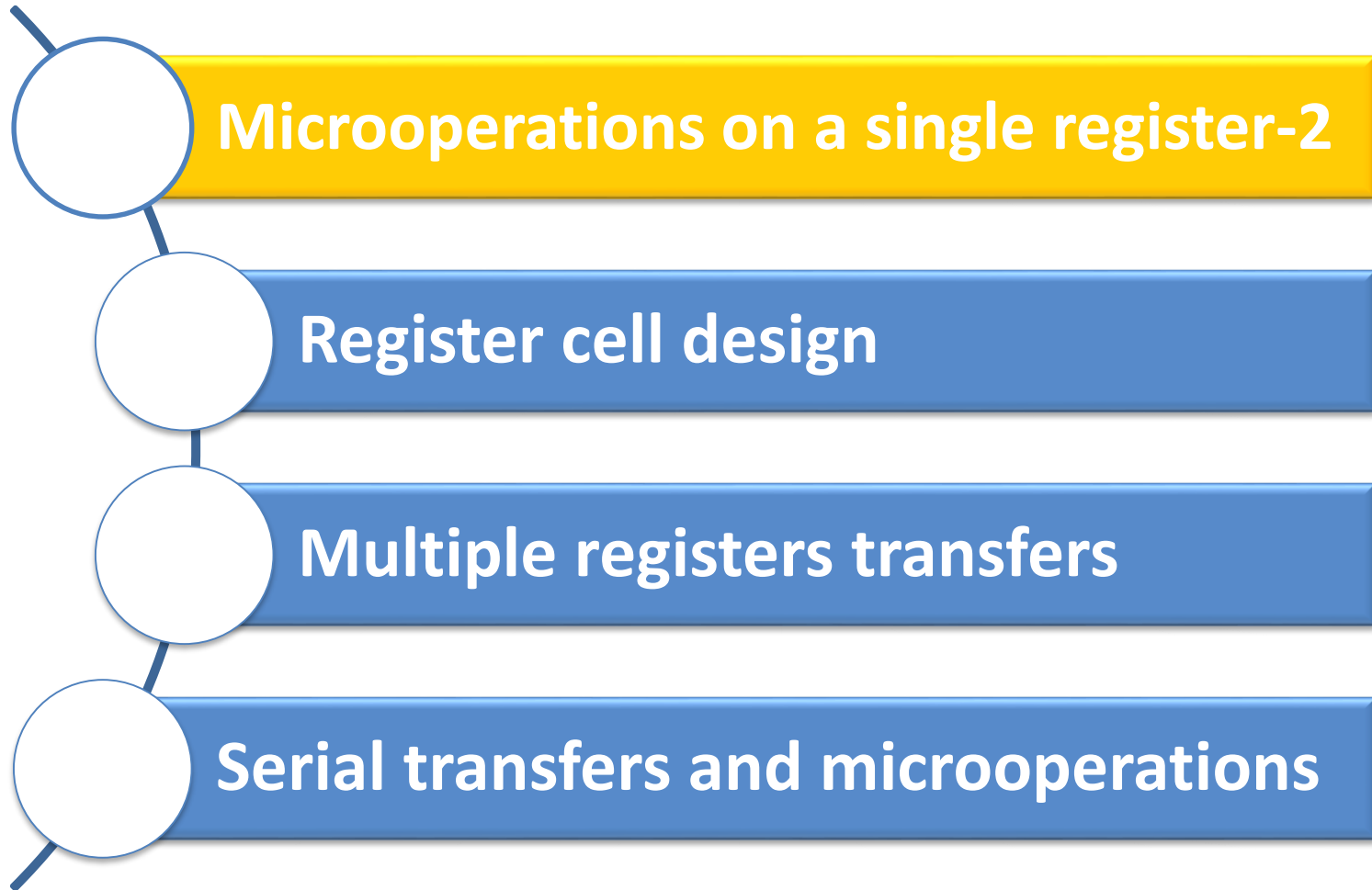


- ❑ Counters are sequential circuits which "count" through a **specific state sequence**. They can count up, count down, or **count through other fixed sequences**. Two distinct types are in common usage:
- ❑ **Ripple Counters**
 - Clock connected to the flip-flop clock input on the LSB bit flip-flop
 - For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous!
 - Output change is delayed more for each bit toward the MSB.
 - Resurgent because of low power consumption
- ❑ **Synchronous Counters**
 - Clock is directly connected to the flip-flop clock inputs
 - Logic is used to implement the desired state sequencing

Ripple Counter

□ How does it work?

  - When there is a positive edge on the clock input of A, A complements
- The clock input for flip-flop B is the complemented output of flip-flop A
- When flip A changes from 1 to 0, there is a positive edge on the clock input of B causing B to complement




Ripple Counter (continued)

□ The arrows show the cause-effect relationship from the prior slide =>

□ The corresponding sequence of states =>
 
$$(B,A) = (0,0), (0,1), (1,0), (1,1), (0,0), (0,1), \dots$$



□ Each additional bit, C, D, ... behaves like bit B, changing half as frequently as the bit before it.

□ For 3 bits: $(C,B,A) = (0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), (1,1,0), (1,1,1), (0,0,0), \dots$




Ripple Counter (continued)

- ❑ These circuits are called *ripple counters* because each edge sensitive transition (positive in the example) causes a change in the next flip-flop's state.
- ❑ The changes “ripple” upward through the chain of flip-flops, i. e., each transition occurs after a clock-to-output delay from the stage before.
- ❑ To see this effect in detail look at the waveforms on the next slide.

Ripple Counter (continued)

□ Starting with $C = B = A = 1$, equivalent to $(C,B,A) = 7$ base 10, the next clock increments the count to $(C,B,A) = 0$ base 10. In fine timing detail:

 - The clock to output delay t_{PHL} causes an increasing delay from clock edge for each stage transition.
- Thus, the count “ripples” from least to most significant bit.
- For n bits, total worst case delay is $n t_{PHL}$.






Synchronous Counters

Synchronous Counters

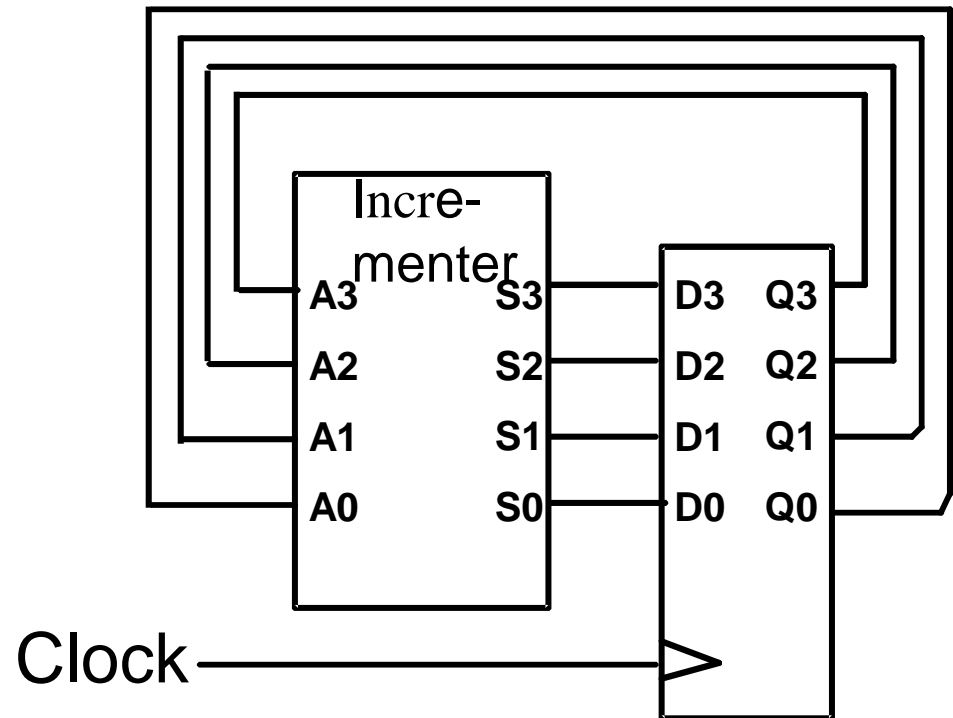- ❑ To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.
- ❑ For an up-counter, use an incrementer =>



Synchronous Counters Internal

Internal details => Incrementer

Internal Logic


- XOR complements each bit
- AND chain causes complement of a bit if all bits toward LSB from it equal 1

Count Enable

- Forces all outputs of AND chain to 0 to “hold” the state

Carry Out

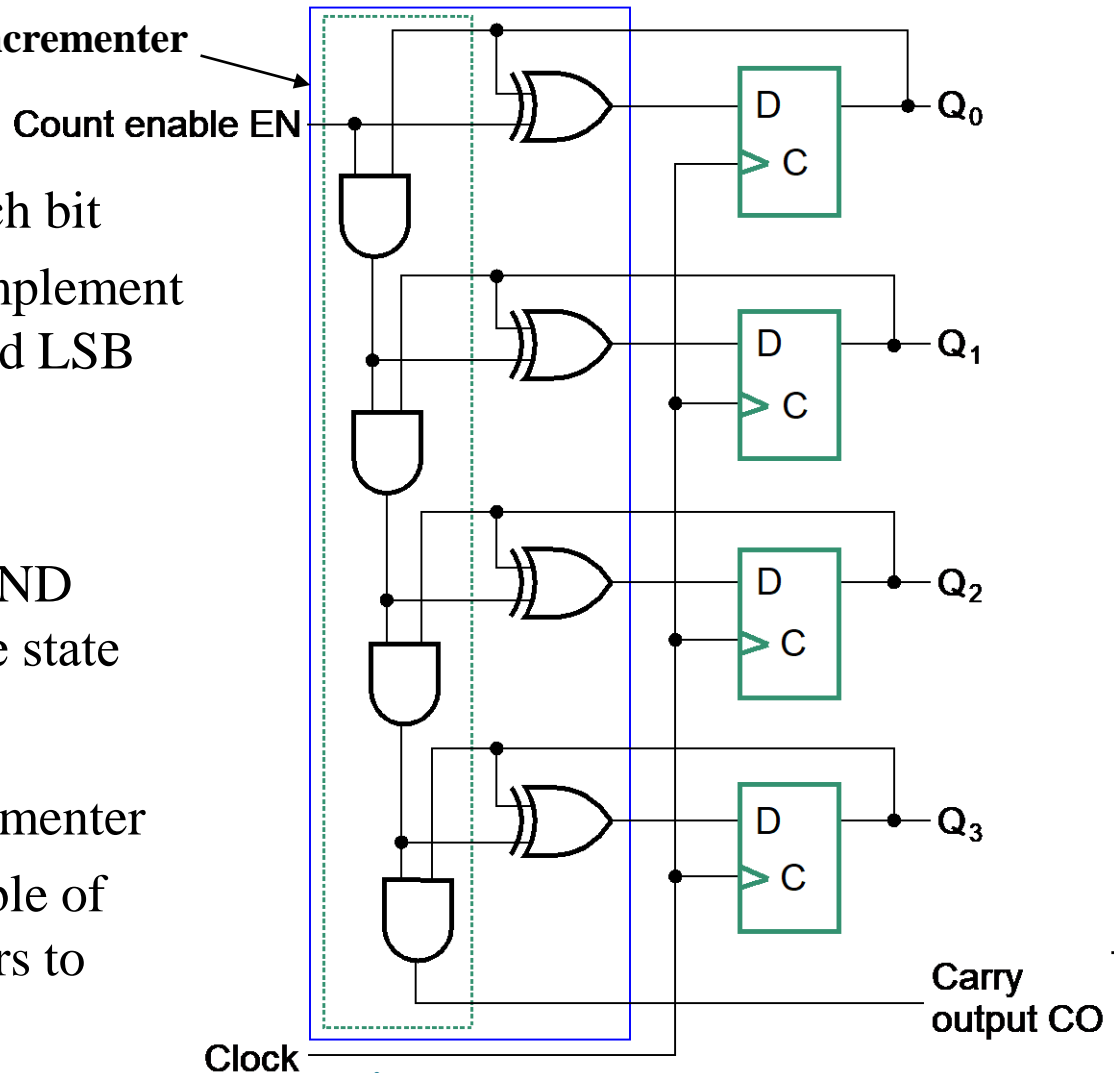- Added as part of incrementer
- Connect to Count Enable of additional 4-bit counters to form larger counters



Reduces delays Synchronous Counters



□ Carry chain

- series of AND gates through which the carry “ripples”
- Yields long path delays
- Called *serial gating*

□ Replace AND carry chain with ANDs => in parallel

- Reduces path delays
- Called *parallel gating*
- Like carry lookahead
- Lookahead can be used on COs and ENs to prevent long paths in large counters


□ Symbol for Synchronous Counter

  

Counter with Parallel Load

- **Add path for input data**
 - enabled for Load = 1
- **Add logic to:**
 - disable count logic for Load = 1
 - disable feedback from outputs for Load = 1
 - enable count logic for Load = 0 and Count = 1
- **The resulting function table:**

Load	Count	Action
0	0	Hold Stored Value
0	1	Count Up Stored Value
1	X	Load D

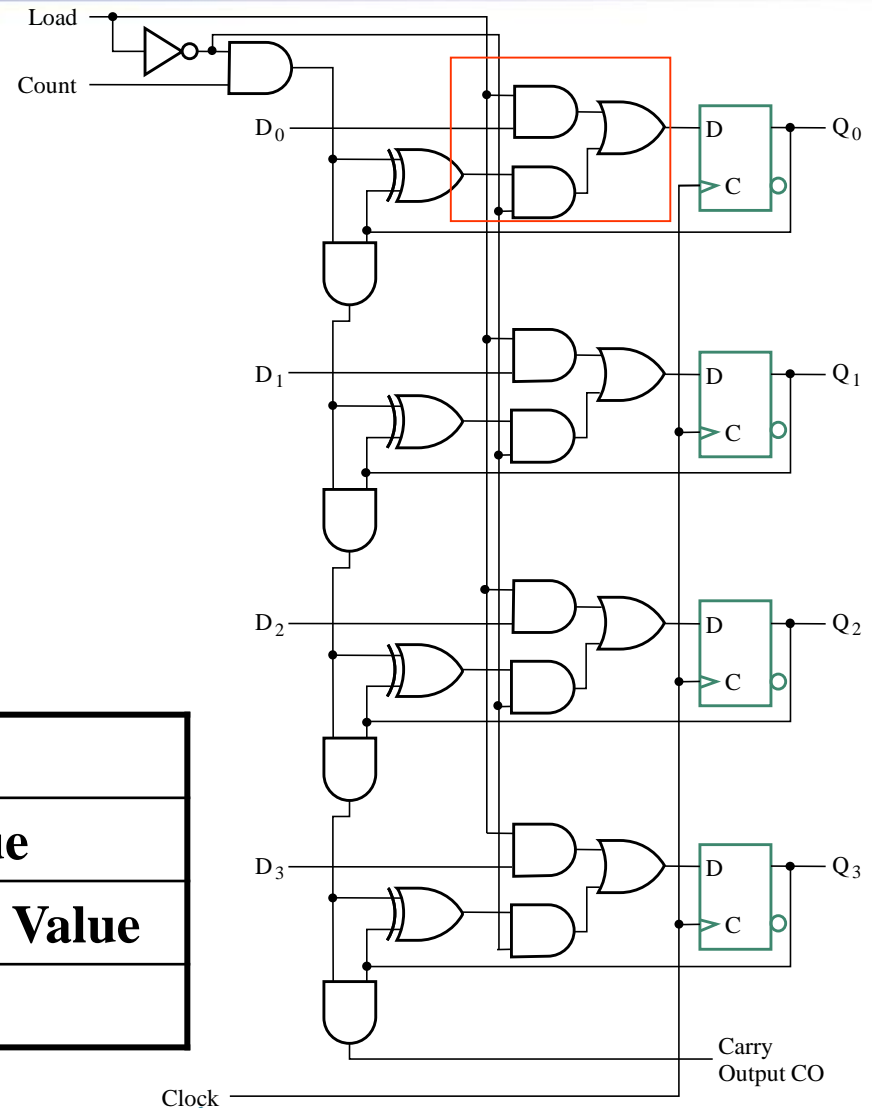



Common Counters



Other Counters

□ See text for:

- *Down Counter* - counts downward instead of upward
- *Up-Down Counter* - counts up or down depending on value a control input such as Up/Down
- *Parallel Load Counter* - Has parallel load of values available depending on control input such as Load

□ *Divide-by- n (Modulo n) Counter*

- Count is remainder of division by n ; n may not be a power of 2 or
- Count is arbitrary sequence of n states specifically designed state-by-state
- Includes modulo 10 which is the *BCD counter*

Design Example: Synchronous BCD

- Use the sequential logic model to design a synchronous BCD counter with D flip-flops
- Input combinations 1010 through 1111 are don't cares

State Table

Current State				Next State			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

are don't cares

$Q_{2n+1} \backslash Q_2 Q_1$		$Q_8 \backslash Q_4$			
		00	01	11	10
00	0	1	0	1	
01	0	1	0	1	
11	x	x	x	x	
10	0	0	x	x	

$Q_{4n+1} \backslash Q_2 Q_1$		$Q_8 \backslash Q_4$			
		00	01	11	10
00	0	0	1	0	
01	1	1	0	1	
11	x	x	x	x	
10	0	0	x	x	

$$Q_{1(n+1)} = \overline{Q_1}$$

$$Q_{2(n+1)} = Q_2 \oplus Q_1 \overline{Q_8}$$

$$Q_{4(n+1)} = Q_4 \oplus Q_1 Q_2$$

$$Q_{8(n+1)} = Q_8 \oplus (Q_1 Q_8 + Q_1 Q_2 Q_4)$$

Input Equations for Synchronous BCD



- Use K-Maps to two-level optimize the next state equations and manipulate into forms containing XOR gates:

$$D_1 = \overline{Q_1}$$

$$D_2 = Q_2 \oplus Q_1 \overline{Q_8}$$

$$D_4 = Q_4 \oplus Q_1 Q_2$$

$$D_8 = Q_8 \oplus (Q_1 Q_8 + Q_1 Q_2 Q_4)$$

- The logic diagram can be draw from these equations


- An asynchronous or synchronous reset should be added

- What happens if the counter is perturbed by a power disturbance or other interference and it enters a state other than 0000 through 1001?

The redundant state Synchronous BCD

- Find the actual values of the six next states for the **don't care combinations** from the equations
- Find the overall state diagram to assess behavior for the don't care states (states in decimal)

Present State				Next State			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1
1	0	1	0	1	0	1	1
1	0	1	1	0	1	1	0
1	1	0	0	1	1	0	1
1	1	0	1	0	1	0	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	1	0

 



Invalid state handling

- ❑ For the BCD counter design, if an invalid state is entered, return to a valid state occurs within **two clock cycles**
- ❑ Is this adequate? If not:
 - Is a signal needed that indicates that an invalid state has been entered? What is the equation for such a signal?
 - Does the design need to be modified to return from an invalid state to a valid state in one clock cycle?
 - Does the design need to be modified to return from a invalid state to a specific state (such as 0)?
- ❑ The action to be taken depends on:
 - the application of the circuit
 - design group policy
- ❑ See pages 244 of the text.



Modulo N Counters

Counting Modulo N




- ❑ The following techniques use an n -bit binary counter with asynchronous or synchronous clear and/or parallel load:
 - Detect a *terminal count* of N in a Modulo- N count sequence to *asynchronously* Clear the count to 0 or asynchronously Load in value 0 (These lead to counts which are present for only a *very short time* and can fail to work for some timing conditions!)
 - Detect a terminal count of $N - 1$ in a Modulo- N count sequence to Clear the count *synchronously* to 0
 - Detect a terminal count of $N - 1$ in a Modulo- N count sequence to synchronously *Load in value 0*
 - Detect a terminal count and use *Load to preset* a count of the terminal count value minus ($N - 1$)
- ❑ Alternatively, custom design a modulo N counter as done for BCD

Counting Modulo 7:

Detect 7 and **Asynchronously** Clear



- ❑ A synchronous 4-bit binary counter with an asynchronous Clear is used to make a Modulo 7 counter.
- ❑ Use the Clear feature to detect the count 7 and clear the count to 0. This gives a count of 0, 1, 2, 3, 4, 5, 6, 7(short)0, 1, 2, 3, 4, 5, 6, 7(short)0, etc.
- ❑ **DON'T DO THIS!** Existence of state 7 may not be long enough to reliably reset all flip-flops to 0. Referred to as a “suicide” counter! (Count “7” is “killed,” but the designer’s job may be dead as well!)

 


Counting Modulo 7:

(N-1)

Synchronously Load on Terminal Count of 6



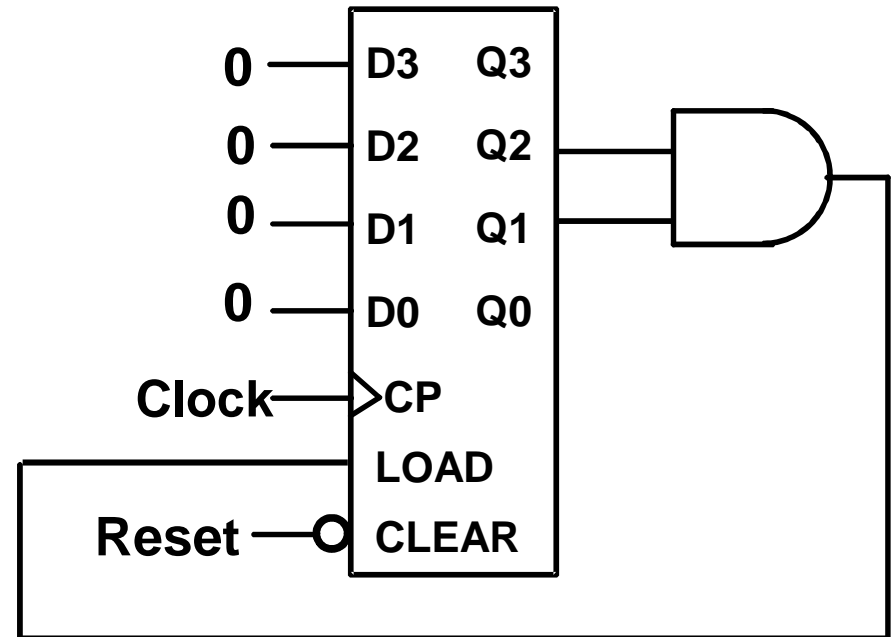
- ❑ A **synchronous** 4-bit binary counter with a synchronous load and an asynchronous clear is used to make a Modulo 7 counter
- ❑ Use the Load feature to detect the count "6" and load in "zero". This gives a count of 0, 1, 2, 3, 4, 5, 6, 0, 1, 2, 3, 4, 5, 6, 0, ...
- ❑ Using don't cares for states above 0110, detection of 6 can be done with $\text{Load} = Q_2 Q_1$





Counting Modulo 6: Synchronously Preset 9 on Reset and Load 9 on Terminal Count 14



 
- A synchronous, 4-bit binary counter with a synchronous Load is to be used to make a Modulo 6 counter.
- Use the Load feature to preset the count to 9 on Reset and detection of count 14.
- This gives a count of 9, 10, 11, 12, 13, 14, 9, 10, 11, 12, 13, 14, 9, ...
- If the terminal count is 15 detection is usually built in as Carry Out (CO)



Fixed Sequences Modulo 6

  

Course Outline

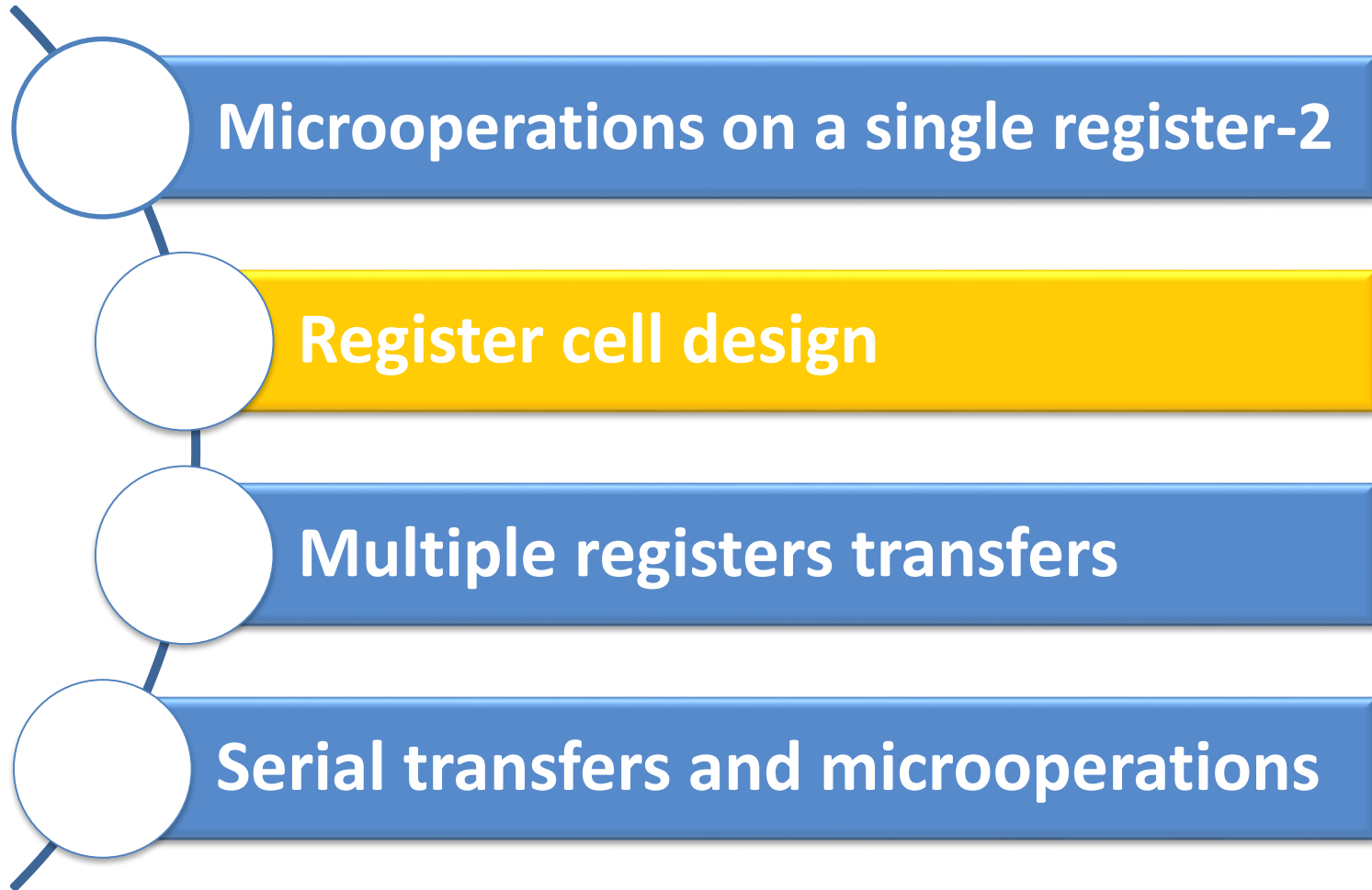



Register Cell Design

- Assume that a register consists of identical cells
- Then register design can be approached as follows:
 - Design representative cell for the register
 - Connect copies of the cell together to form the register
 - Applying appropriate “**boundary conditions**” to cells that need to be different and contract if appropriate
- **Register cell** design is the first step of the above process



Register Cell Specifications

- ❑ **A register**
- ❑ **Data inputs to the register**
- ❑ **Control input combinations to the register**
 - **Example 1: Not encoded**
 - ❑ Control inputs: Load, Shift, Add
 - ❑ At most, one of Load, Shift, Add is 1 for any clock cycle
(0,0,0), (1,0,0), (0,1,0), (0,0,1)
 - **Example 2: Encoded**
 - ❑ Control inputs: S1, S0
 - ❑ All possible binary combinations on S1, S0
(0,0), (0,1), (1,0), (1,1)



Register Cell Specifications

□ A set of register functions (typically specified as register transfers)

■ Example:

Load: $A \leftarrow B$

Shift: $A \leftarrow \text{sr } B$

Add: $A \leftarrow A + B$

□ A hold state specification


■ Example:

□ Control inputs: Load, Shift, Add

□ If all control inputs are 0, hold the current register state

Multiplexer Approach

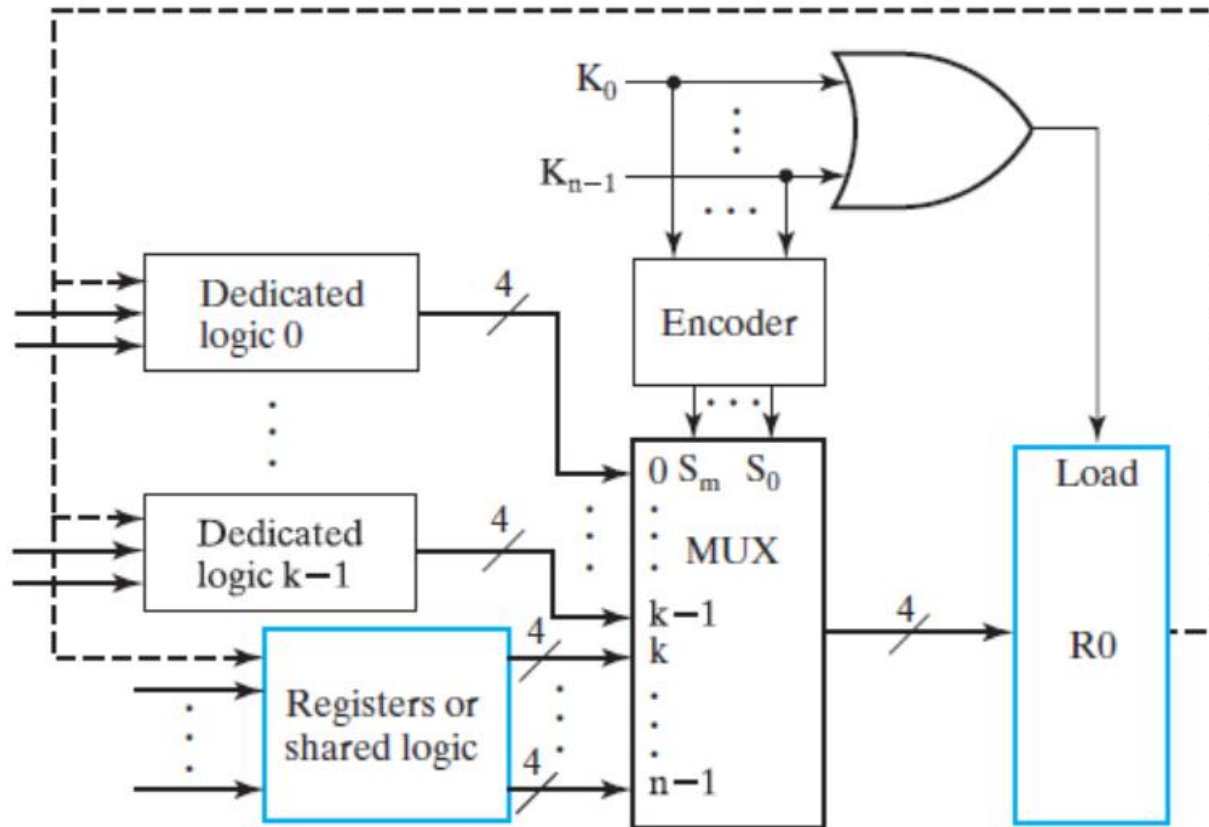- Uses an n-input multiplexer with a variety of transfer sources and functions




Multiplexer Approach

- ❑ Load enable by OR of control signals K_0, K_1, \dots, K_{n-1}
 - assumes no load for 00...0

- ❑ Use:

- Encoder + Multiplexer (shown) or
- $n \times 2$ AND-OR

to select sources and/or transfer functions

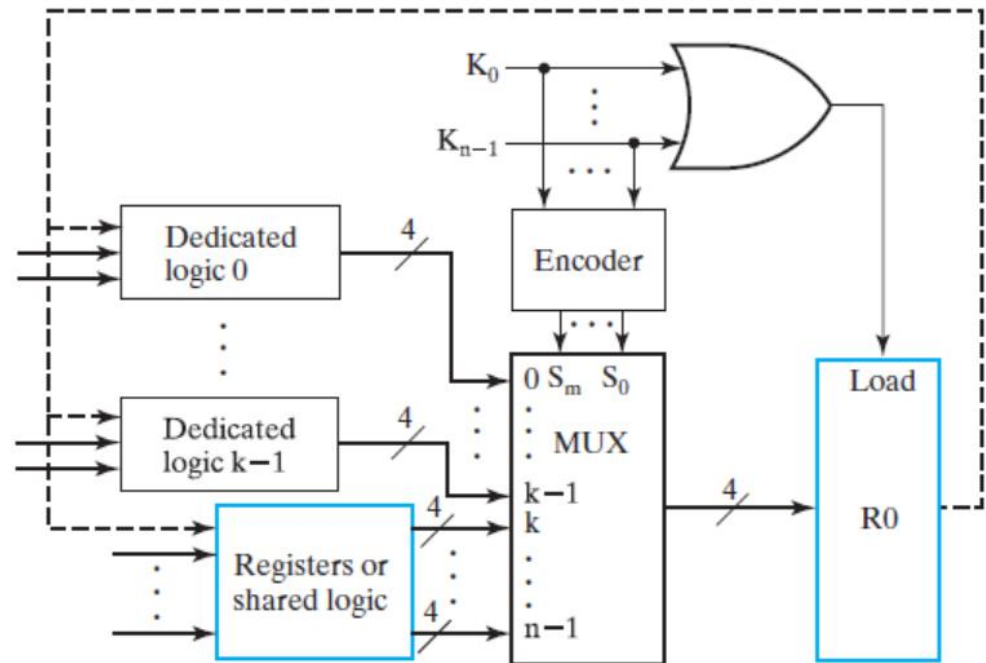



Example 1: Register Cell Design

□ Register A (m-bits) Specification:

- Data input: B
- Control inputs (CX, CY)
- Control input combinations (0,0), (0,1) (1,0)
- Register transfers:
 - CX: $A \leftarrow B \vee A$
 - CY : $A \leftarrow B \oplus A$
- Hold state: (0,0)

Register Cell Design



□ Load Control

$$\text{Load} = \text{CX} + \text{CY}$$

□ Since all control combinations appear as if encoded (0,0), (0,1), (1,0) can use multiplexer without encoder:

$$S1 = \text{CX}$$

$$S0 = \text{CY}$$

$$\text{D0} = A_i \quad \text{Hold A}$$

$$\text{D1} = A_i \leftarrow B_i \oplus A_i \quad \text{CY} = 1$$

$$\text{D2} = A_i \leftarrow B_i \vee A_i \quad \text{CX} = 1$$

□ Note that the decoder part of the 3-input multiplexer can be shared between bits if desired

Sequential Circuit Design Approach



SKIP

- **Find a state diagram or state table**
 - Note that there are only two states with the state assignment equal to the register cell output value
- **Use the design procedure in Chapter 5 to complete the cell design**
- **For optimization:**
 - Use K-maps for up to 4 to 6 variables
 - Otherwise, use computer-aided or manual optimization

Example 1 Again

□ State Table:

	Hold	$A_i \vee B_i$		$A_i \oplus B_i$	
A_i	$CX = 0$ $CY = 0$	$CX = 1$ $B_i = 0$	$CX = 1$ $B_i = 1$	$CY = 1$ $B_i = 0$	$CY = 1$ $B_i = 1$
0	0	0	1	0	1
1	1	1	1	1	0

- Four variables(CX 、 CY 、 A_i 、 B_i) give a total of 16 state table entries
 - By using:
 - Combinations of variable names and values
 - *Don't care* conditions (for $CX = CY = 1$)
- only 8 entries are required to represent the 16 entries

- $$\mathbf{D}_i(\mathbf{A}_{i(n+1)})$$





Example 1 Again (continued)

- The resulting SOP equation:

$$D_i = CX B_i + CY \bar{A}_i B_i + A_i \bar{B}_i + \bar{C}\bar{Y} A_i$$

- Using factoring and DeMorgan's law:

$$D_i = CX B_i + \bar{A}_i (CY B_i) + A_i (\overline{CY B_i})$$

$$D_i = CX B_i + A_i \oplus (CY B_i)$$

The gate input cost per cell = $2 + 8 + 2 + 2 = 14$


- The gate input cost per cell for the previous version is:

Per cell: 19

Shared decoder logic: 8

- Cost gain by sequential design > 5 per cell
- Also, no Enable on the flip-flop makes it cost less

Course Outline

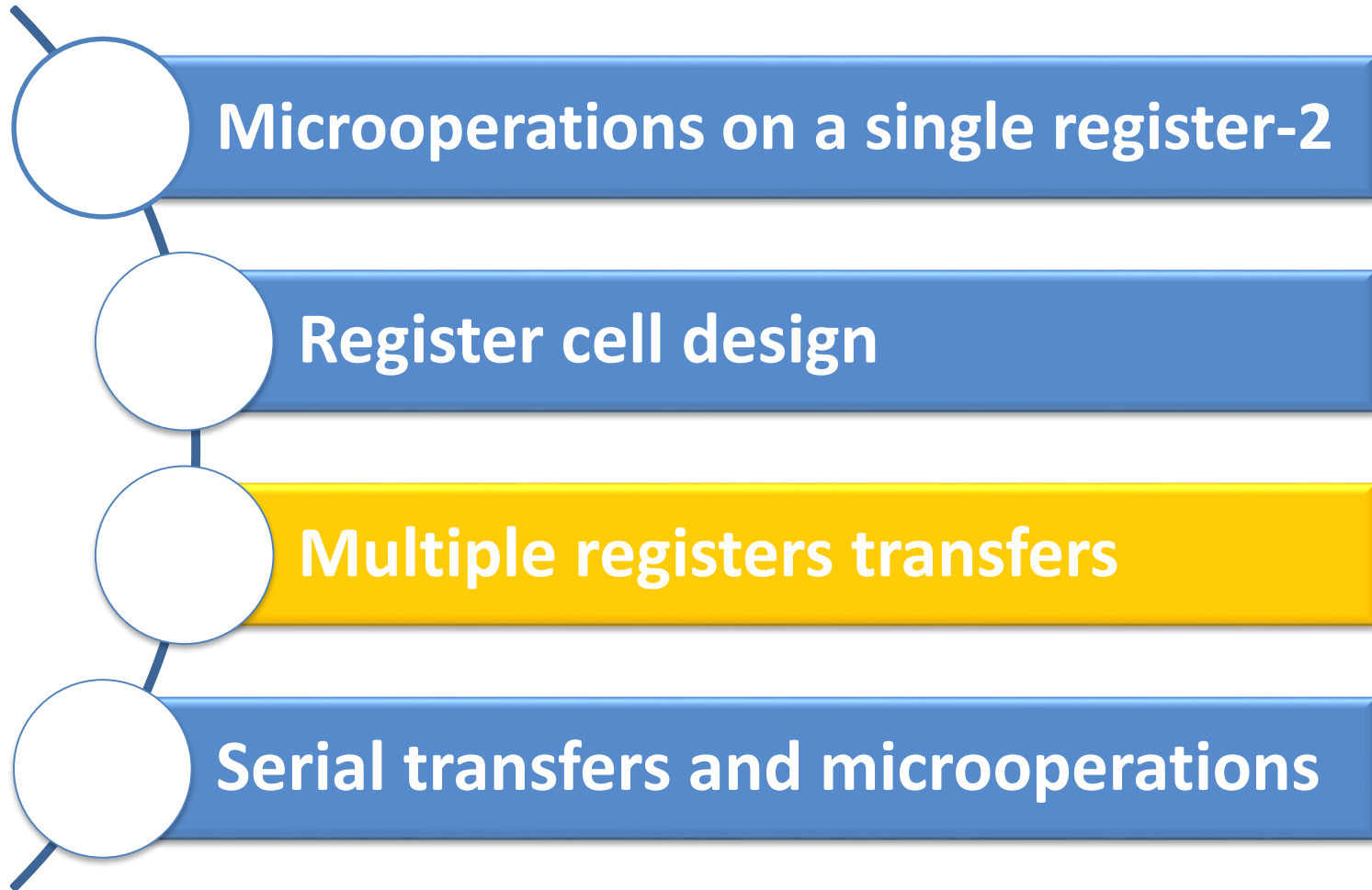


Multiplexer and Bus-Based Transfers for Multiple Registers



- ❑ ***Multiplexer dedicated*** to each register
- ❑ ***Shared*** transfer paths for registers
 - A shared transfer object is called a *bus* (Plural: *buses*)
- ❑ **Bus implementation using:**
 - multiplexers
 - three-state nodes and drivers
- ❑ **In most cases, the number of bits is the length of the receiving register**


Dedicated MUX-Based Transfers

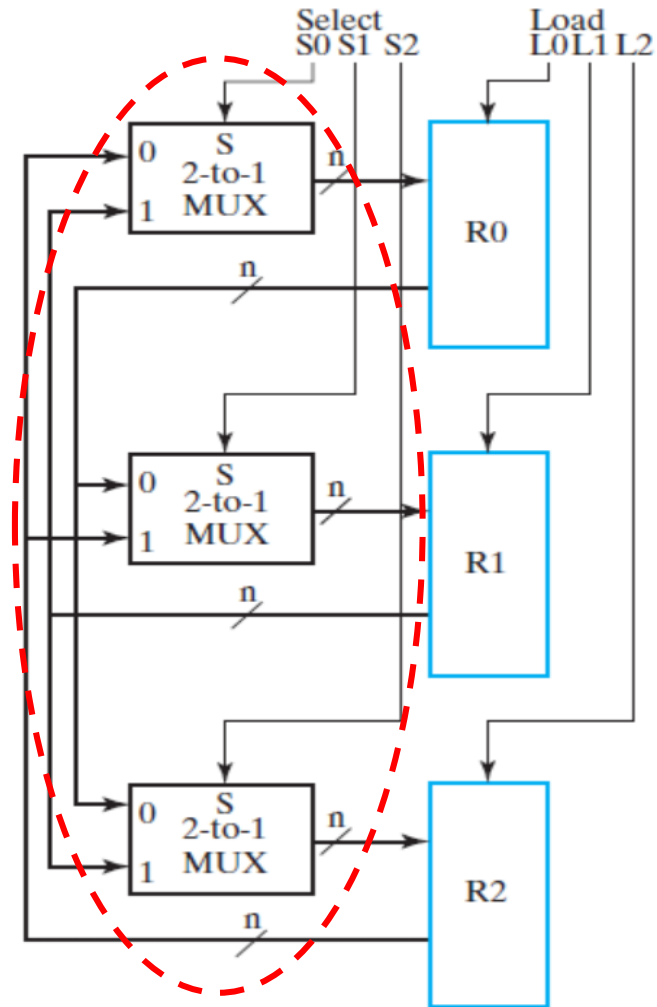- ❑ Multiplexer connected to each register input produces a very flexible transfer structure =>
- ❑ Characterize the simultaneous transfers possible with this structure.




Multiplexer *Bus*

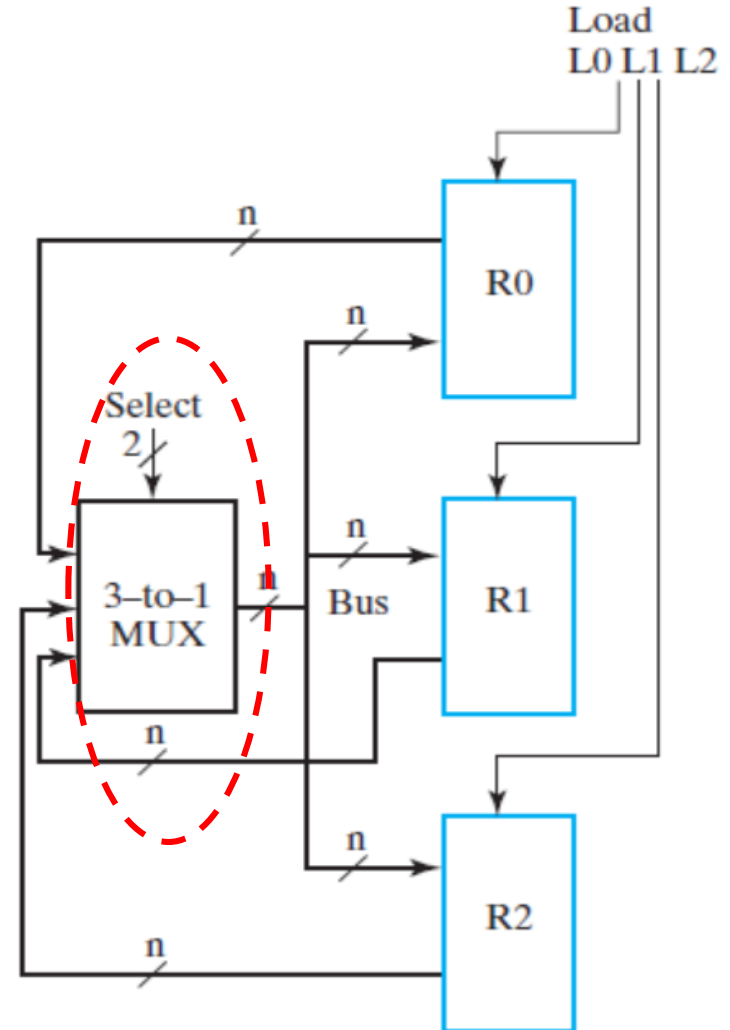- ❑ A single bus driven by a multiplexer lowers cost, but limits the available transfers =>
- ❑ Characterize the simultaneous transfers no possible with this structure.
- ❑ Characterize the cost savings compared to dedicated multiplexers




Three-State Bus

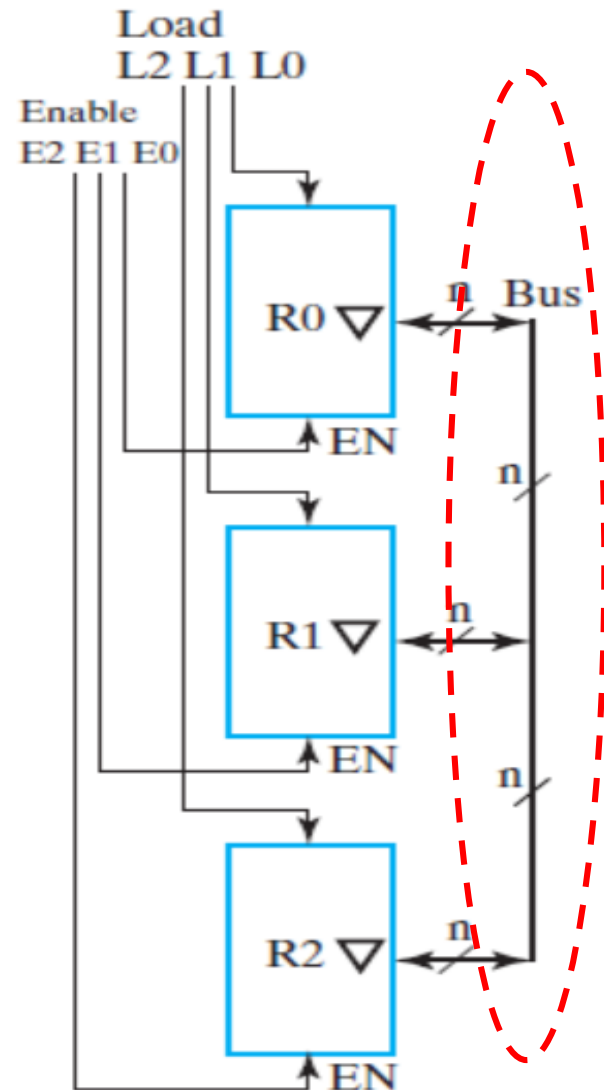- ❑ The 3-input MUX can be replaced by a 3-state node (bus) and 3-state buffers.
- ❑ Cost is further reduced, but transfers are limited
- ❑ Characterize the simultaneous transfers not possible with this structure.
- ❑ Characterize the cost savings and compare
- ❑ Other advantages?



Course Outline

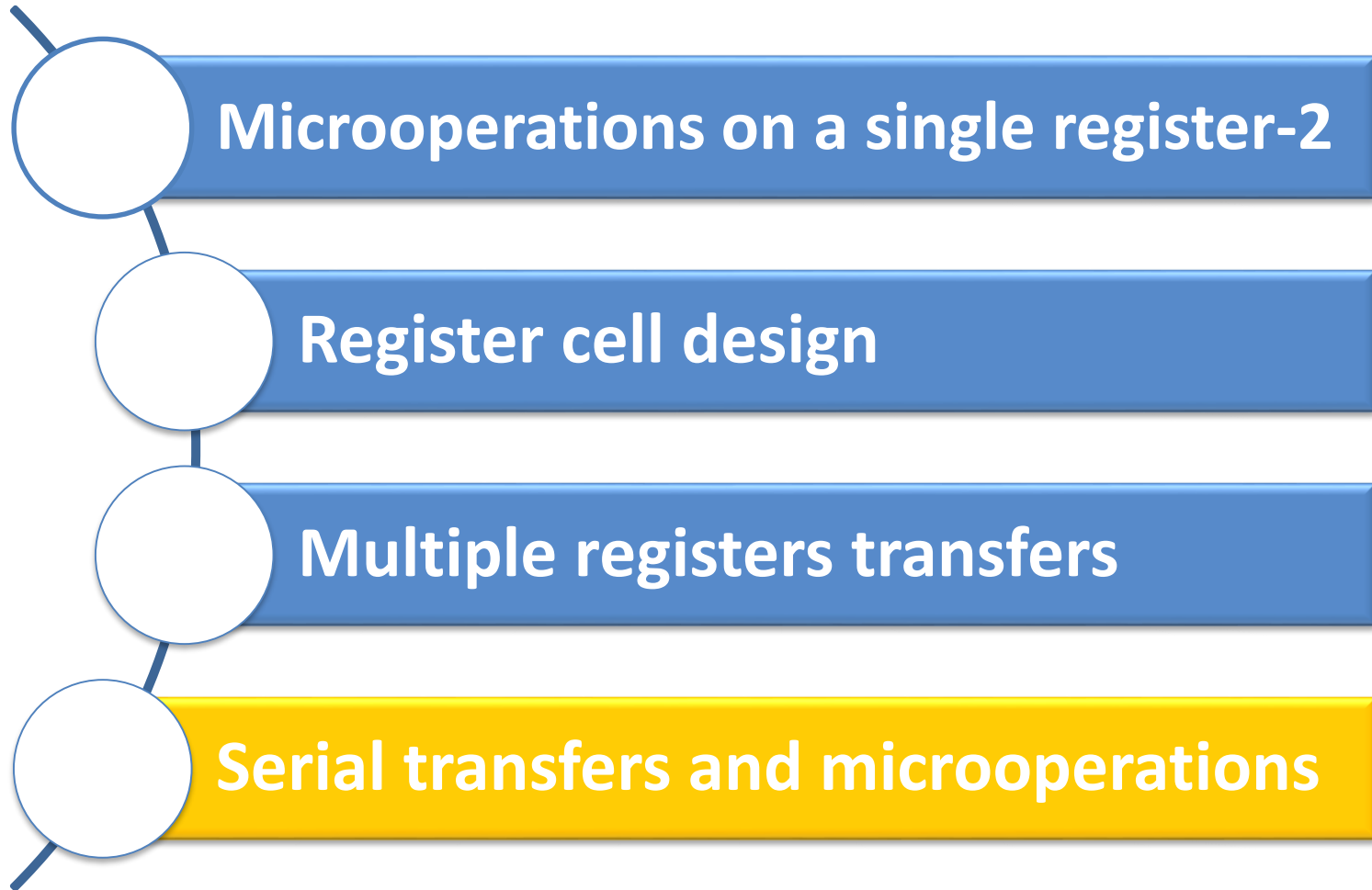



Serial Transfers and Microoperations

□ Serial Transfers

- Used for “narrow” transfer paths
- Example 1: Telephone or cable line
 - Parallel-to-Serial conversion at source
 - Serial-to-Parallel conversion at destination
- Example 2: Initialization and Capture of the contents of many flip-flops for test purposes
 - Add shift function to all flip-flops and form large shift register
 - Use shifting for simultaneous Initialization and Capture operations

□ Serial microoperations

- Example 1: Addition
- Example 2: Error-Correction for CDs




Serial Microoperations


- By using two shift registers for operands, a full adder, and a flip flop (for the carry), we can add two numbers serially, starting at the least significant bit.
- Serial addition is a low cost way to add large numbers of operands, since a “tree” of full adder cells can be made to any depth, and each new level doubles the number of operands.
- Other operations can be performed serially as well, such as parity generation/checking or more complex error-check codes.
- Shifting a binary number left is equivalent to **multiplying by 2**.
- Shifting a binary number **right** is equivalent to **dividing by 2**.

Synchronous serial transfer

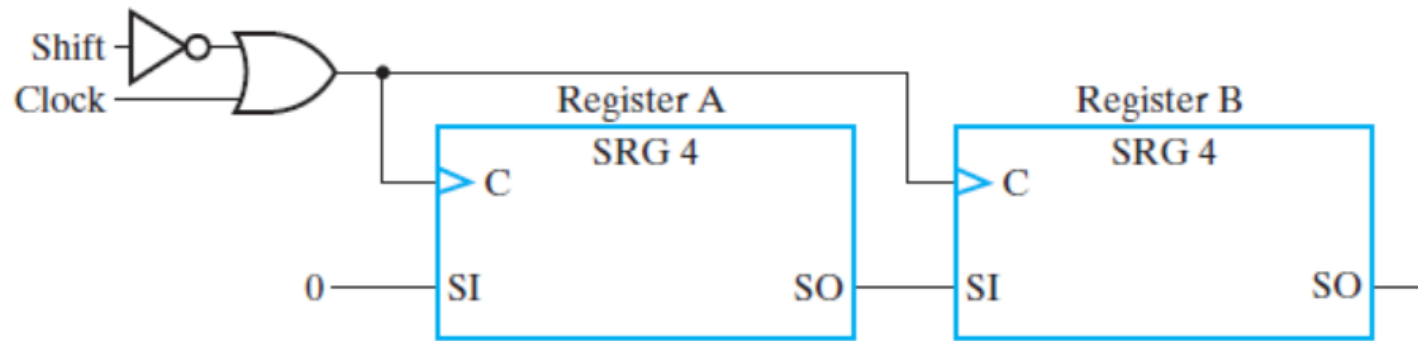- The serial transfer of information from register *A* to register *B* is done with shift register




(a) Block diagram

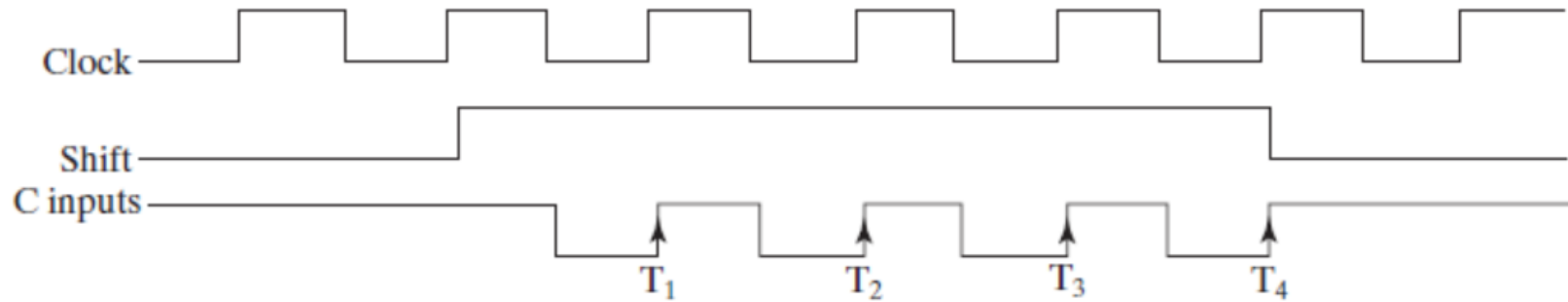


(b) Timing diagram



Asynchronous serial transfer

 

(a) DB25针接口

 


(b) DB9针接口

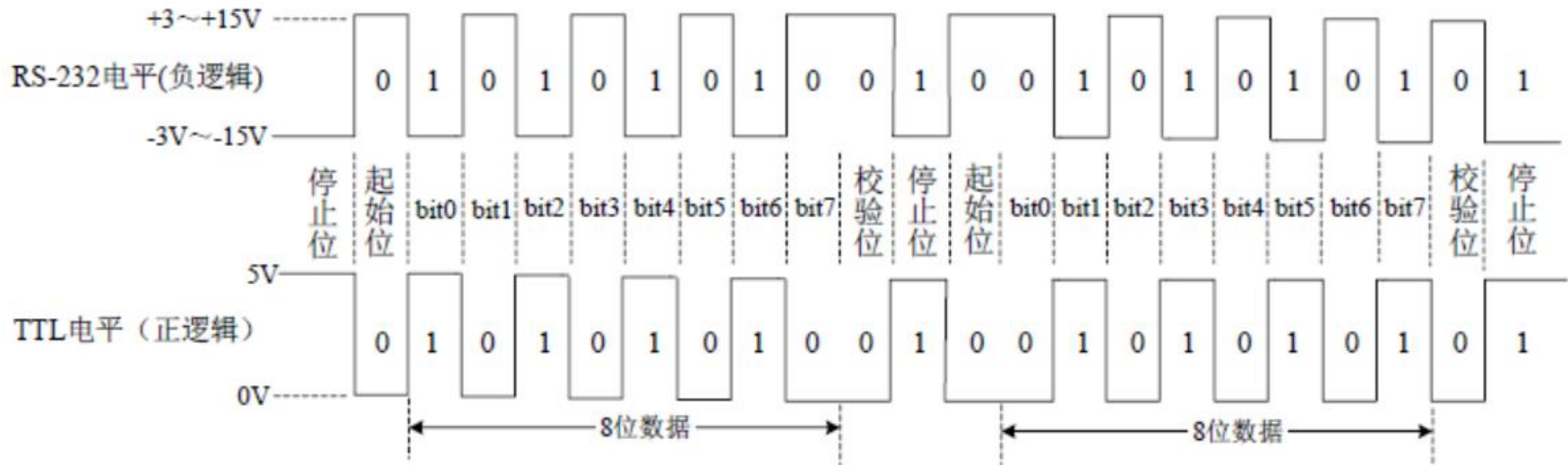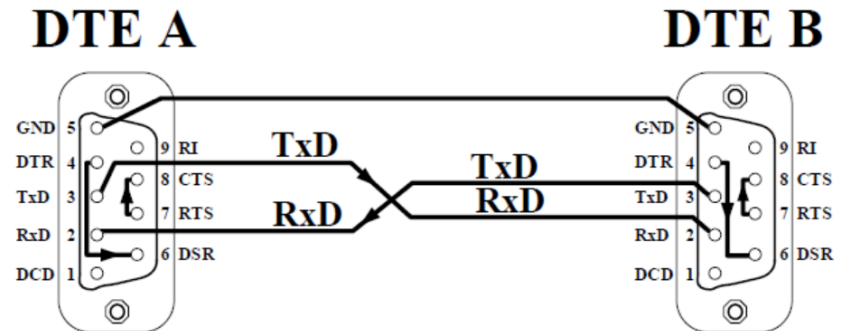

Serial Adder

- ❑ The circuit shown uses two shift registers for operands A(3:0) and B(3:0).
- ❑ A full adder, and one more flip flop (for the carry) is used to compute the sum.
- ❑ The result is stored in the A register and the final carry in the flip-flop
- ❑ With the operands and the result in shift registers, a tree of full adders can be used to add a large number of operands. Used as a common digital signal processing technique.

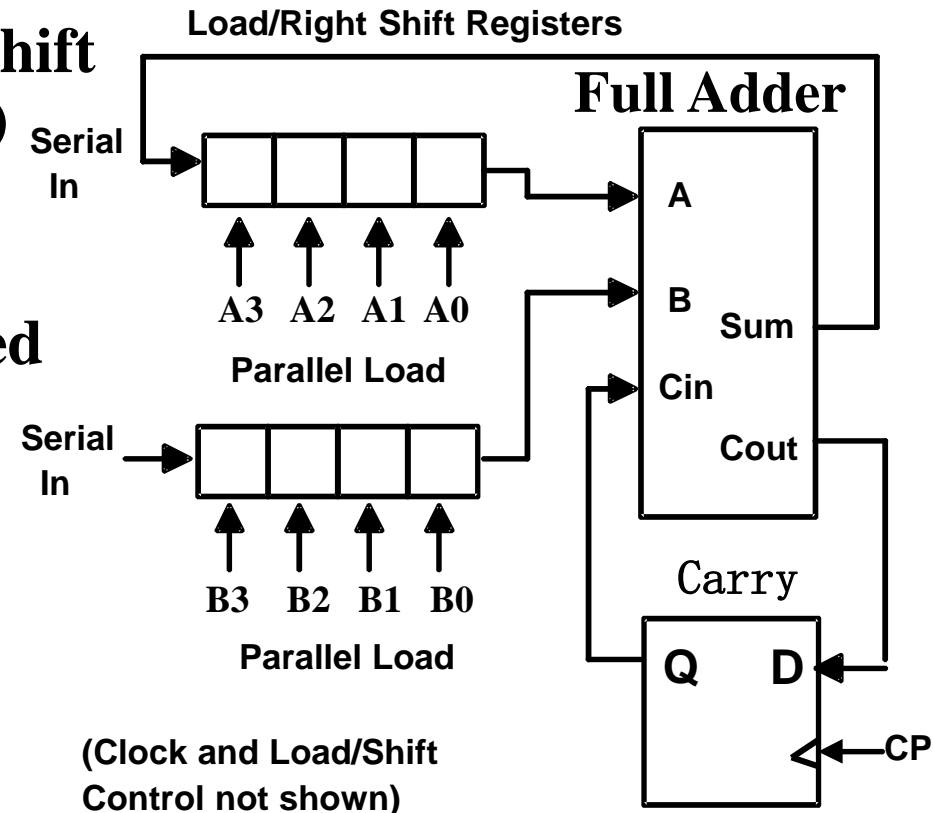



第六章作业 二

Ch6-2

page392-393:

6-6, 6-13, 6-16, 6-17, 6-19

From Registers To Registers, On this matter!

Thank you!



Quiz

1. **A serial 2's complementer is to be designed. A binary integer of arbitrary length is presented to the serial 2's complementer, least significant bit first, on input X. When a given bit is presented on input X, the corresponding output bit is to appear during the same clock cycle on output Z. To indicate that a sequence is complete and that the circuit is to be initialized to receive another sequence, input Y becomes 1 for one clock cycle. Otherwise, Y is 0.**
 - a) **Find the state diagram for the serial 2's complementer.**
 - b) **Find the state table for the serial 2's complementer.**
 - c) **Find the output equations and next-state equations.**
 - d) **Draw the circuit diagram.**