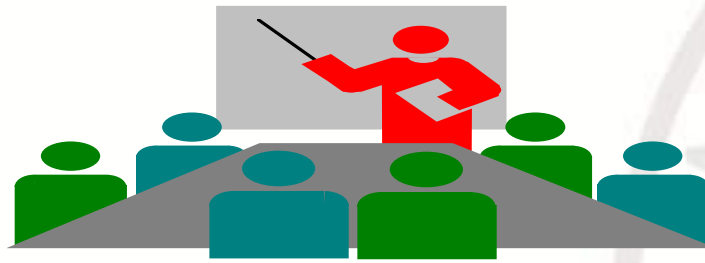




浙江大学
ZHEJIANG UNIVERSITY



数字逻辑设计

LOGIC and Computer Design Fundamentals

CHAPTER 4

Sequential Logic

Storage Elements and Sequential Circuit Analysis (part I)

施青松

Asso. Prof. Shi Qingsong

College of Computer Science and Technology, Zhejiang University

zjsqs@zju.edu.cn

□ Part 1 - Storage Elements and Analysis


- Introduction to sequential circuits
- Types of sequential circuits
- Storage elements
 - Latches
 - Flip-flops
- Sequential circuit analysis
 - State tables
 - State diagrams
 - Equivalent states
 - Moore and Mealy Models

□ Part 2 - Sequential Circuit Design

□ Part 3 – State Machine Design




Course Outline

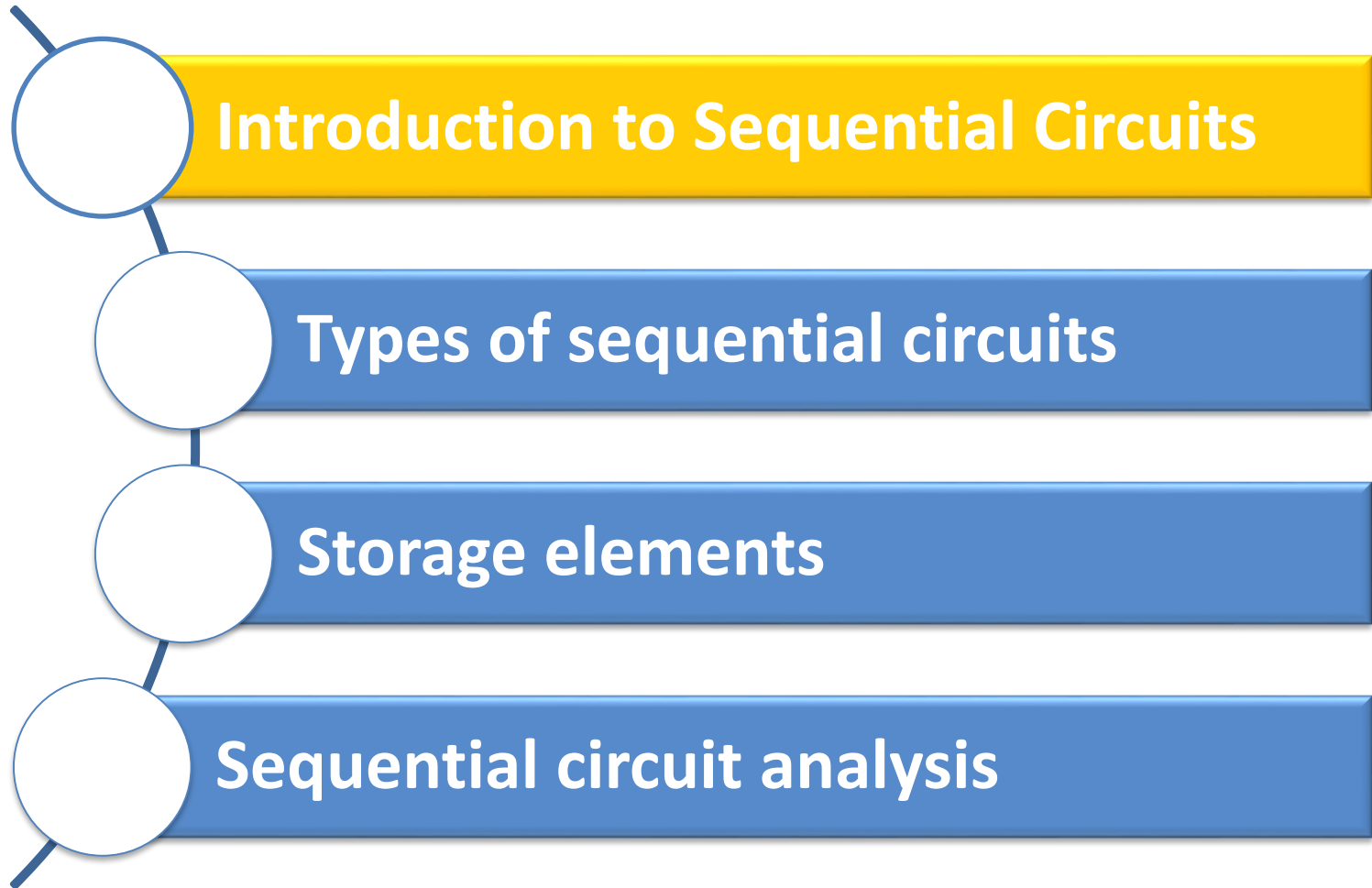

Introduction to Sequential Circuits

□ A Sequential circuit contains:

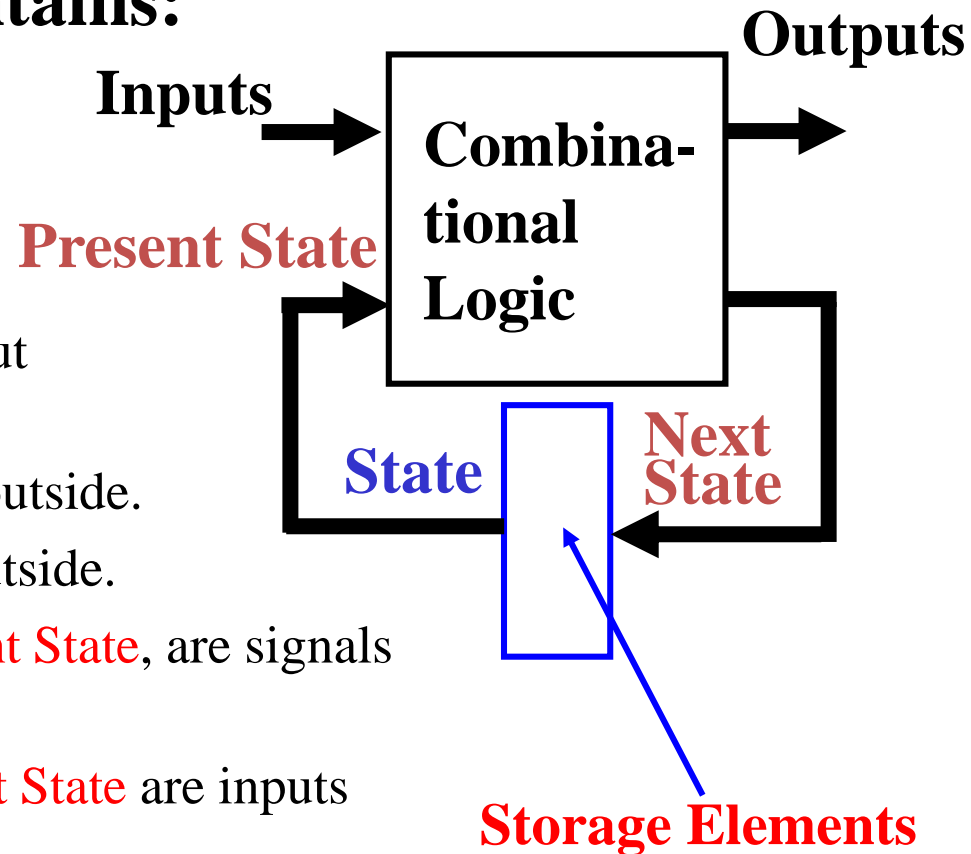- Storage elements:
Latches or Flip-Flops
- Combinational Logic:
 - Implements a multiple-output switching function
 - **Inputs** are signals from the outside.
 - **Outputs** are signals to the outside.
 - Other inputs, **State** or **Present State**, are signals from storage elements.
 - The remaining outputs, **Next State** are inputs to storage elements.



Introduction to Sequential Circuits



□ Combinatorial Logic

■ *Next state function*



Next State = $f(\text{Inputs}, \text{State})$

■ *Output function (Mealy)*

□ Outputs = $g(\text{Inputs}, \text{State})$


■ *Output function (Moore)*

□ Outputs = $h(\text{State})$

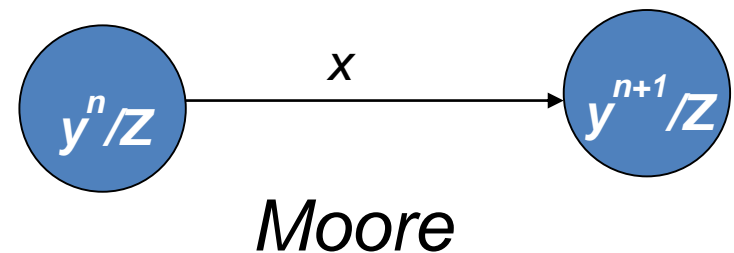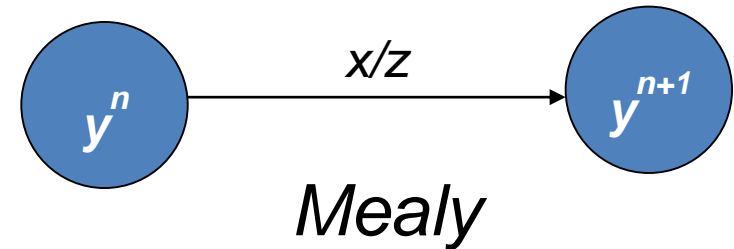

□ Output function type depends on specification and effects the design significantly

Course Outline

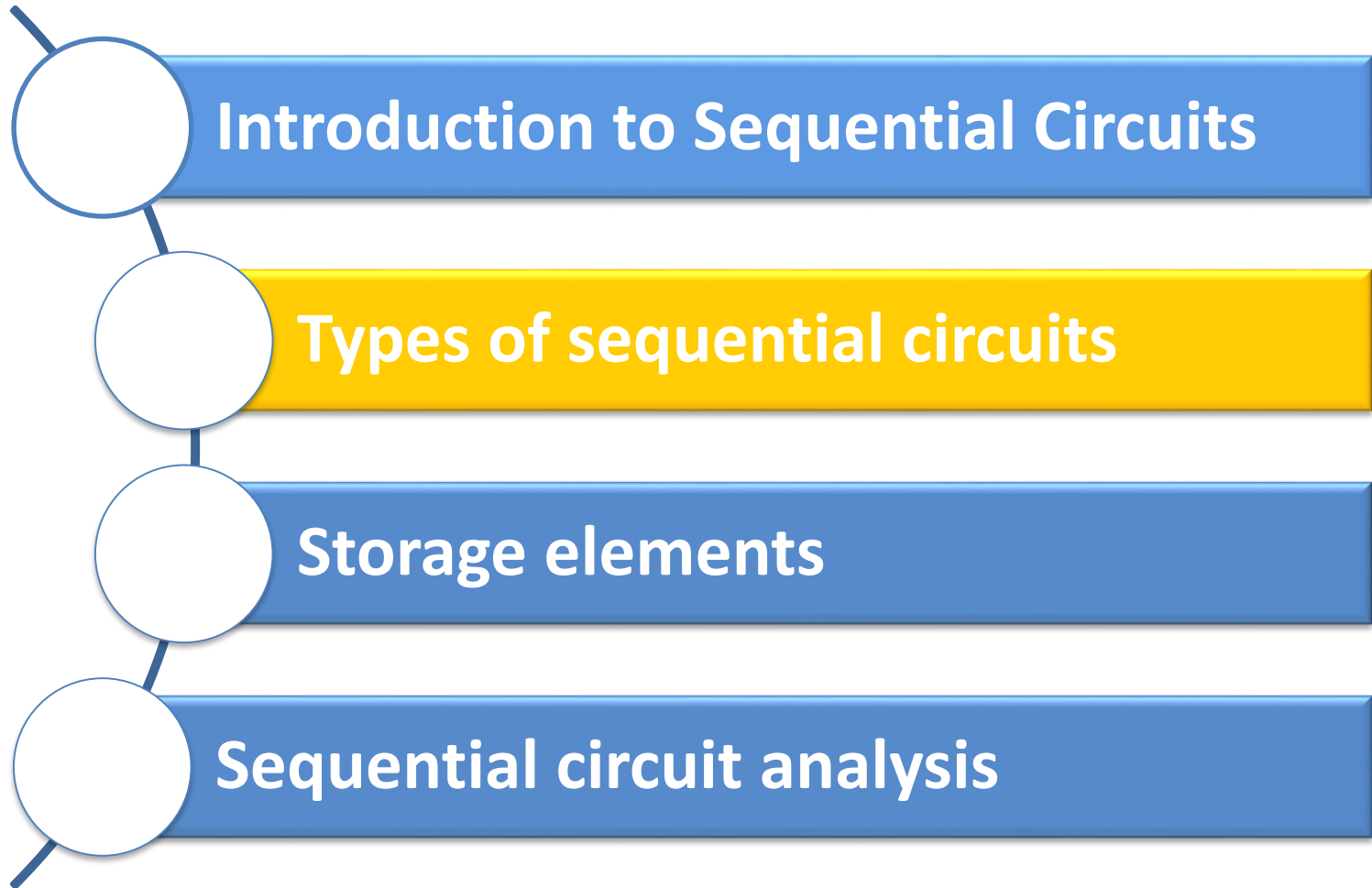



Types of Sequential Circuits

□ Depends on the **times** at which:

- storage elements observe their inputs, and
- storage elements change their state

□ Synchronous

- Behavior defined from knowledge of its signals at **discrete instances** of time
- Storage elements observe inputs and can change state only in relation to a timing signal (**clock pulses** from a **clock**)

□ Asynchronous

- Behavior defined from knowledge of inputs at **any instant of time** and the order in continuous time in which inputs change
- If **clock** just regarded as **another input**, all circuits are asynchronous!
- Nevertheless, the synchronous abstraction makes complex designs tractable!




Discrete Event Simulation

- ❑ In order to understand the time behavior of a sequential circuit we use **discrete event simulation**.
- ❑ Rules:
 - Gates modeled by an **ideal** (instantaneous) function and a **fixed gate delay**
 - Any **change in input values** is evaluated to see if it causes a **change in output value**
 - Changes in output values are scheduled for the fixed gate delay after the input change
 - At the time for a scheduled output change, the output value is changed along with any inputs it drives

Simulated NAND Gate

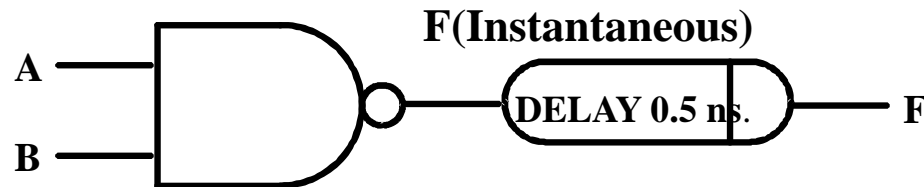- Example: A 2-Input NAND gate with a 0.5 ns. delay:






- Assume A and B have been 1 for a long time
- At time $t=0$, A changes to a 0 at $t=0.8$ ns, back to 1.

t (ns)	A	B	F(I)	F	Comment
$-\infty$	1	1	0	0	A=B=1 for a long time
0	$1 \Rightarrow 0$	1	$1 \Leftarrow 0$	0	F(I) changes to 1
0.5	0	1	1	$1 \Leftarrow 0$	F changes to 1 after a 0.5 ns delay
0.8	$1 \Leftarrow 0$	1	$1 \Rightarrow 0$	1	F(Instantaneous) changes to 0
0.13	1	1	0	$1 \Rightarrow 0$	F changes to 0 after a 0.5 ns delay



Gate Delay Models

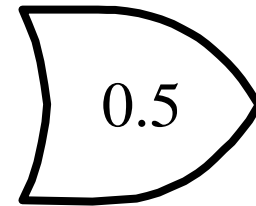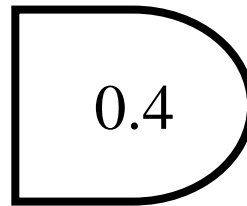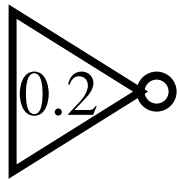- Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:



Circuit Delay Model

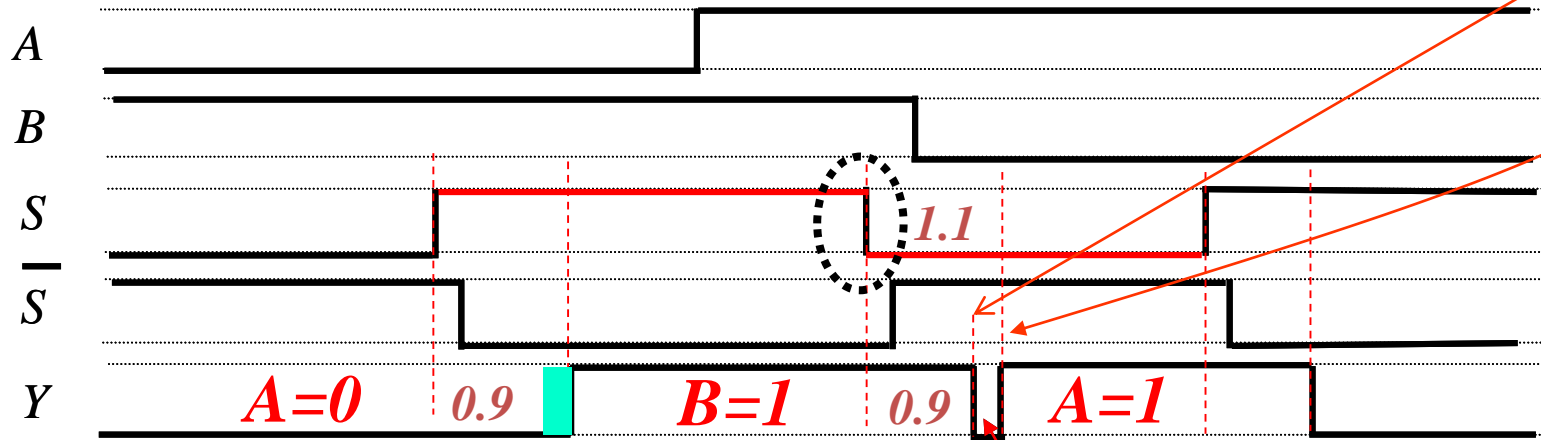
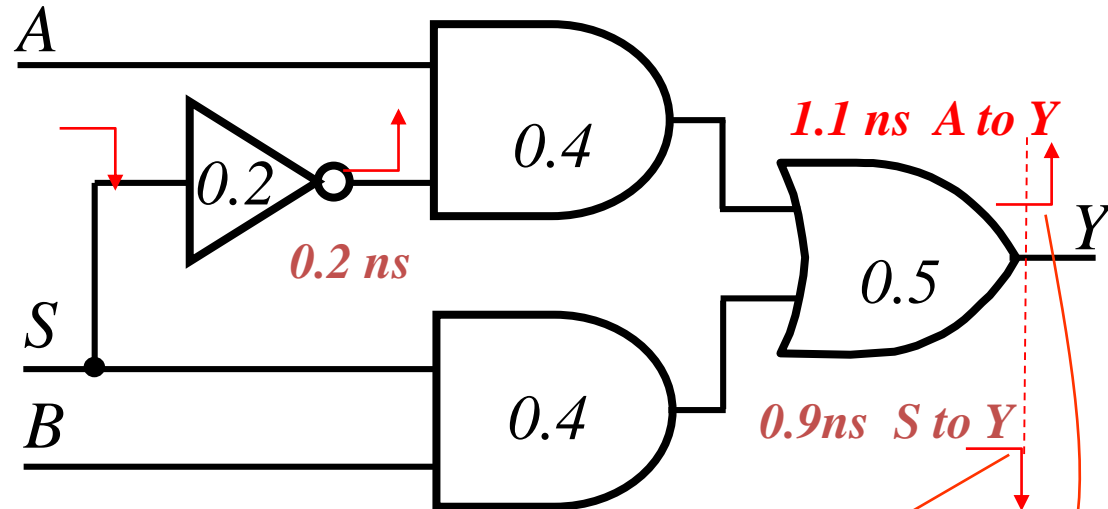
- Consider a simple 2-input multiplexer:
- With function:
 - $Y = A$ for $S = 1$
 - $Y = B$ for $S = 0$



- “Glitch” is due to delay of inverter

Storing State

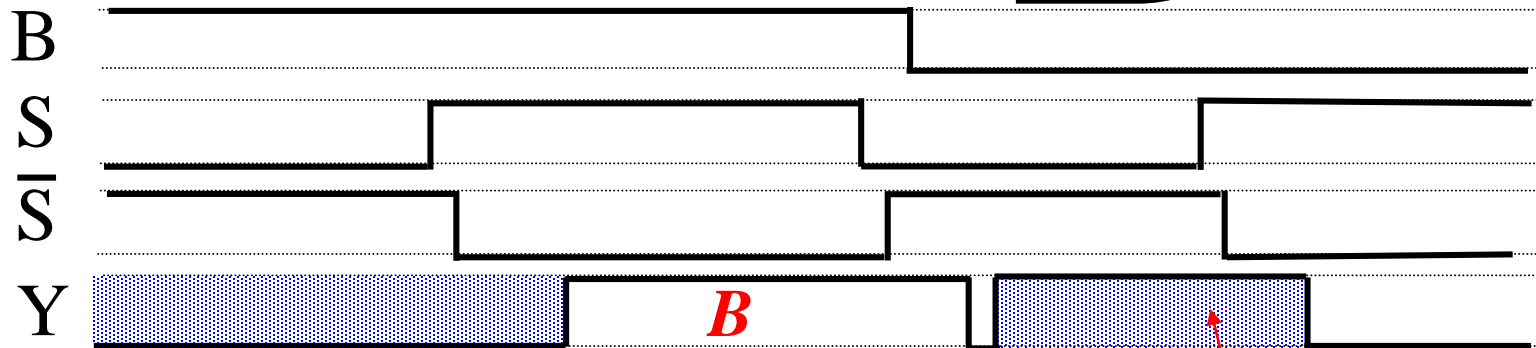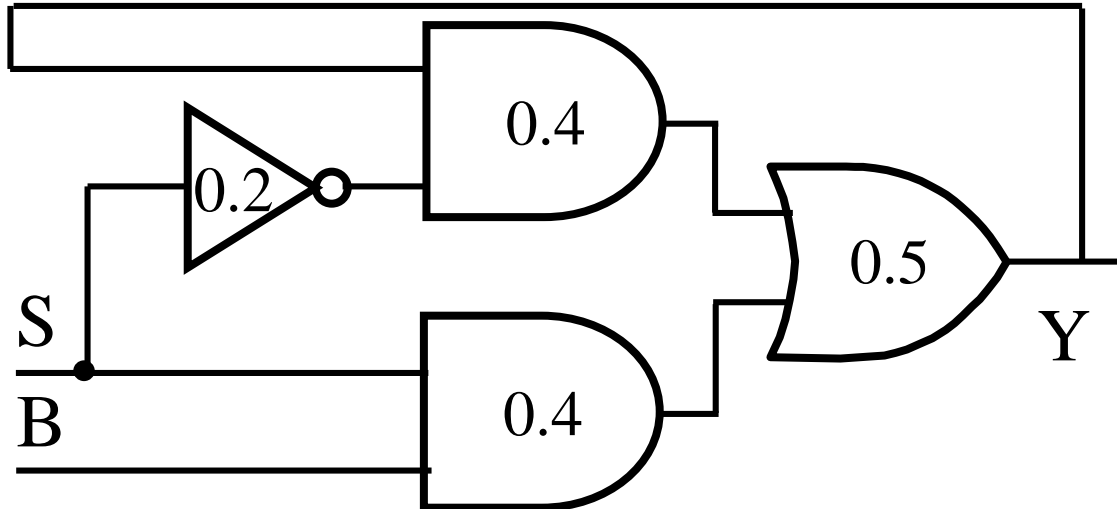- What if A connected to Y?
- Circuit becomes:
- With function:
 - $Y = B$ for $S = 1$, and $Y(t)$ dependent on $Y(t - 0.9)$ for $S = 0$



- The simple **combinational circuit** has now become a **sequential circuit** because its output is a function of a time sequence of input signals!

Storing State (Continued)


- Simulation example as input signals change with time. Changes occur every 100 ns, so that the tenths of ns delays are negligible.

Time	B	S	Y	Comment
	1	0	0	Y “remembers” 0
	1	1	1	Y = B when S = 1
	1	0	1	Now Y “remembers” B = 1 for S = 0
	0	0	1	No change in Y when B changes
	0	1	0	Y = B when S = 1
	0	0	0	Y “remembers” B = 0 for S = 0
	1	0	0	No change in Y when B changes

- Y represent the **state** of the circuit, not just an output.

Storing State (Continued)

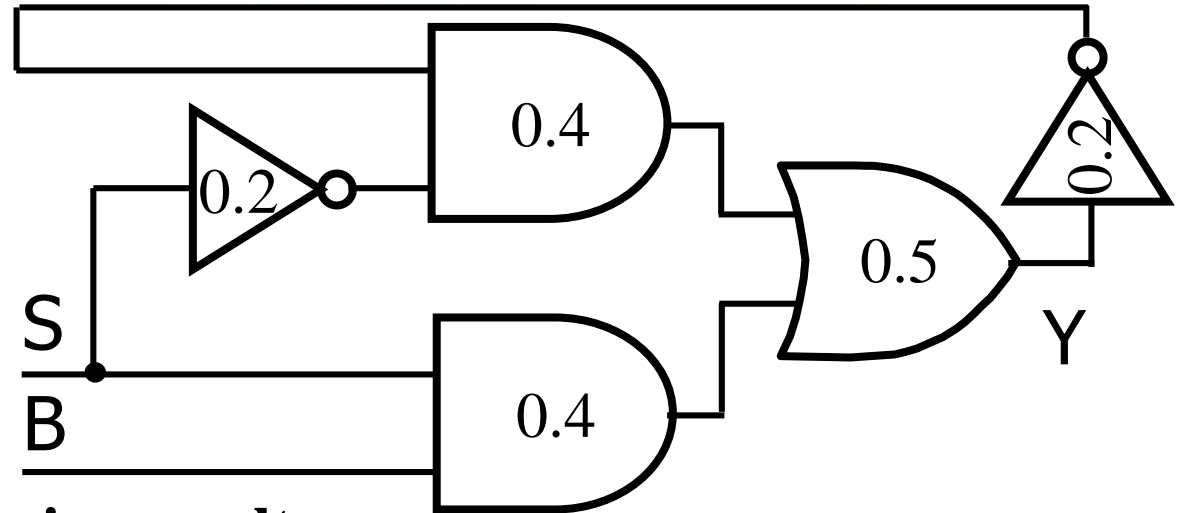- Suppose we place an inverter in the “feedback path.”




- The following behavior results:

- The circuit is said to be unstable.
- For $S = 0$, the circuit has become what is called an *oscillator*. Can be used as crude clock.

B	S	Y	Comment
0	1	0	$Y = B$ when $S = 1$
1	1	1	
1	0	1	Now Y “remembers” A
1	0	0	Y, 1.1 ns later
1	0	1	Y, 1.1 ns later
1	0	0	Y, 1.1 ns later

Course Outline

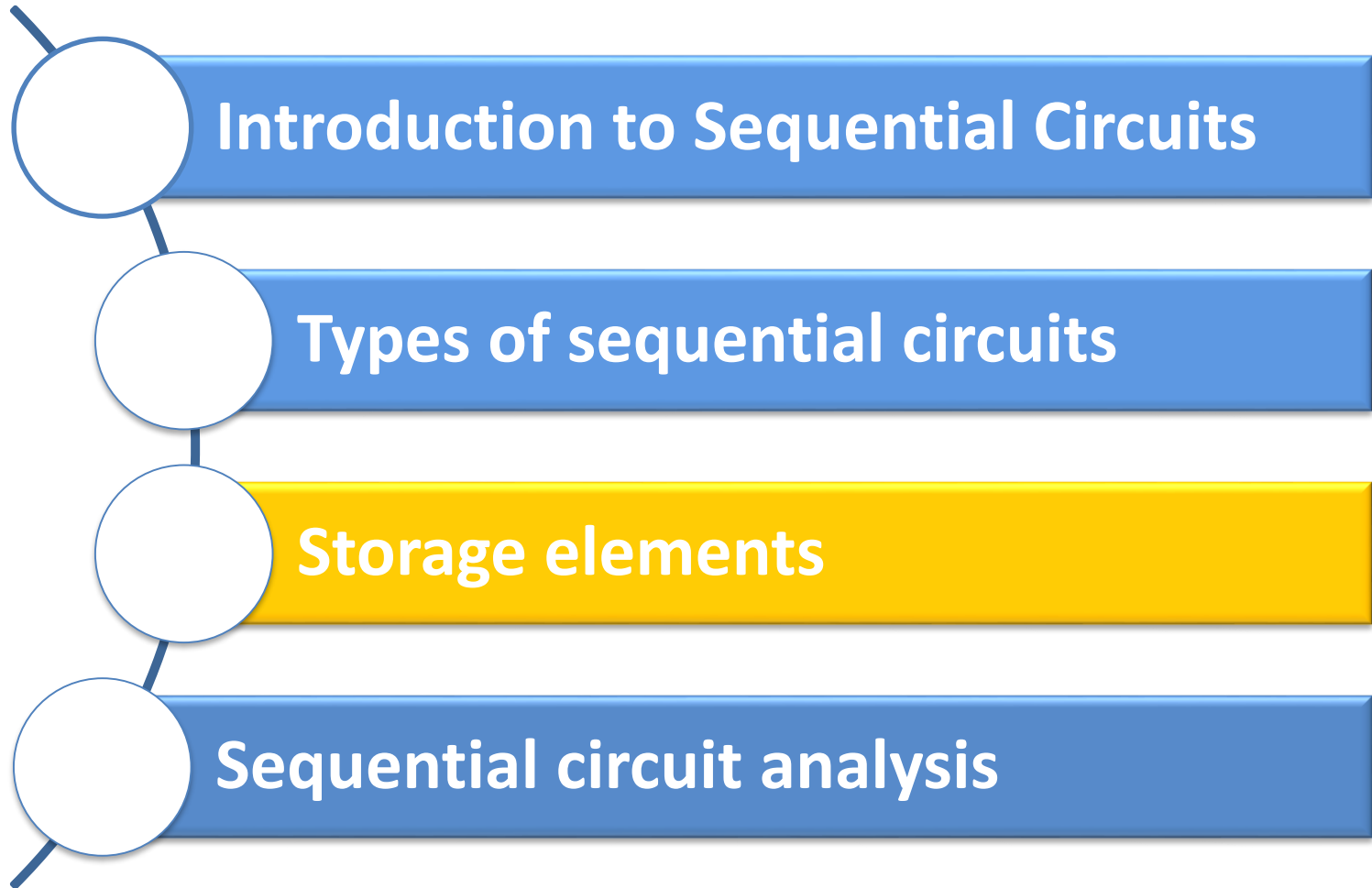



Latches

Latches

□ many components to storing historical state:

- Capacitors, Inductors, a delay line, a memory, etc.

- Latches, Triggers

□ Satisfy the following three conditions can be referred to as to as latches:

1. Long term maintaining a given stable state ;
2. There are two stable states, "0", "1";
3. Under certain conditions, can change state at anytime,
 - ie: set to “1” is set to “0”.


□ the most simple is latch RS latch and D latch



S-R Latch

Basic (NAND) \bar{S} – \bar{R} Latch

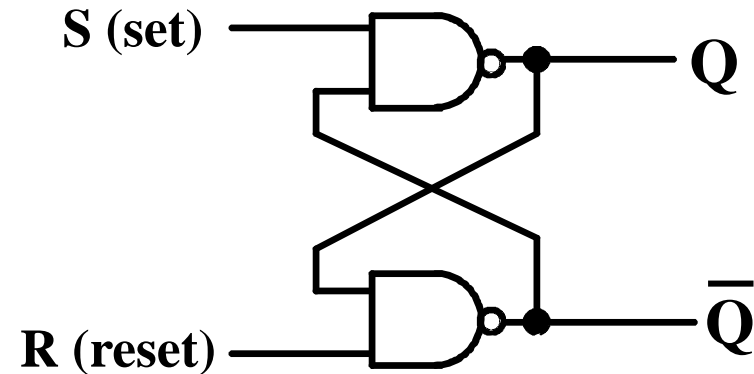- “Cross-Coupling” two NAND gates gives the \bar{S} – \bar{R} Latch:



- Which has the time sequence behavior:


Time

R	S	Q	\bar{Q}	Comment
1	1	Q	\bar{Q}	Stored state Hold
1	0	1	0	“Set” Q to 1
1	1	1	0	Now Q “remembers” 1
0	1	0	1	“Reset” Q to 0
1	1	0	1	Now Q “remembers” 0
0	0	1	1	Both go high
1	1	?	?	Stored state unknown

- $S = 0, R = 0$ is **forbidden** as input pattern

Basic (NOR) S – R Latch

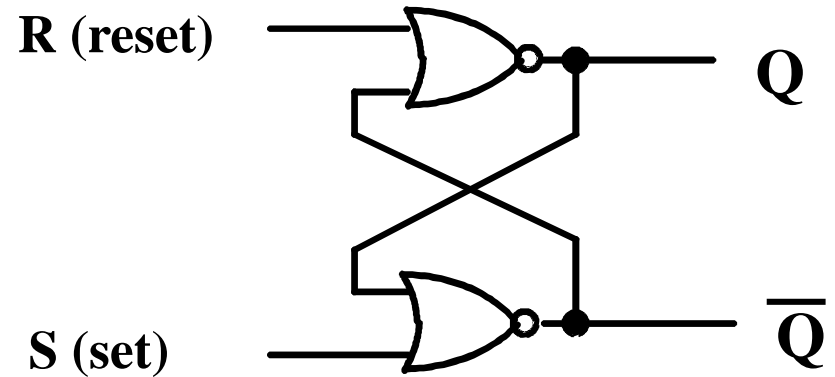- Cross-coupling two NOR gates gives the S – R Latch:




- Which has the time sequence behavior:

- $S = 1, R = 1$ is **forbidden** as input pattern

Time	R	S	Q	\bar{Q}	Comment
	0	0	Q	\bar{Q}	Stored state Hold
	0	1	1	0	“Set” Q to 1
	0	0	1	0	Now Q “remembers” 1
	1	0	0	1	“Reset” Q to 0
	0	0	0	1	Now Q “remembers” 0
	1	1	0	0	Both go low
	0	0	?	?	Stored state unknown!

Clocked S - R Latch

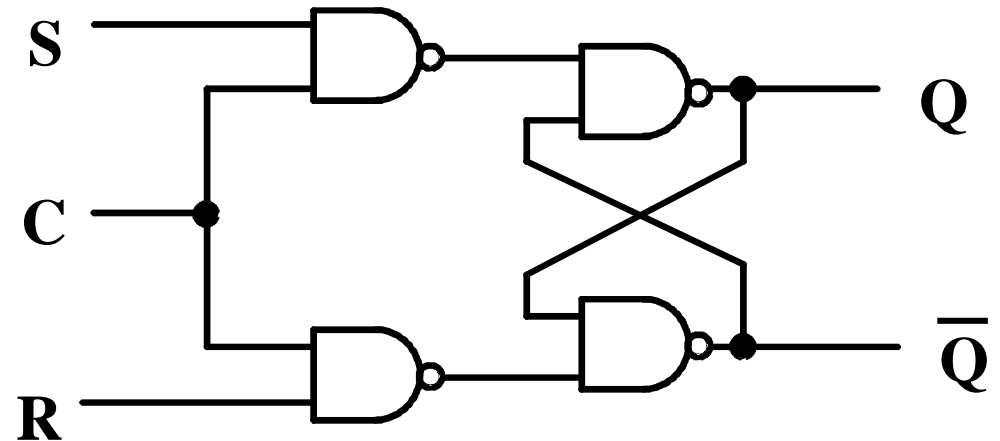
- Adding two NAND gates to the basic \overline{S} - \overline{R} NAND latch gives the clocked S - R latch:



- Has a time sequence behavior similar to the basic S-R latch **except that** the S and R inputs are only observed when the line C is high.
- C means “control” or “clock”.

Clocked S - R Latch (continued)

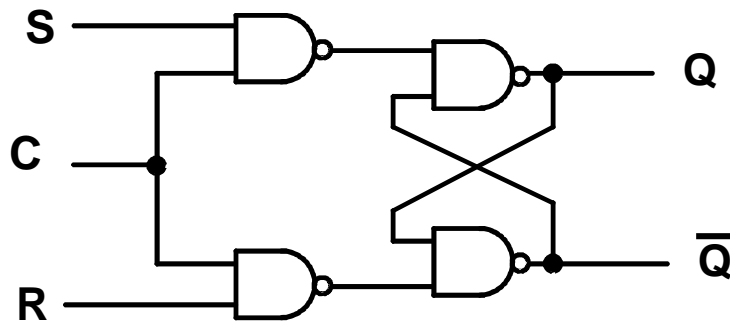- The Clocked S-R Latch can be described by a table:



- The table describes what happens after the clock [at time (t+1)] based on:
 - current inputs (S,R) and
 - current state $Q(t)$.

C	S	R	$Q(t + 1)$
0	X	X	holding
1	0	0	holding
1	0	1	Q=0: Reset
1	1	0	Q=1: Set
1	1	1	Indeterminate


$Q(t)$	S	R	$Q(t+1)$	Comment
0	0	0	0	No change
0	0	1	0	Clear Q
0	1	0	1	Set Q
0	1	1	???	Indeterminate
1	0	0	1	No change
1	0	1	0	Clear Q
1	1	0	1	Set Q
1	1	1	???	Indeterminate




D Latch

D Latch

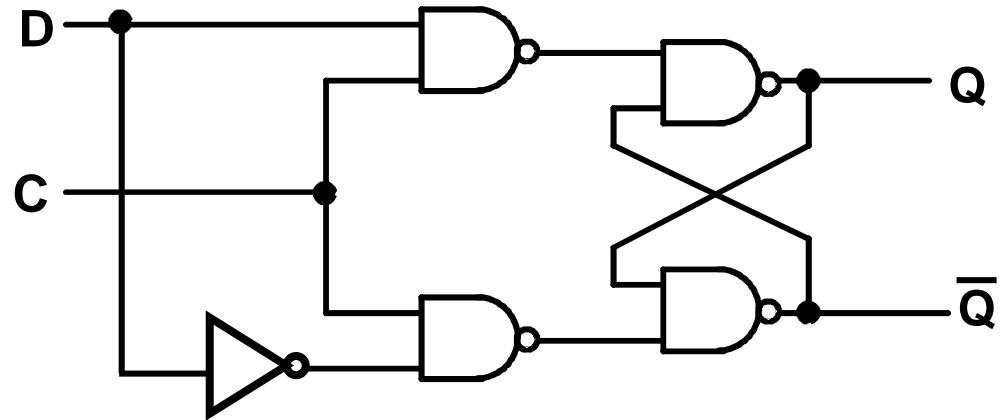- Adding an inverter to the S-R Latch, gives the D Latch:
- Note that there are no “indeterminate” states!



The graphic symbol for a D Latch is:

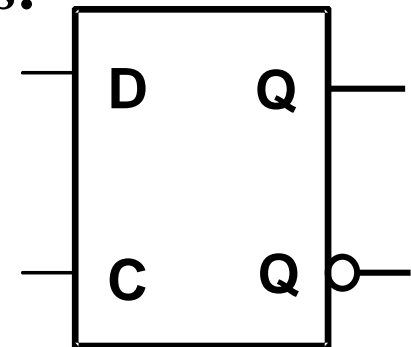

Q	D	Q(t+1)	Comment
0	0	0	No change
0	1	1	Set Q
1	0	0	Clear Q
1	1	1	No Change



The Latch Timing Problem



The Latch Timing Problem


- ❑ In a sequential circuit, paths may exist through combinational logic:
 - From **one** storage element to **another**
 - From a storage element back to the **same** storage element
- ❑ The combinational logic between a latch output and a latch input may be as simple as an interconnect
- ❑ For a clocked D-latch, the output Q depends on the input D whenever the clock input C has value 1



The Latch Timing Problem (continued)

□ Consider the following circuit:

□ Suppose that initially $Y = 0$.

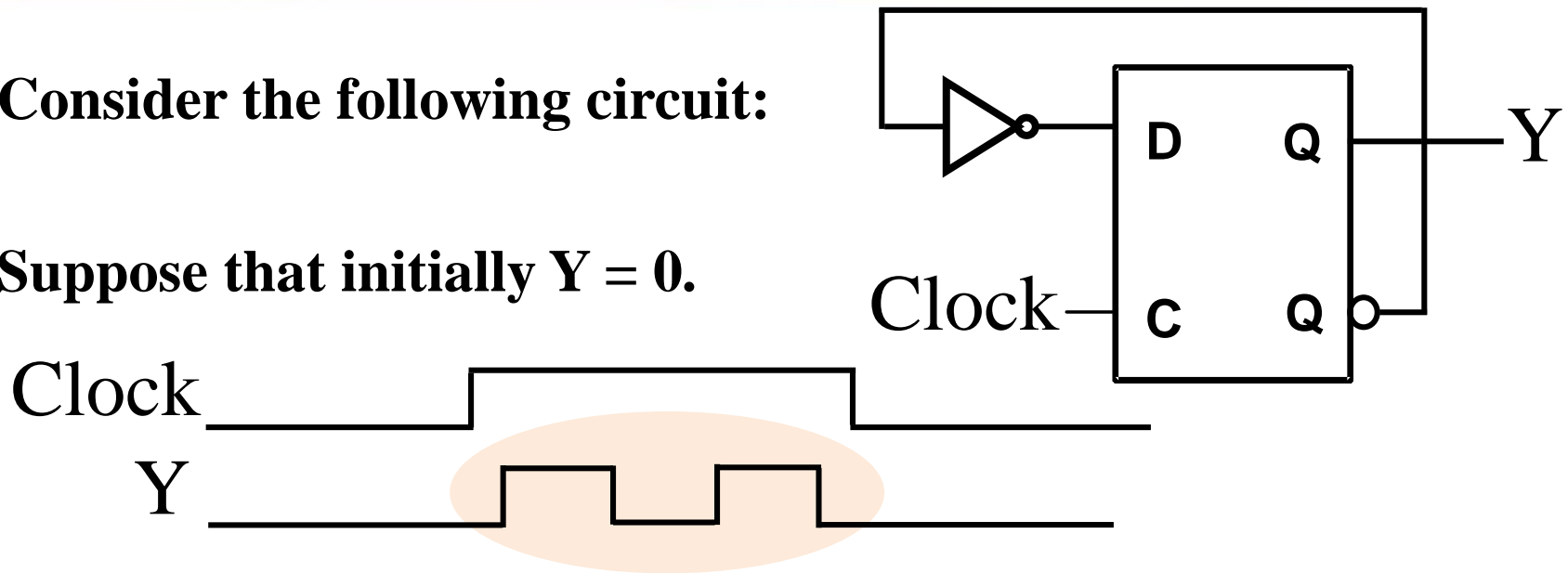

□ As long as $C = 1$, the value of Y **continues** to change!

□ The changes are based on the **delay** present on the loop through the connection **from Y back to Y**.

□ This behavior is clearly **unacceptable**.

□ **Desired behavior**: Y changes **only once** per clock pulse



The Latch Timing Problem (continued)

- A solution to the latch timing problem is to **break** the closed path from Y to Y within the storage element
- The commonly-used, path-breaking solutions replace the clocked D-latch with:
 - a master-slave flip-flop
 - an edge-triggered flip-flop




Triggers

S-R Triggers


S-R Master-Slave Flip-Flop



- Consists of two clocked S-R latches in series with the clock on the second latch inverted
- The input is observed by the first latch with $C = 1$
- The output is changed by the second latch with $C = 0$
- The path from input to output is broken by the difference in clocking values ($C = 1$ and $C = 0$).
- The behavior demonstrated by the example with D driven by Y given previously is prevented since the clock must change from 1 to 0 before a change in Y based on D can occur.

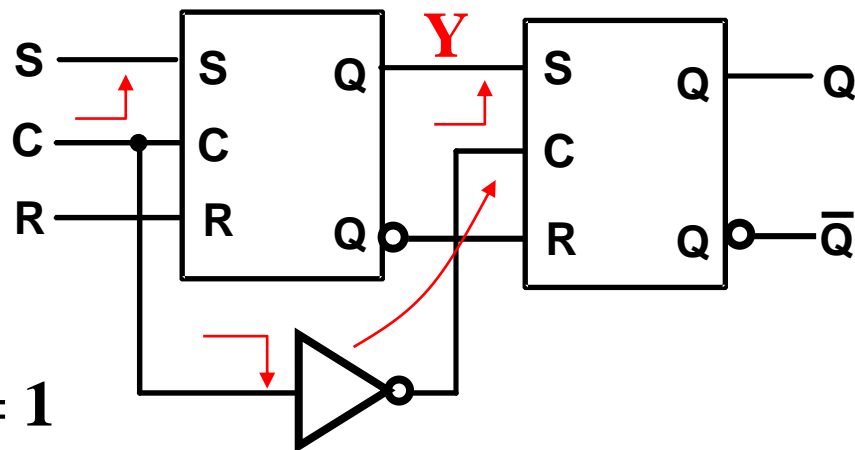

S-R Master-Slave timing-1

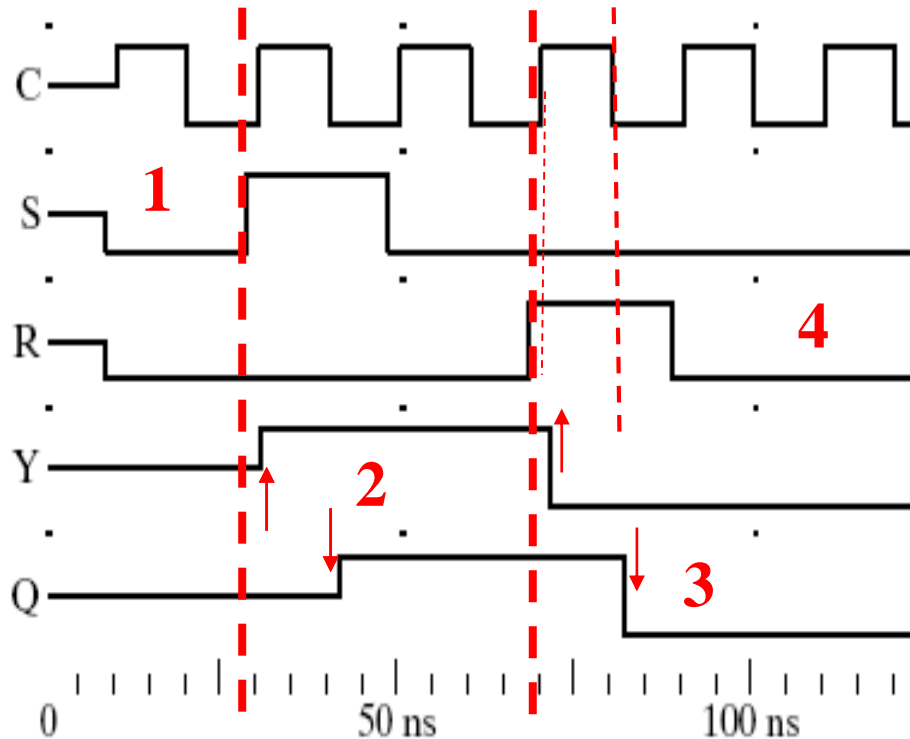


1. Hold
2. Reset "0"
3. Set "1"
4. Hold

- hold requirement:

- When the pulse arrives: $Q = 0$ and the before end of the pulse: $RS = 00$, Q should be kept to "0"
- When the pulse arrives: $Q = 1$ and the before end of the pulse: $RS = 00$, Q should be kept to "1"

S-R Master-Slave timing-2

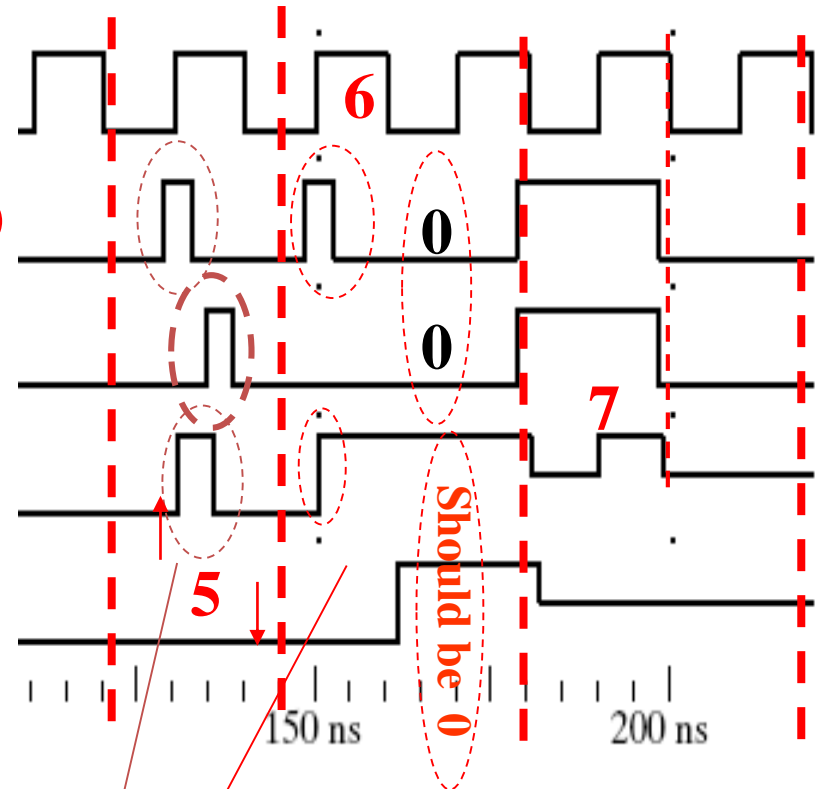- 5. **1s catching**
At the high level:
 First sampled: $RS=10, Y=1$
 Then sampled: $RS=01, Y=0$
 Before falling edge get : $RS=00$
 At falling edge untaken:
 $Y=1$, **Hold Q: $Q=0$**
- 6. **1s catching**
 At rising : $RS=10, Y=1$
 At falling: $RS=00$, Hold $Y=1$




In the pulse arrives before $Q = 0$, at the end of the pulse $RS = 00$, Q should be kept at "0"

- 7. $RS=11$, Uncertain **1s catching**



S-R Master-Slave timing: Integrated


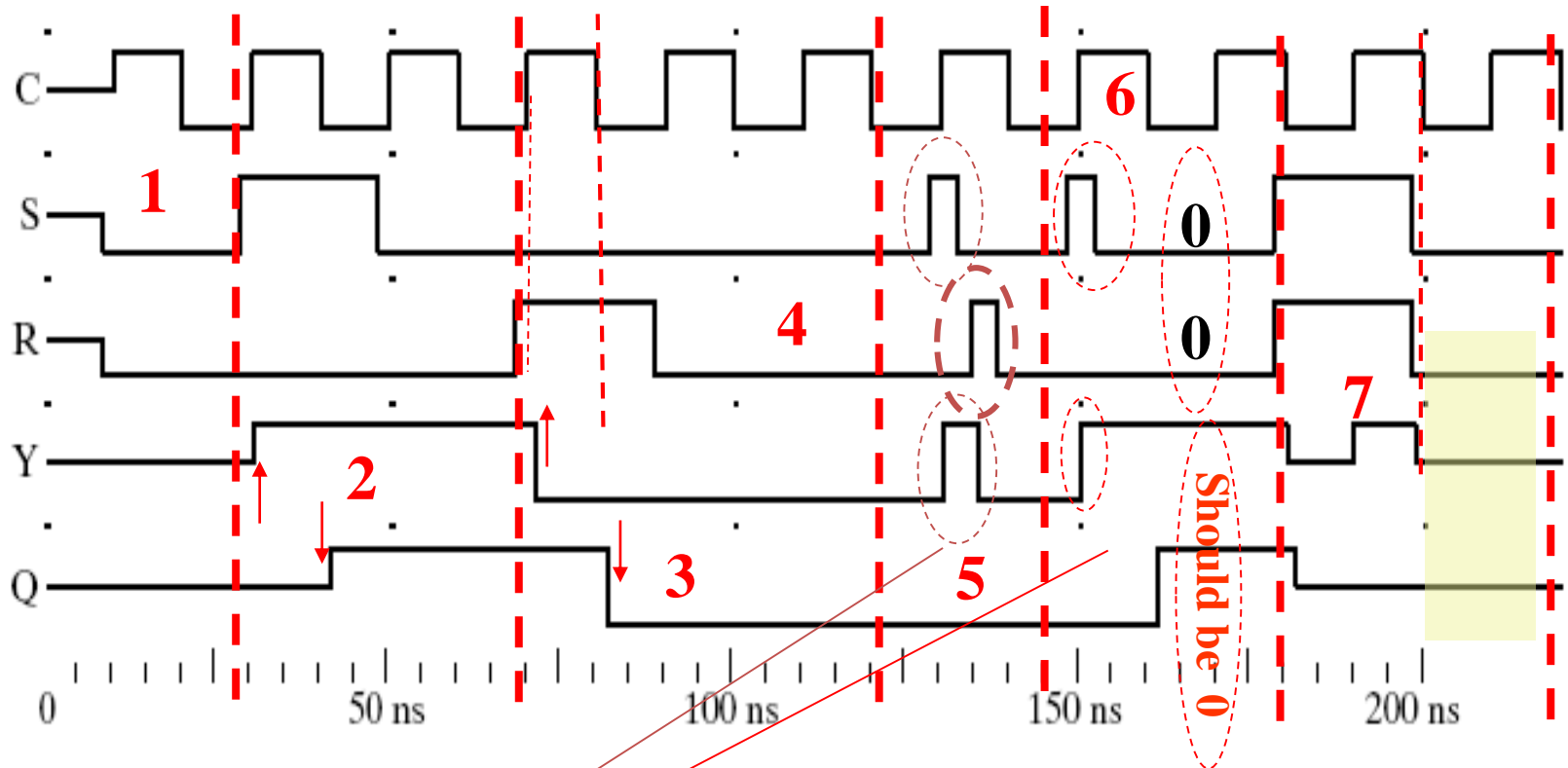


1s catching

In the pulse arrives before $Q = 0$, at the end of the pulse $RS = 00$, Q should be kept at "0"

Flip-Flop Problem

- ❑ The change in the flip-flop output is delayed by the pulse width which makes the circuit slower or
- ❑ S and/or R are permitted to change while C = 1
 - Suppose $Q = 0$ and S goes to 1 and then back to 0 with R remaining at 0
 - ❑ The master latch sets to 1
 - ❑ A 1 is transferred to the slave
 - Suppose $Q = 1$ and S goes to 1 and back to 0 and R goes to 1 and back to 0
 - ❑ The master latch sets and then resets
 - ❑ A 0 is transferred to the slave
 - This behavior is called *1s catching*

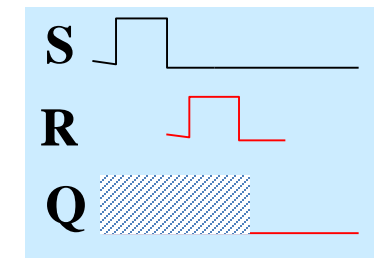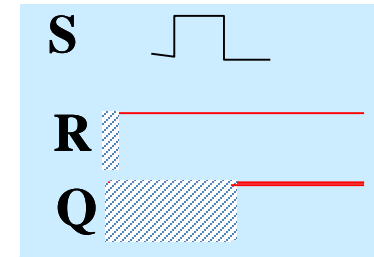



D Triggers




Flip-Flop Solution

- ❑ Use edge-triggering instead of master-slave
- ❑ An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a **transition** of the clock signal
- ❑ Edge-triggered flip-flops can be built directly at the electronic circuit level, or
- ❑ A **master-slave** D flip-flop which also exhibits **edge-triggered behavior** can be used.


Edge-Triggered D Flip-Flop

- ❑ The edge-triggered D flip-flop is the same as the master-slave D flip-flop
- ❑ It can be formed by:
 - Replacing the first clocked S-R latch with a clocked D latch or
 - Adding a D input and inverter to a master-slave S-R flip-flop
- ❑ The delay of the S-R master-slave flip-flop can be **avoided** since the **1s-catching** behavior is not present with D replacing S and R inputs
- ❑ The change of the D flip-flop output is associated with the negative edge at the end of the pulse
- ❑ It is called a **negative-edge triggered** flip-flop

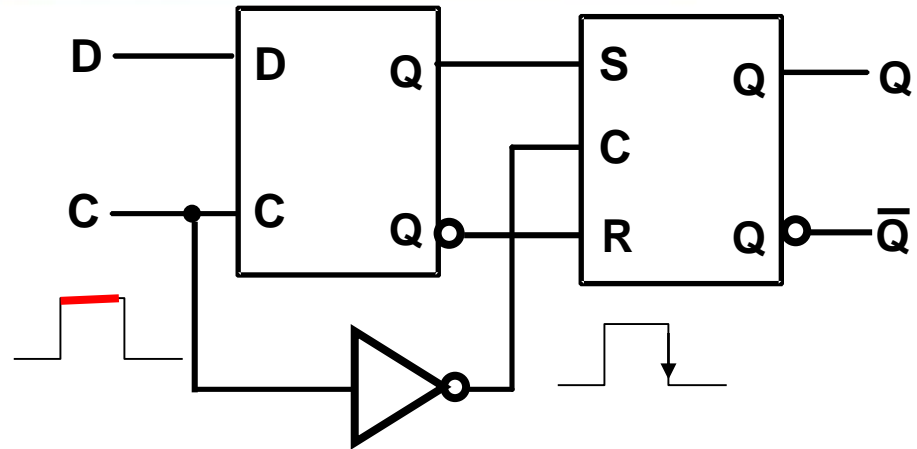

Positive-Edge Triggered D Flip-Flop

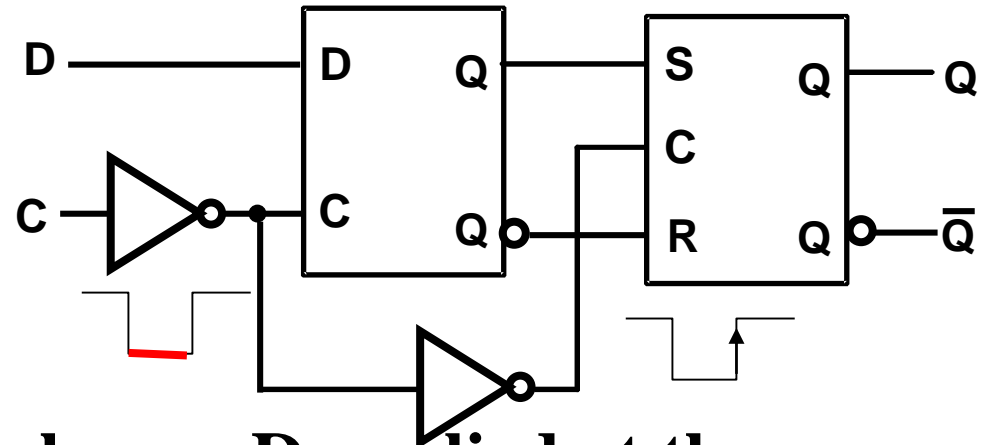- Formed by adding inverter to clock input




- Q changes to the value on D applied at the positive clock edge within timing constraints to be specified
- Our choice as the **standard flip-flop** for most sequential circuits

This is an equivalent edge trigger behavior

Positive edge to maintain the blocking type D flip-flop circuit



• Problem 4-3

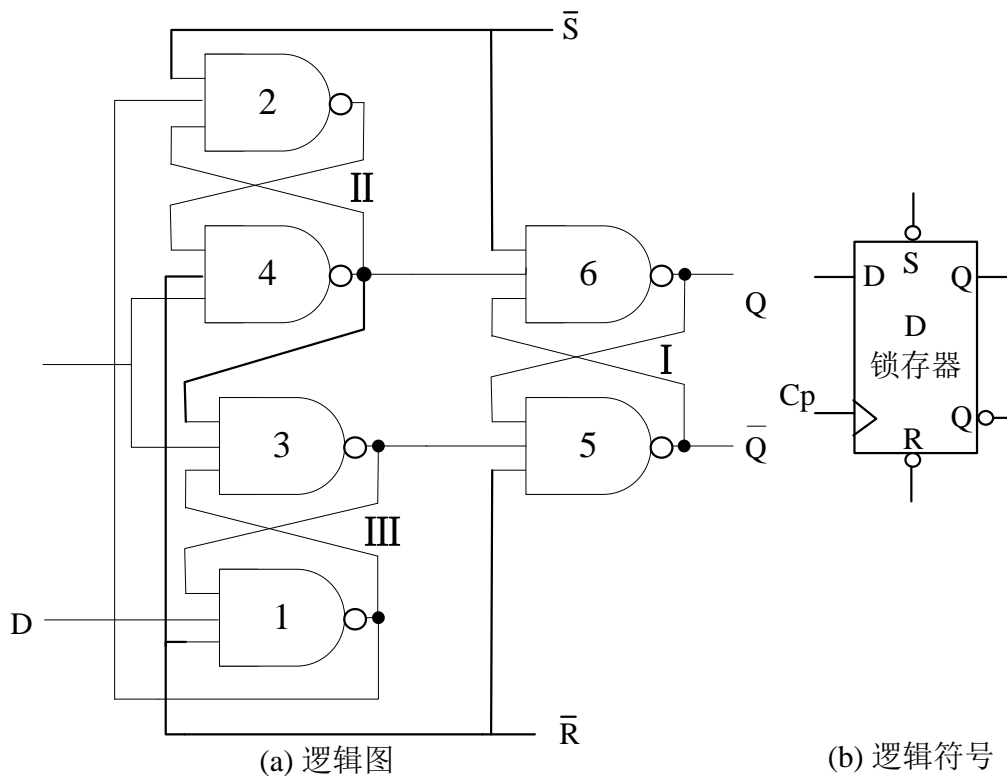


(b) 逻辑符号

异步控制		上升沿触发			
\bar{R}	\bar{S}	Cp	D	Q	\bar{Q}
0	1	X	X	0	1
1	0	X	X	1	0
1	1	↑	0	0	1
1	1	↑	1	1	0


(c) 功能表

Standard Symbols for Storage Elements

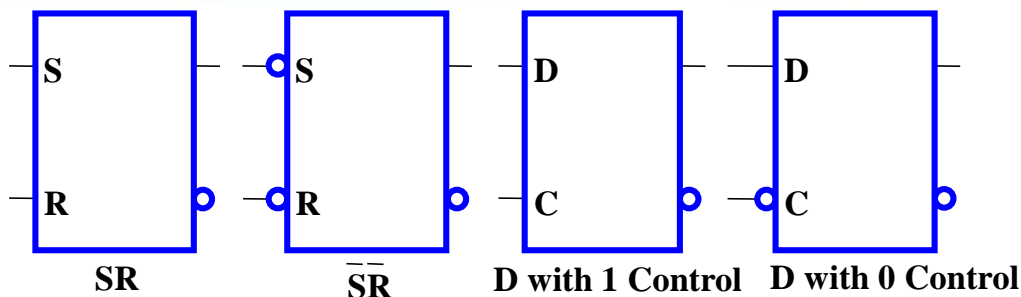

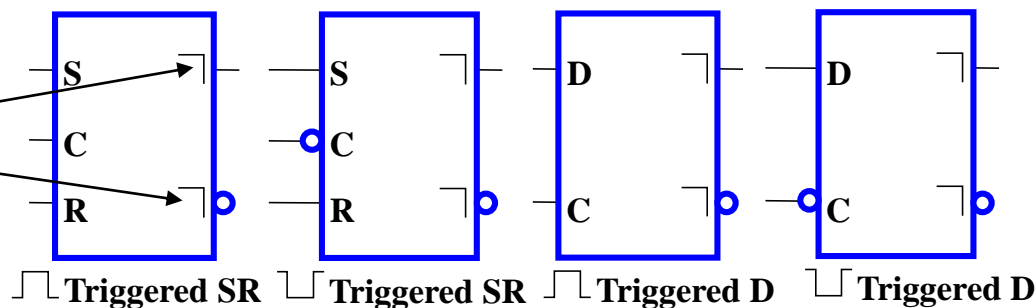
(a) Latches

- **Master-Slave:**
Postponed output indicators



(b) Master-Slave Flip-Flops


- **Edge-Triggered:**
Dynamic indicator

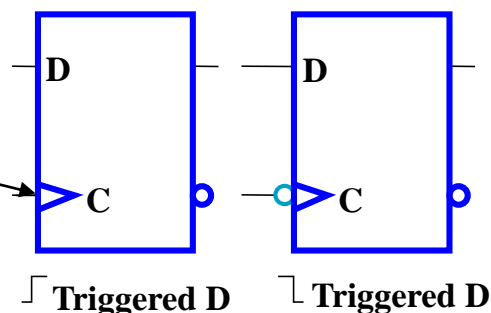

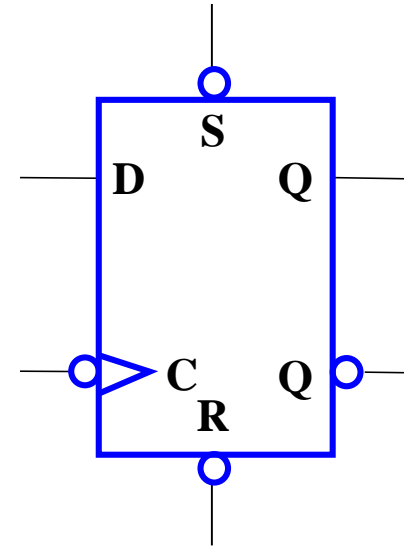(c) Edge-Triggered Flip-Flops

Direct Inputs

- ❑ At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation
- ❑ This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously.
- ❑ Direct R and/or S inputs that control the state of the latches within the flip-flops are used for this initialization.
- ❑ For the example flip-flop shown
 - 0 applied to \overline{R} resets the flip-flop to the 0 state
 - 0 applied to S sets the flip-flop to the 1 state







Flip-Flop Timing Parameters

Flip-Flop Timing Parameters

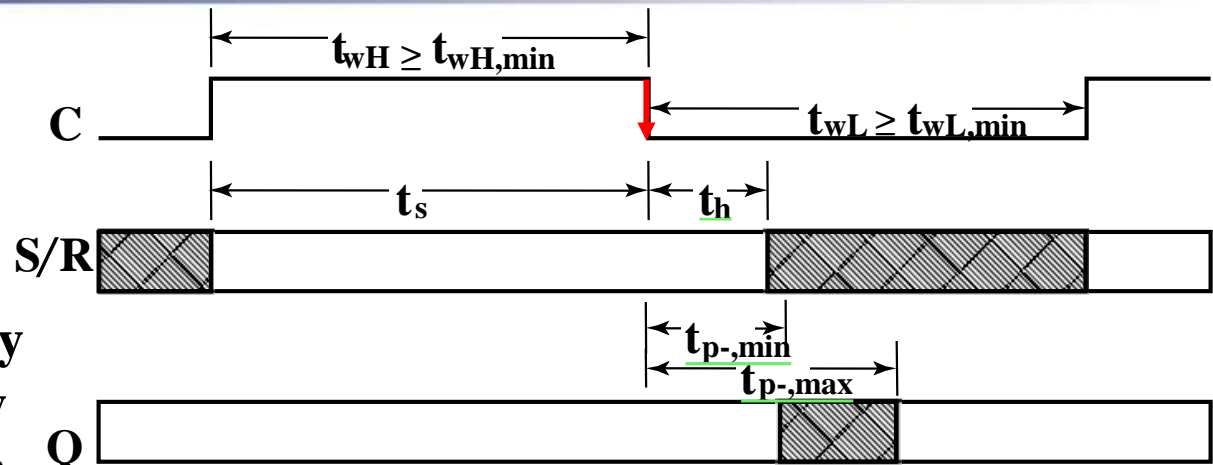- t_s - setup time
- t_h - hold time
- t_w - clock pulse width
- t_{px} - propagation delay
 - t_{PHL} - High-to-Low
 - t_{PLH} - Low-to-High
 - $t_{pd} = \max(t_{PHL}, t_{PLH})$



(a) Pulse-triggered (positive pulse)

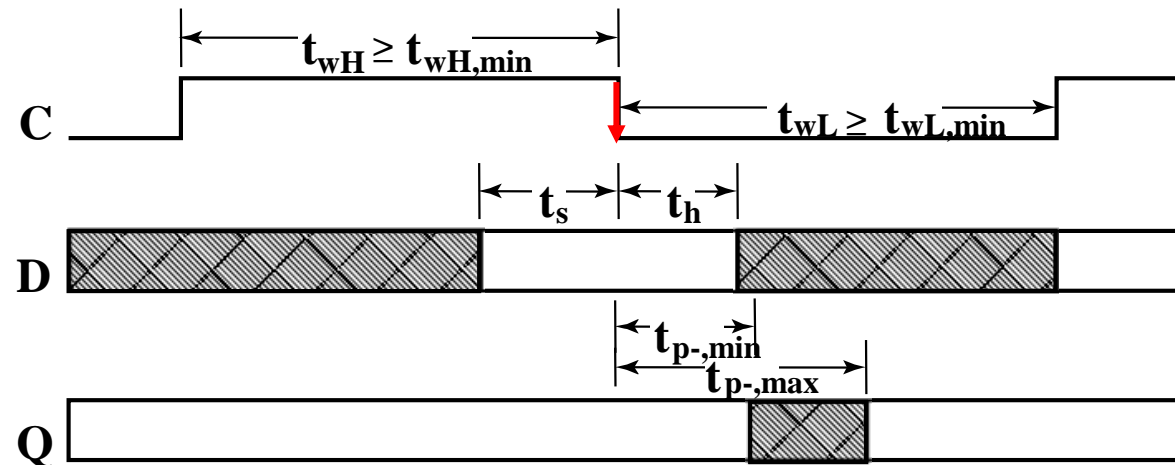


(b) Edge-triggered (negative edge)

Flip-Flop Timing Parameters (continued)





- t_s - setup time
 - Master-slave - Equal to the width of the triggering pulse
 - Edge-triggered - Equal to a time interval that is generally much less than the width of the the triggering pulse
- t_h - hold time - *Often equal to zero*
- t_{px} - propagation delay
 - Same parameters as for gates **except**
 - Measured **from clock edge** that triggers the output change **to** the output change


Summary : R-S Locker

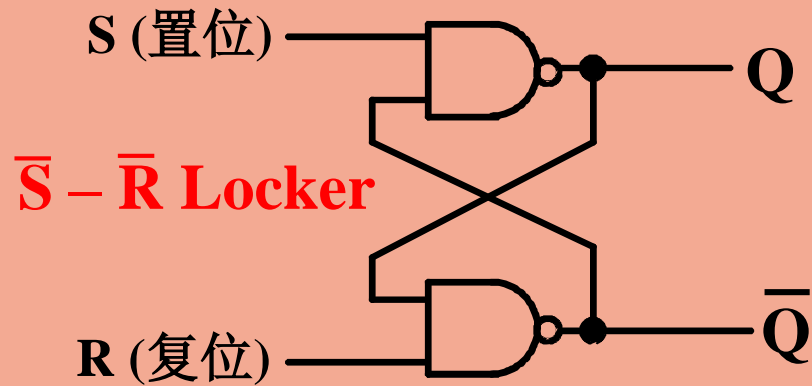


R	S	Q	\bar{Q}	Function
0	0	1	1	00→11 unknown
0	1	0	1	Reset 0
1	0	1	0	set 1
1	1	Q	\bar{Q}	Hold

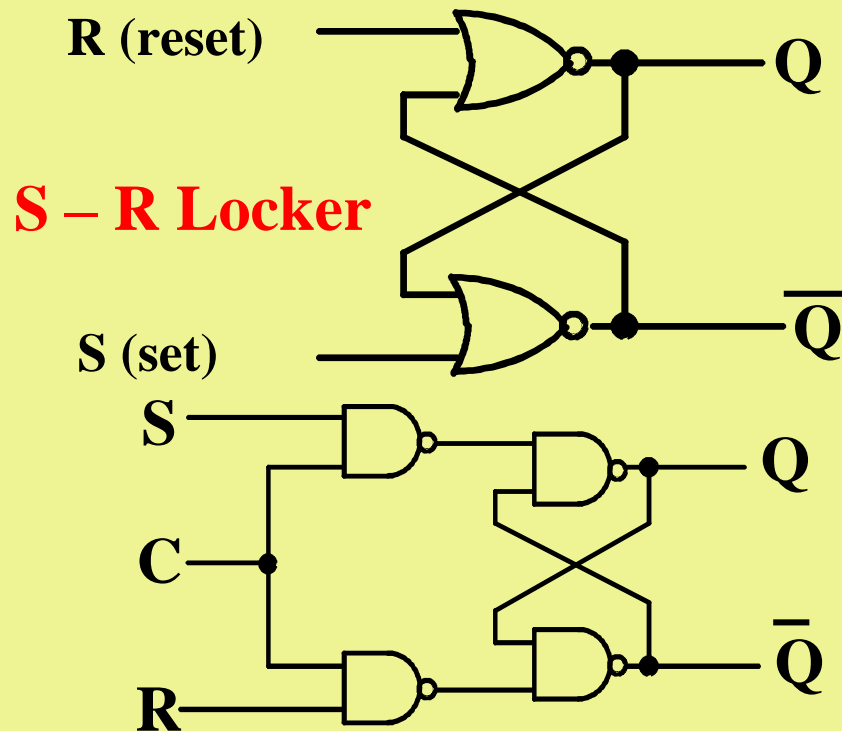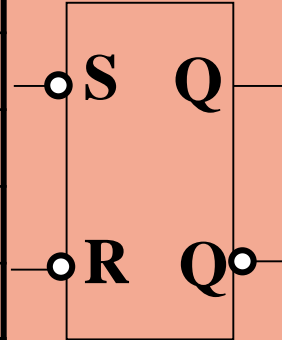


R	S	Q	\bar{Q}	Function
0	0	Q	\bar{Q}	保持
0	1	1	0	Set 1
1	0	0	1	Reset 0
1	1	0	0	11→00 unknown

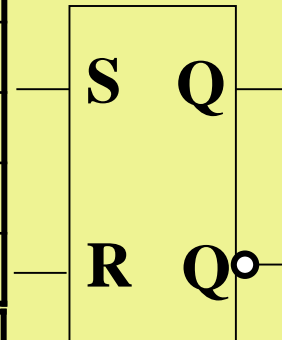



C	R	S	Q	\bar{Q}	Function
0	x	x	Q	\bar{Q}	Hold
1	0	0	Q	Q	Hold
1	0	1	1	0	Set 1
1	1	0	0	1	Reset 0
1	1	1	1	1	11→00 unknown

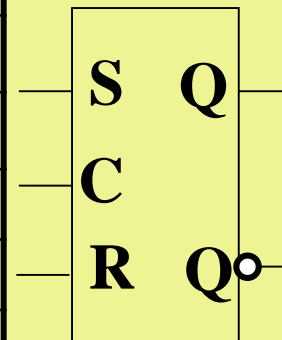



Summary: D-Locker & Flip-Flop

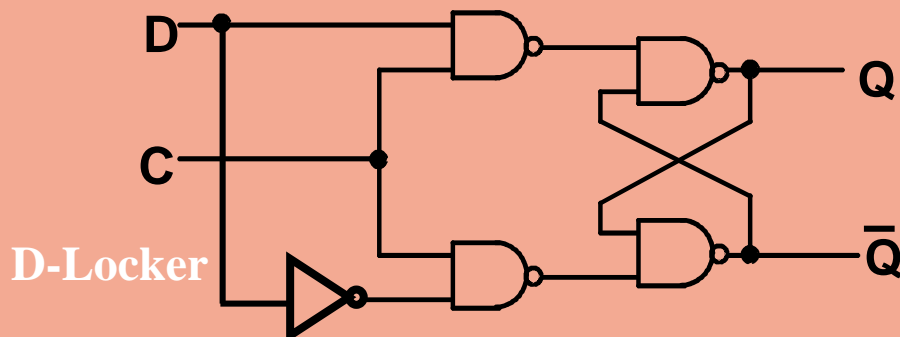


C	D	Q	Q	Fun.
0	x	Q	Q	Hold
1	0	0	1	Set0
1	1	1	0	reset

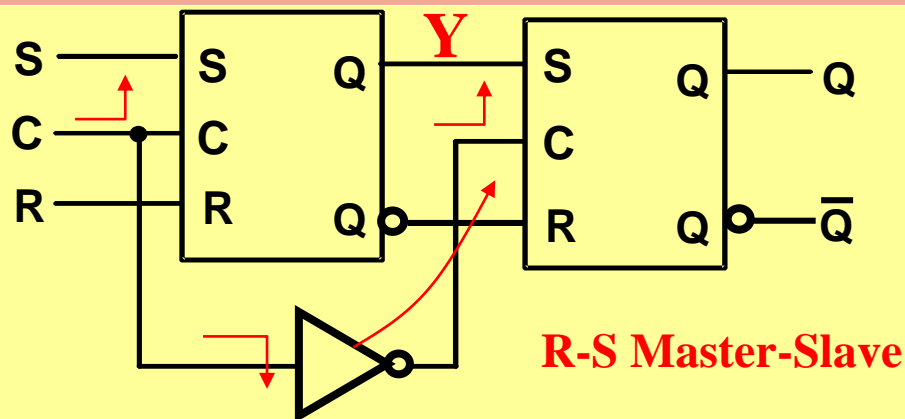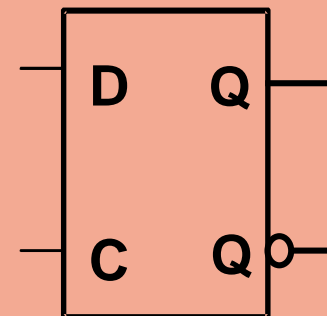


C	D	Q	Q	Hold
0	x	Q	Q	Hold
	0	0	1	Set0
	1	1	0	reset

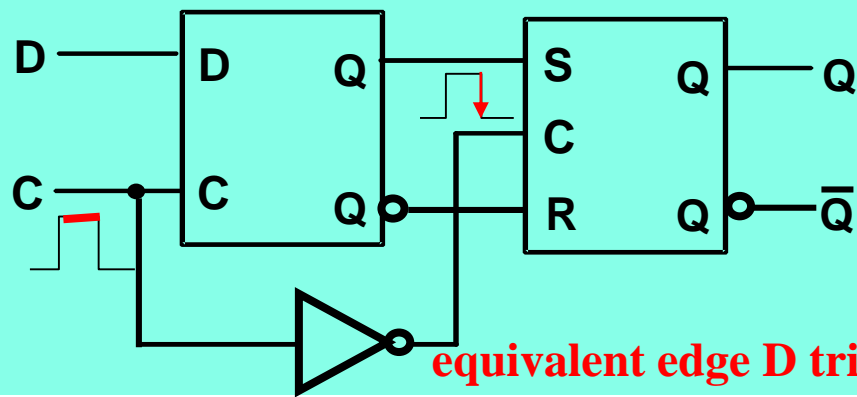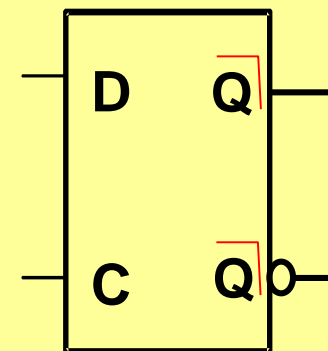

C	D	Q	Q	Fun.
0	x	Q	Q	Hold
↓	0	0	1	Set0
↓	1	1	0	reset

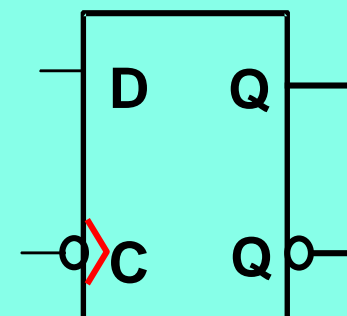


Course Outline

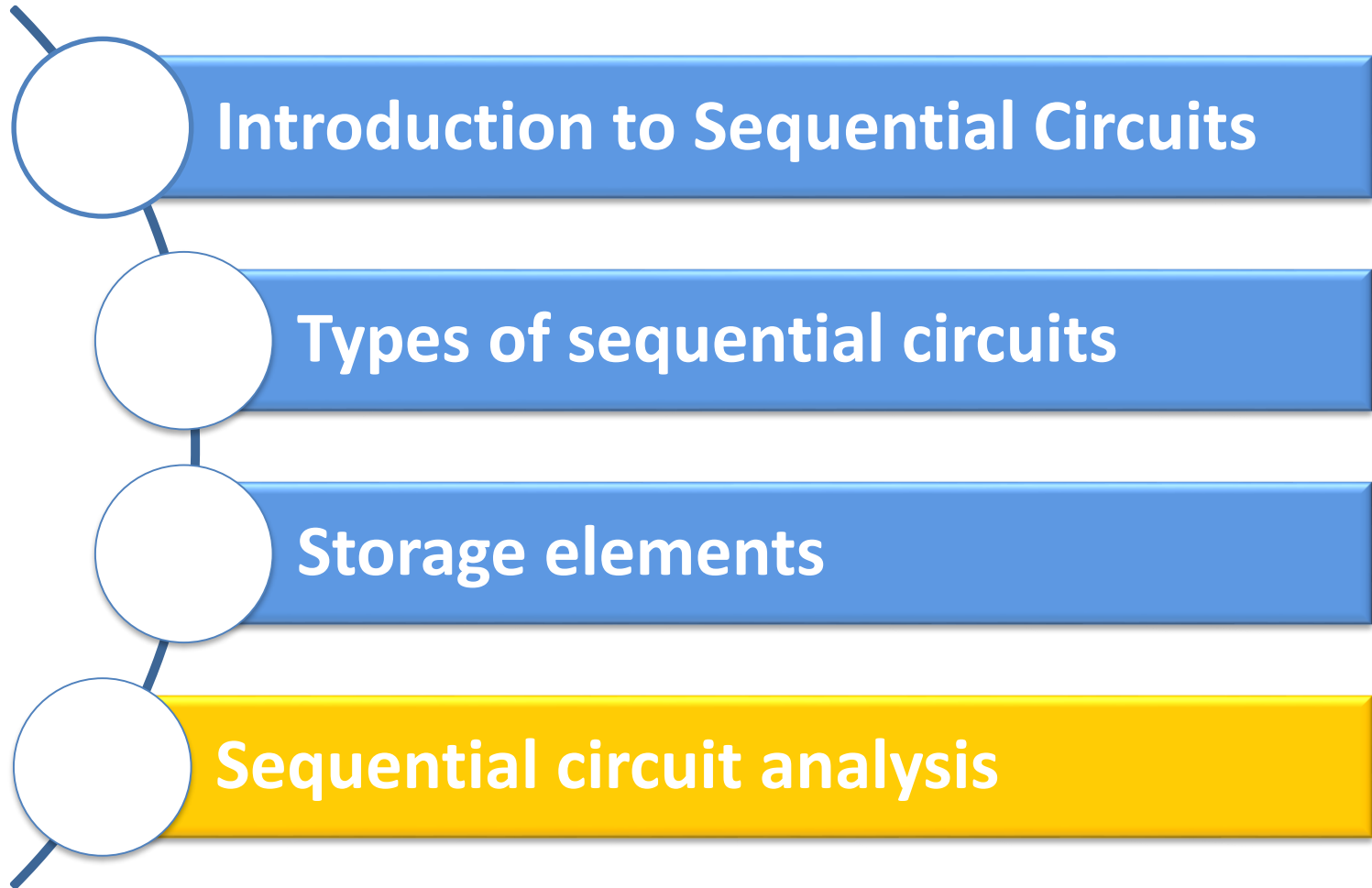

Sequential Circuit Analysis


■ General Model

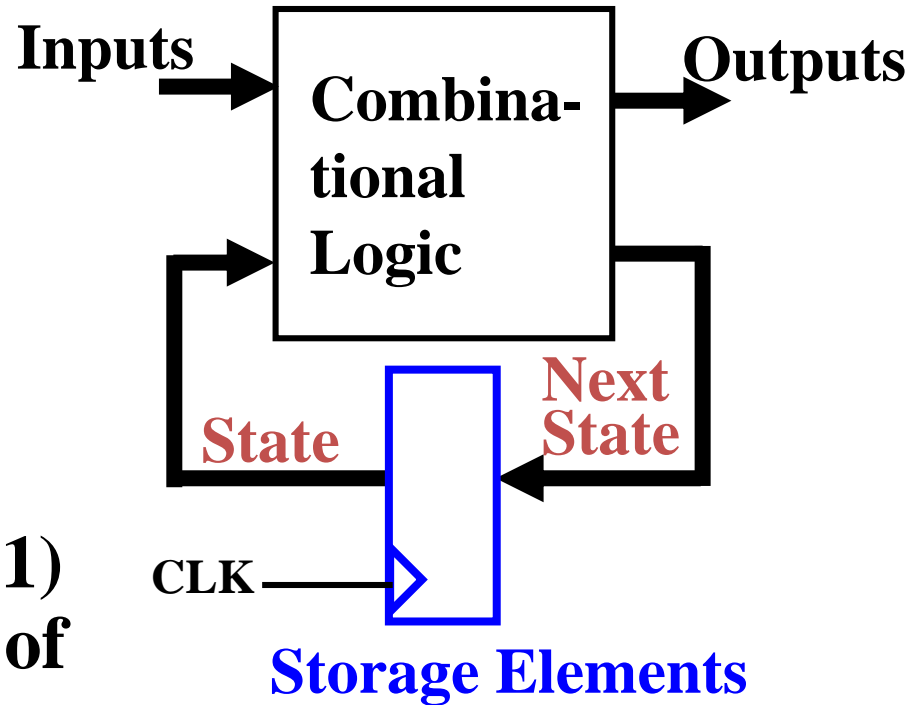- Current State at time (t) is stored in an array of flip-flops.
- Next State at time $(t+1)$ is a Boolean function of State and Inputs.
- Outputs at time (t) are a Boolean function of State (t) and (sometimes) Inputs (t) .



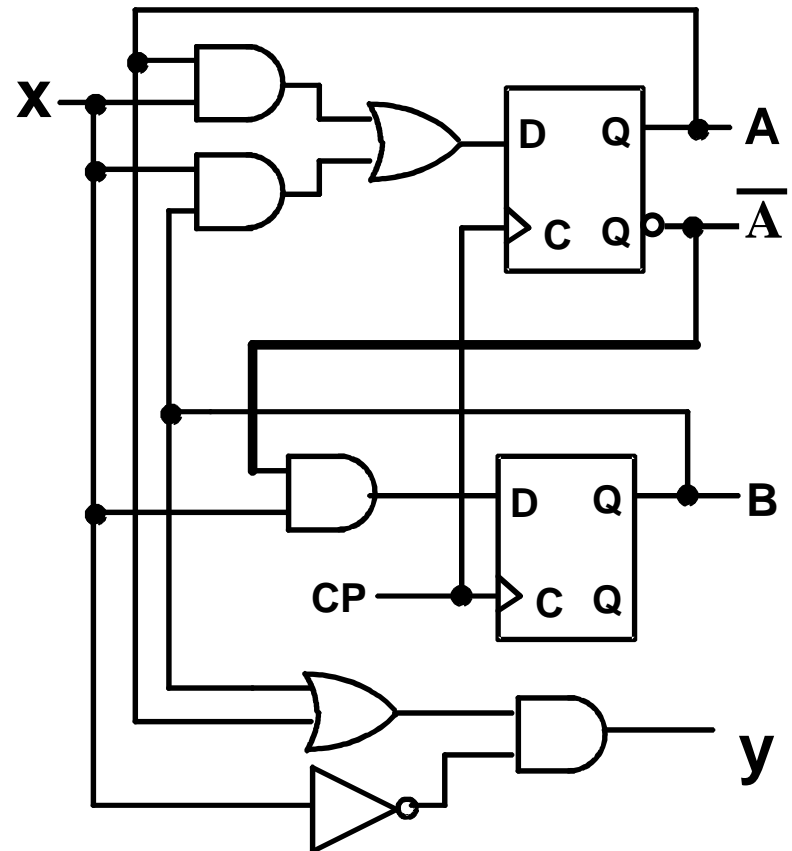Example 1 (from Fig. 5-15)

- **Input:** $x(t)$
- **Output:** $y(t)$
- **State:** $(A(t), B(t))$
- What is the **Output Function**?
 $y =$
- What is the **Trigger input Function**?
 $D_A =$
 $D_B =$
- What is the **Next State Function**?
 $A(t+1) =$
 $B(t+1) =$



Example 1 (from Fig. 5-15) (continued)



■ Triggers the excitation equation:


- $D_A = A(t)x(t) + B(t)x(t)$
- $D_B = \bar{A}(t)x(t)$

■ Next State Function

- $A(t+1) = A(t)x(t) + B(t)x(t)$
- $B(t+1) = \bar{A}(t)x(t)$

■ Output Function:


- $y(t) = \bar{x}(t)(B(t) + A(t))$

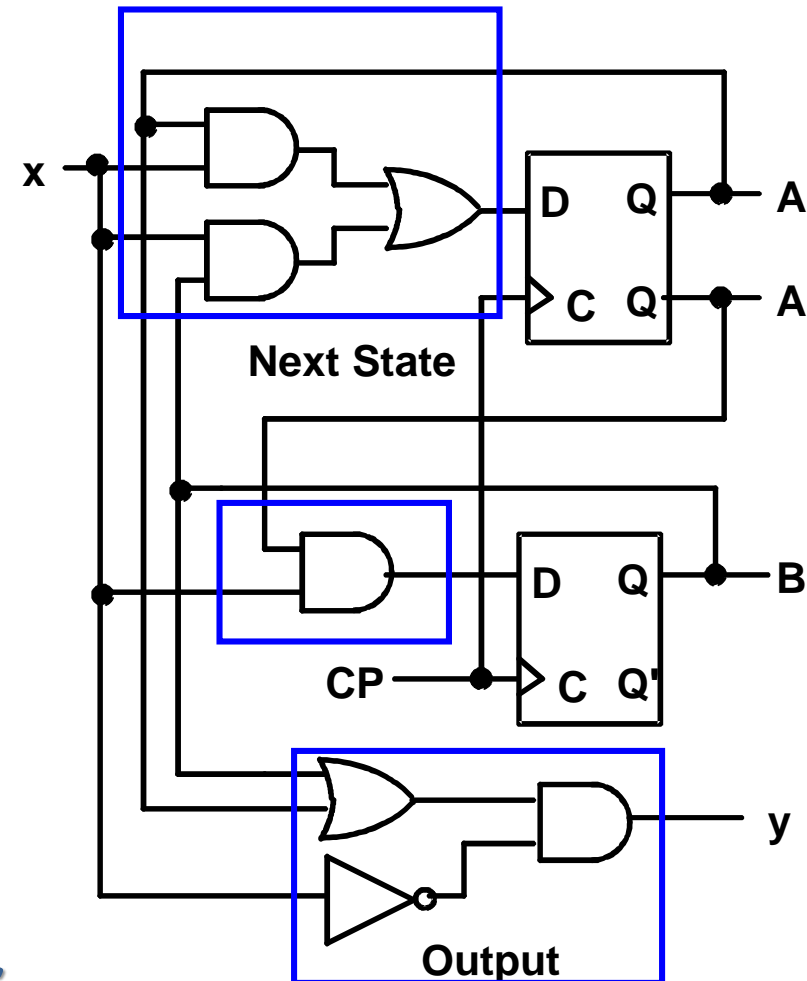

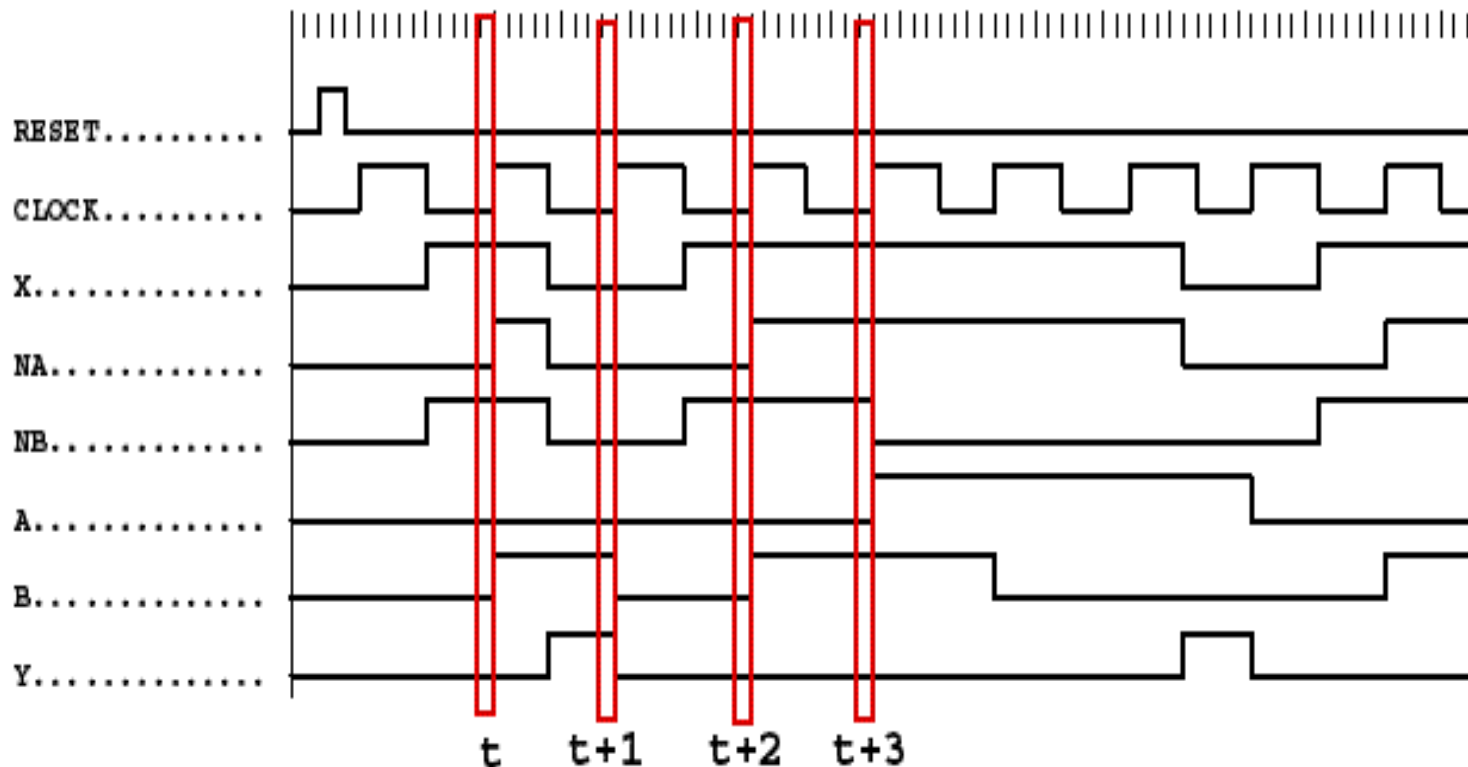Example 1(from Fig. 5-15) (continued)



- Where in time are inputs, outputs and states defined?





State Table Characteristics

- **State table** – a multiple variable table with the following four sections:
 - **Present State** – the values of the state variables for each allowed state.
 - **Input** – the input combinations allowed.
 - **Next-state** – the value of the state at time $(t+1)$ based on the **present state** and the **input**.
 - **Output** – the value of the output as a function of the **present state** and (sometimes) the **input**.
- From the viewpoint of a truth table:
 - the inputs are **Input, Present State**
 - and the outputs are **Output, Next State**



Example 1: State Table (from Fig. 5-15)

- The state table can be filled in using the next state and output equations:

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = \bar{A}(t)x(t)$$

$$y(t) = \bar{x}(t)(B(t) + A(t))$$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0



Example 1: Alternate State Table

- **2-dimensional** table that matches well to a K-map. Present state rows and input columns in Gray code order.
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \bar{A}(t)x(t)$
 - $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State A(t) B(t)	Next State		Output	
	$x(t)=0$ A(t+1)B(t+1)	$x(t)=1$ A(t+1)B(t+1)	$x(t)=0$ y(t)	$x(t)=1$ y(t)
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0



State Diagrams

- The sequential circuit function can be represented in graphical form as a **state diagram** with the following components:
 - A **circle** with the state name in it for each state
 - A **directed arc** from the **Present State** to the **Next State** for each **state transition**
 - A label on each **directed arc** with the **Input** values which causes the **state transition**, and
 - A label:
 - On each **circle** with the **output** value produced, or
 - On each **directed arc** with the **output** value produced.




State Diagrams

- Label form:
 - On **circle** with output included:
 - state/output
 - Moore type output depends only on state
 - On **directed arc** with the **output** included:
 - input/output
 - Mealy type output depends on state and input

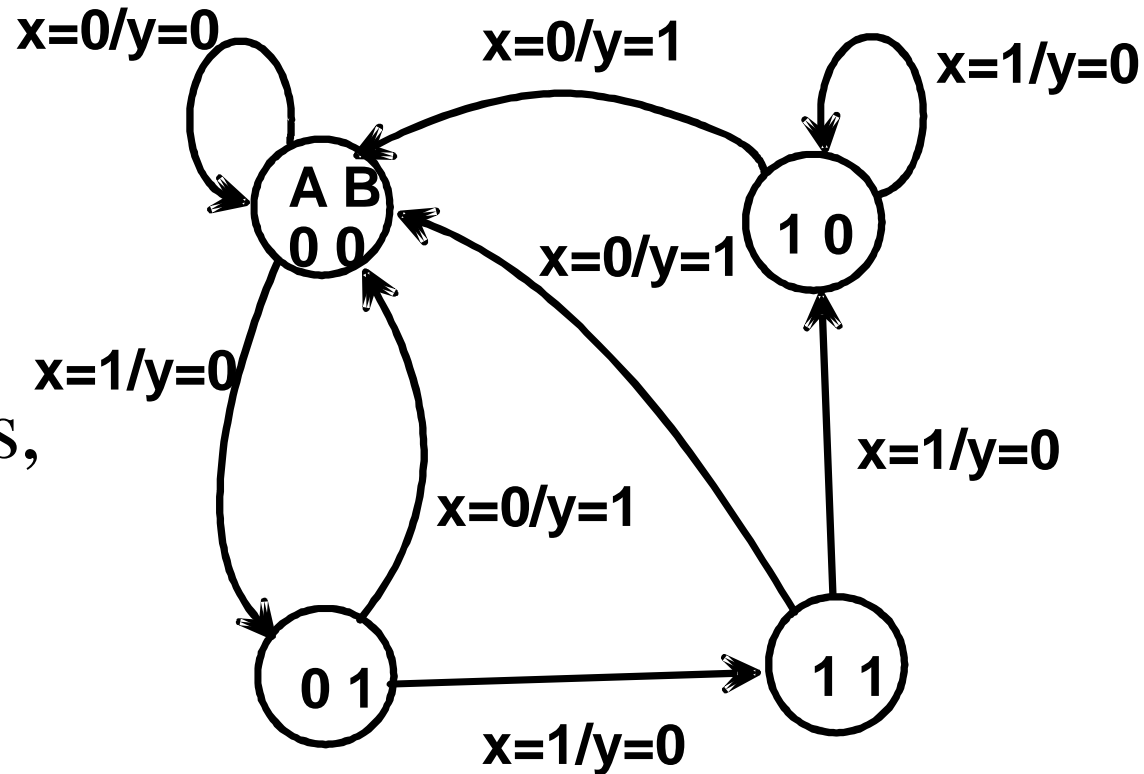Example 1: State Diagram

- Which type?
- Diagram gets confusing for large circuits
- For small circuits, usually easier to understand than the state table






Equivalent State Definitions

- Two states are *equivalent* if their response for **each possible input sequence** is an **identical output sequence**.
- Alternatively, two states are *equivalent* if their outputs produced for each input symbol is identical and their next states for each input symbol are the same or equivalent.



Equivalent State Example

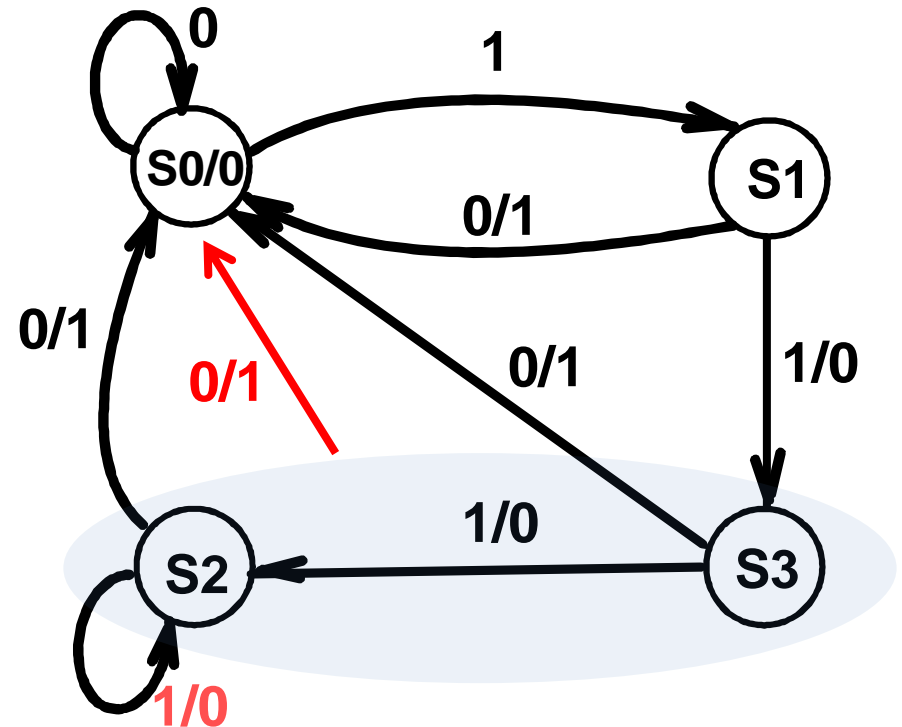- Text Figure 5-17(a):
- For states S3 and S2,
 - the output for input 0 is 1 and input 1 is 0, and
 - the next state for input 0 is S0 and for input 1 is S2.
 - By the alternative definition, states S3 and S2 are equivalent.



Equivalent State Example

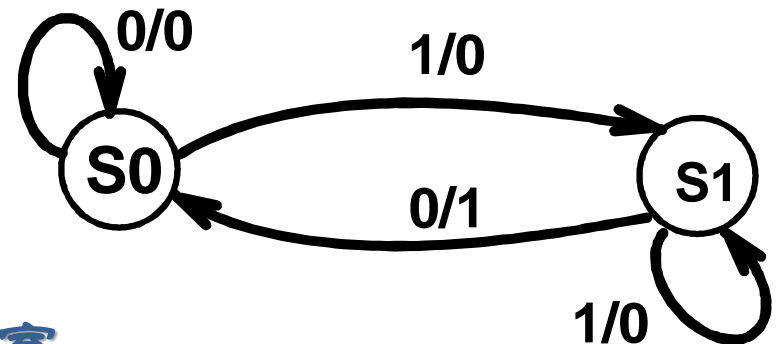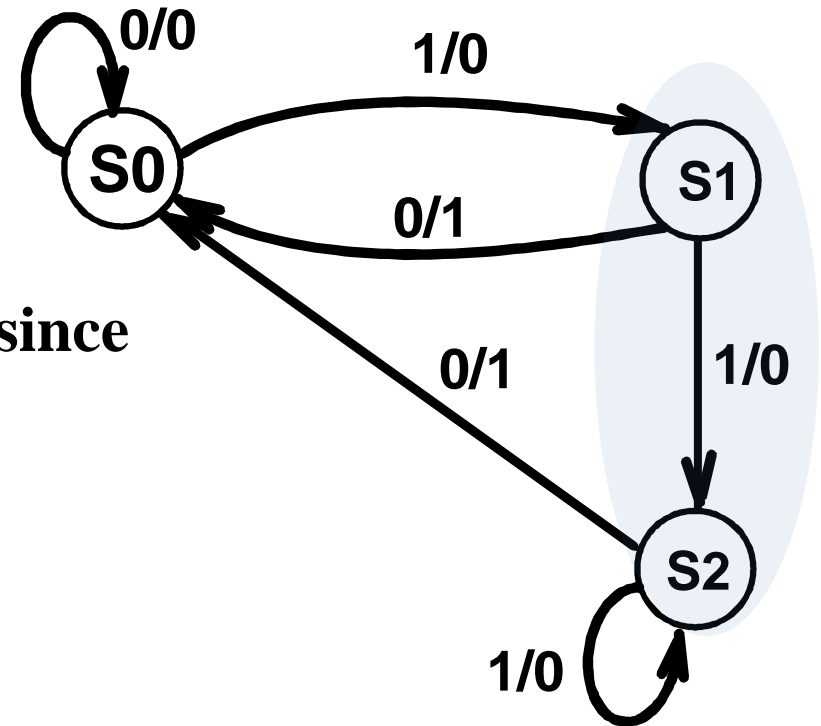- Replacing S3 and S2 by a single state gives state diagram:
- Examining the new diagram, states S1 and S2 are equivalent since
 - their outputs for input 0 is 1 and input 1 is 0, and
 - their next state for input 0 is S0 and for input 1 is S2,
- Replacing S1 and S2 by a single state gives state diagram:





Moore and Mealy Models

- Sequential Circuits or Sequential Machines are also called *Finite State Machines* (FSMs). Two formal models exist:

- **Moore Model**

- Named after E.F. Moore
- Outputs are a function **ONLY** of **states**
- Usually specified on the **states**.


- **Mealy Model**

- Named after G. Mealy
- Outputs are a function of **inputs** AND **states**
- Usually specified on the state transition **arcs**.


Outputs

Moore and Mealy Example Tables

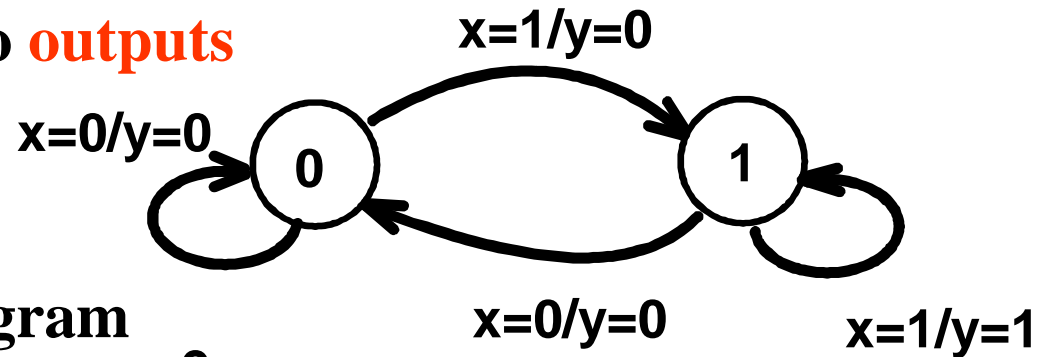- Mealy Model State Diagram maps **inputs and state** to **outputs**



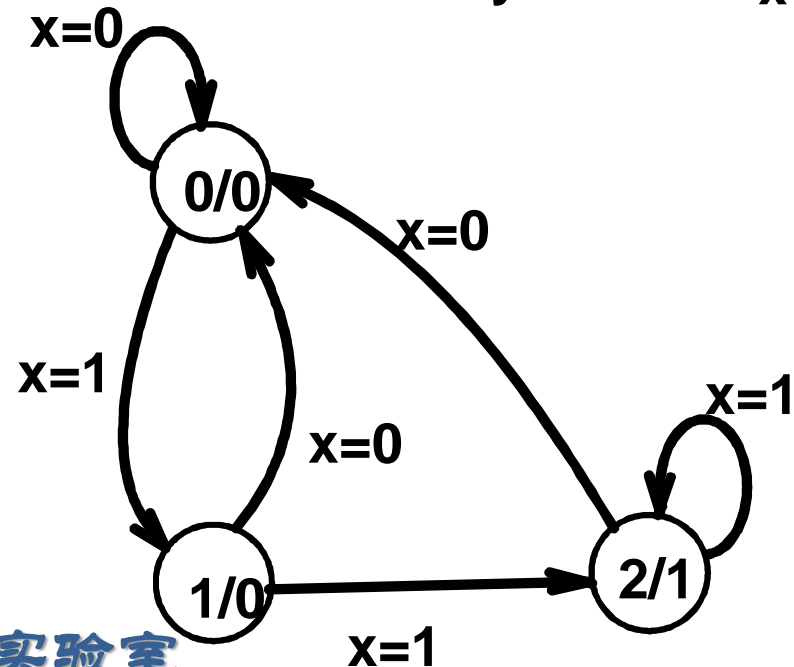- Moore Model State Diagram maps **states** to **outputs**



Moore and Mealy Example Tables

- Moore Model state table maps state to outputs


Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

- Mealy Model state table maps inputs and state to outputs

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

Mixed Moore and Mealy Outputs


- In real designs, some outputs may be Moore type and other outputs may be Mealy type.
- Example: Figure 5-17(a) can be modified to illustrate this
 - State 00: Moore
 - States 01, 10, and 11: Mealy
- Simplifies output specification

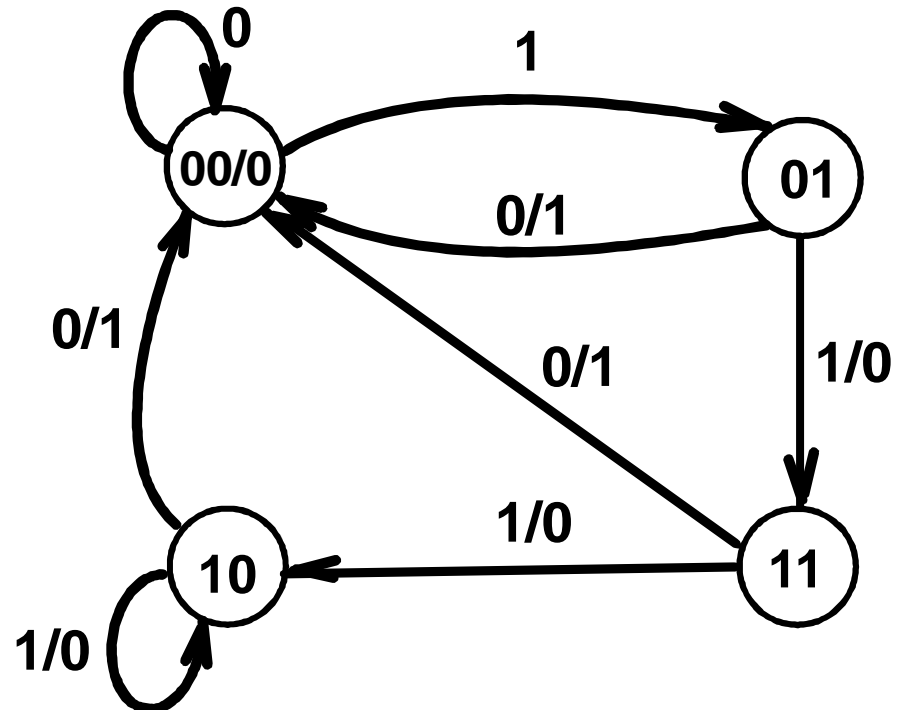

Example 2: Sequential Circuit Analysis



■ Logic Diagram:

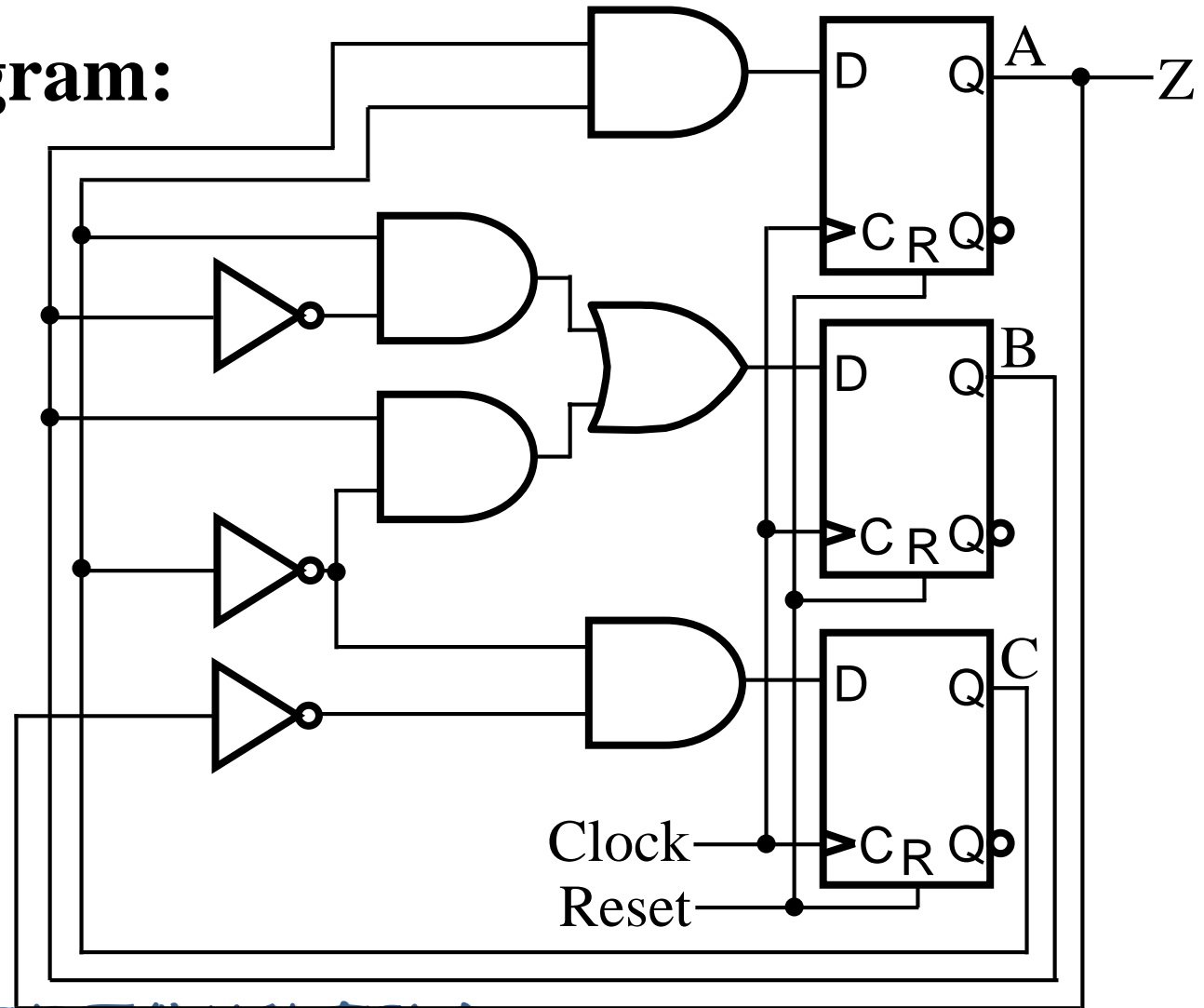



Example 2: Flip-Flop Input Equations

- **Variables**
 - **Inputs: None**
 - **Outputs: Z**
 - **State Variables: A, B, C**
- **Initialization: Reset to (0,0,0)**
- **Equations**
 - $A(t+1) =$ $Z =$
 - $B(t+1) =$
 - $C(t+1) =$



Example 2: Flip-Flop Input Equations

■ Variables

- Inputs: None
- Outputs: Z
- State Variables: A, B, C

■ Initialization: Reset to (0,0,0)

■ Equations

- $A(t+1) = B(t)C(t)$ $Z = A(t)$
- $B(t+1) = \overline{B}(t)C(t) + B(t)\overline{C}(t)$
- $C(t+1) = \overline{A}(t)\overline{C}(t)$



Example 2: State Table

$$X' = X(t+1)$$

A B C	A'B'C'	Z
0 0 0		
0 0 1		
0 1 0		
0 1 1		
1 0 0		
1 0 1		
1 1 0		
1 1 1		




Example 2: State Table

$$X' = X(t+1)$$

A B C	A'B'C'	Z
0 0 0	0 0 1	0
0 0 1	0 1 0	0
0 1 0	0 1 1	0
0 1 1	1 0 0	0
1 0 0	0 0 0	1
1 0 1	0 1 0	1
1 1 0	0 1 0	1
1 1 1	1 0 0	1


Example 2: State Diagram

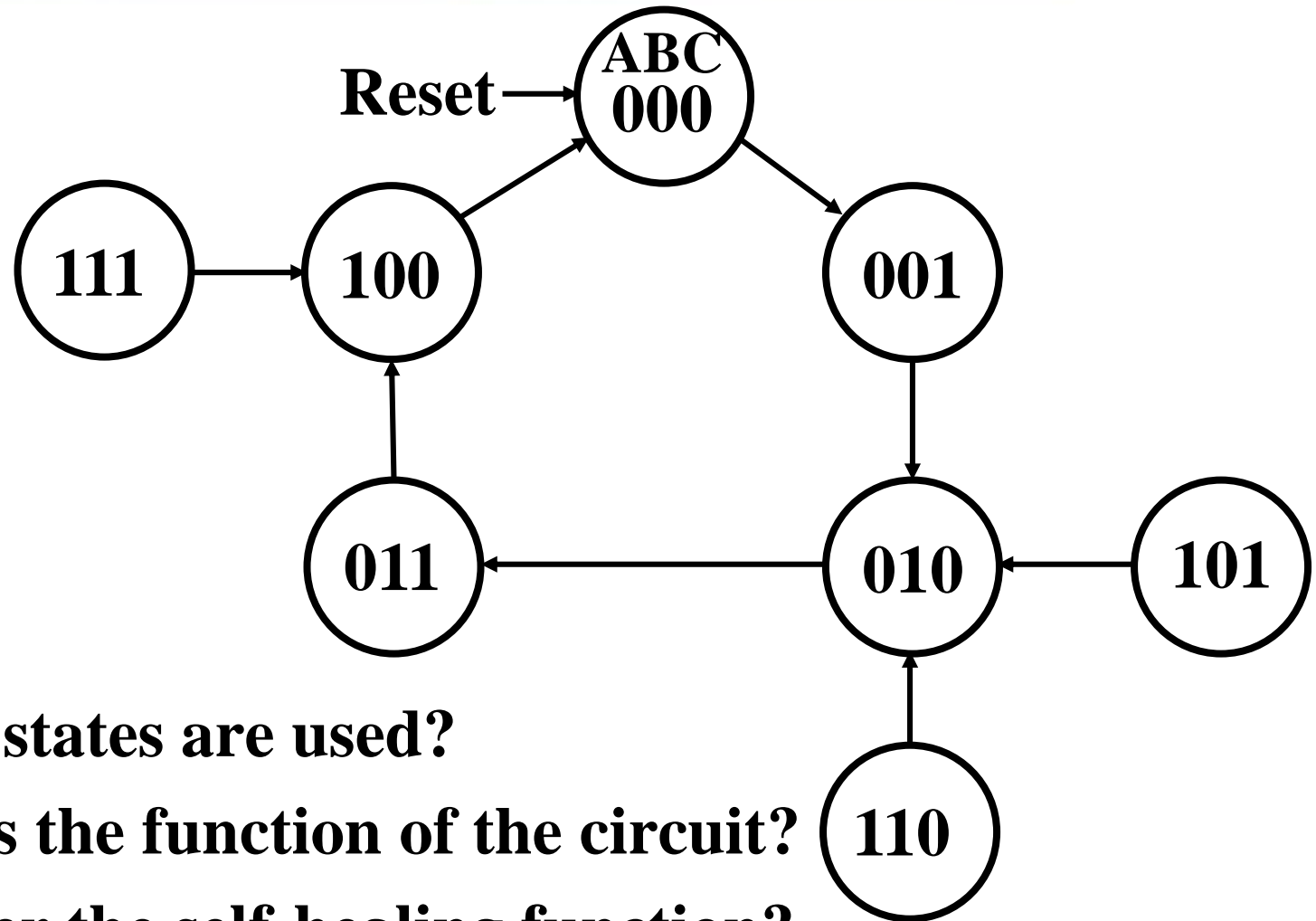

- Which states are used?
- What is the function of the circuit?
- Whether the self-healing function?


Circuit and System Level Timing

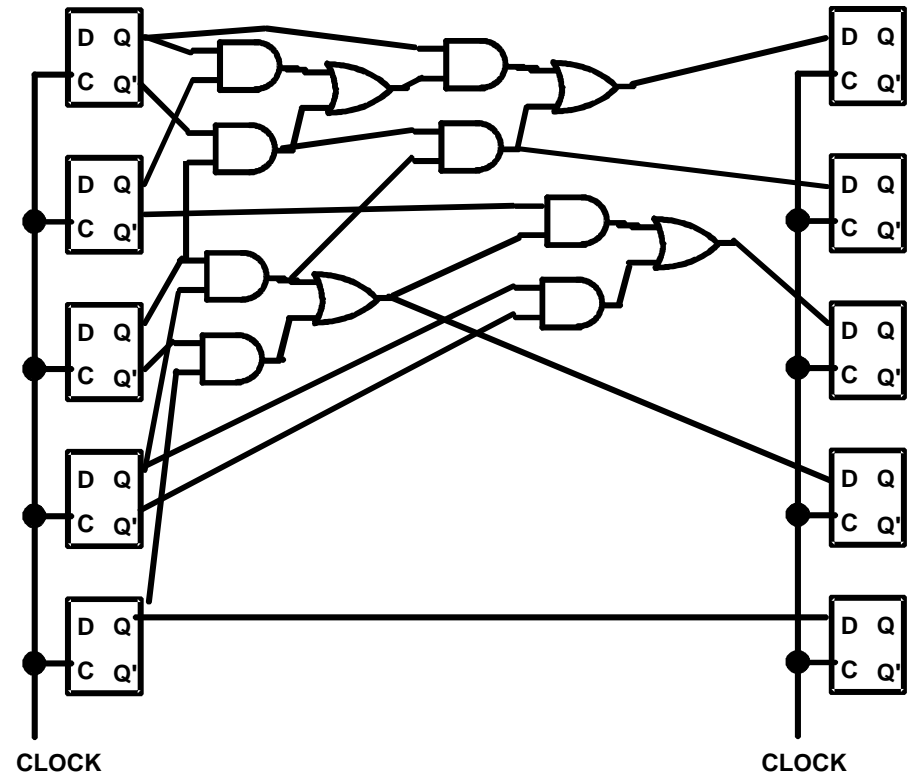- Consider a system comprised of ranks of flip-flops connected by logic:
- If the **clock period** is **too short**, some data changes will not propagate through the circuit to flip-flop inputs before the setup time interval begins




Circuit and System Level Timing (continued)

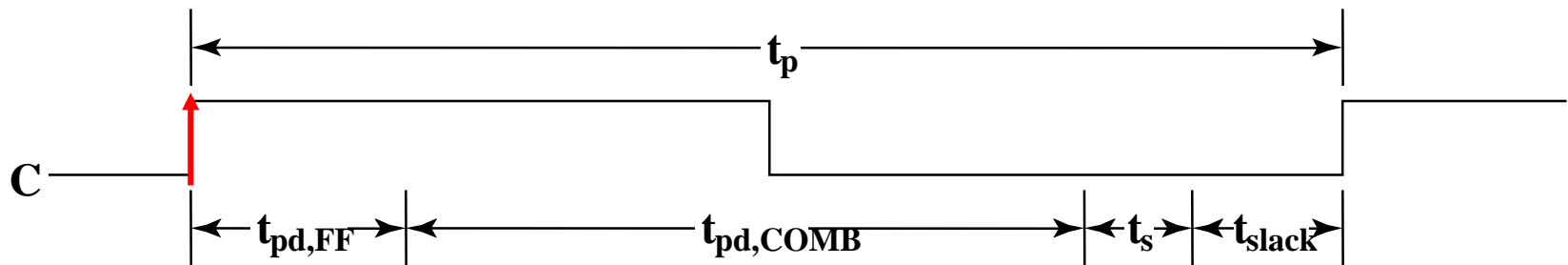- Timing components along a path from flip-flop to flip-flop



(a) Edge-triggered (positive edge)

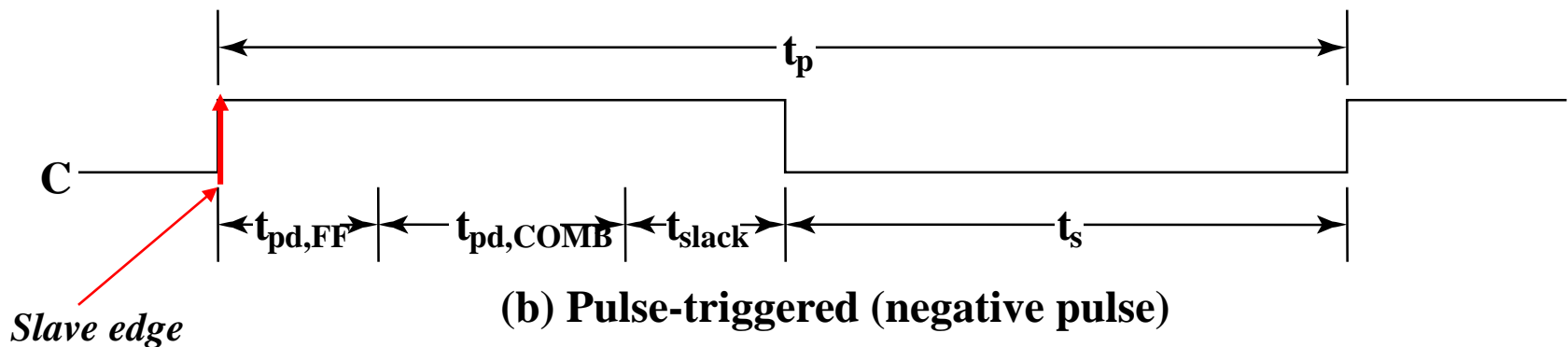

(b) Pulse-triggered (negative pulse)

Circuit and System Level Timing (continued)



■ New Timing Components

- t_p - clock period - The interval between occurrences of a specific clock edge in a periodic clock
- $t_{pd,COMB}$ - total delay of combinational logic along the path from flip-flop output to flip-flop input
- t_{slack} - extra time in the clock period in addition to the sum of the delays and setup time on a path
 - Can be either positive or negative
 - Must be greater **than or equal to zero** on all paths for correct operation



Circuit and System Level Timing (continued)

■ Timing Equations

$$t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

- For t_{slack} greater than or equal to zero,

$$t_p \geq \max (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

for all paths from flip-flop output to flip-flop input

- Can be calculated more precisely by using t_{PHL} and t_{PLH} values instead of t_{pd} values, but requires consideration of inversions on paths



Calculation of Allowable $t_{pd,COMB}$

- Compare the allowable combinational delay for a specific circuit:
 - a) Using edge-triggered flip-flops
 - b) Using master-slave flip-flops
- Parameters
 - $t_{pd,FF}(\max) = 1.0 \text{ ns}$
 - $t_s(\max) = 0.3 \text{ ns}$ for edge-triggered flip-flops
 - $t_s = t_{wH} = 1.0 \text{ ns}$ for master-slave flip-flops
 - Clock frequency = 250 MHz

Calculation of Allowable $t_{pd,COMB}$

■ Calculations: $t_p = 1/\text{clock frequency} = 4.0 \text{ ns}$

■ Edge-triggered:


■ $4.0 \geq 1.0 + t_{pd,COMB} + 0.3$

■ $t_{pd,COMB} \leq 2.7 \text{ ns}$


■ Master-slave:

■ $4.0 \geq 1.0 + t_{pd,COMB} + 1.0$

■ $t_{pd,COMB} \leq 2.0 \text{ ns}$

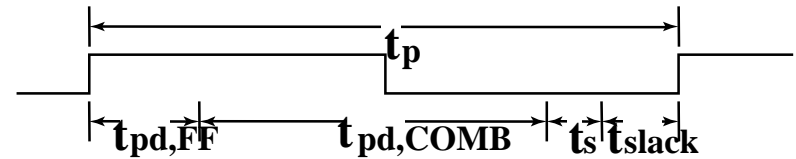

Edge-triggered (positive edge)

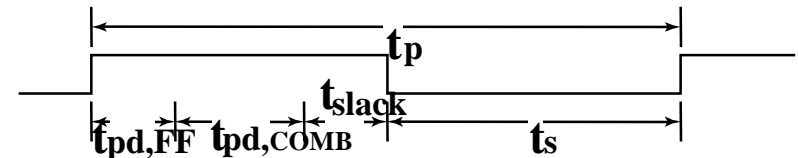

Pulse-triggered (negative pulse)

■ Comparison: Suppose that for a gate, average $t_{pd} = 0.3 \text{ ns}$

■ Edge-triggered: Approximately 9 gates allowed on a path

■ Master-slave: Approximately 6 to 7 gates allowed on a path



第四章作业一

Ch4-1

page280-293: 4-2, 4-7, 4-8, 4-11

Triggers, but it was so!

Thank you!

