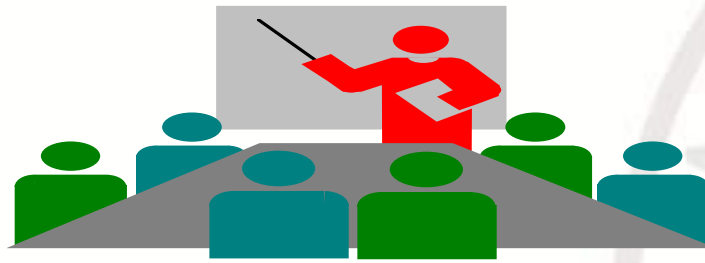




浙江大学
ZHEJIANG UNIVERSITY



数字逻辑设计

LOGIC and Computer Design Fundamentals

CHAPTER 4

Sequential Logic

Sequential Circuit Design (part II)

施青松

Asso. Prof. Shi Qingsong


College of Computer Science and Technology, Zhejiang University

zjsqs@zju.edu.cn

- **Part 1 - Storage Elements and Sequential Circuit Analysis**
- **Part 2- Sequential Circuit Design**
 - Specification
 - Formulation
 - State Assignment
 - Flip-Flop Input and Output Equation Determination
 - Verification
- **Part 3 – State Machine Design**



Course Outline

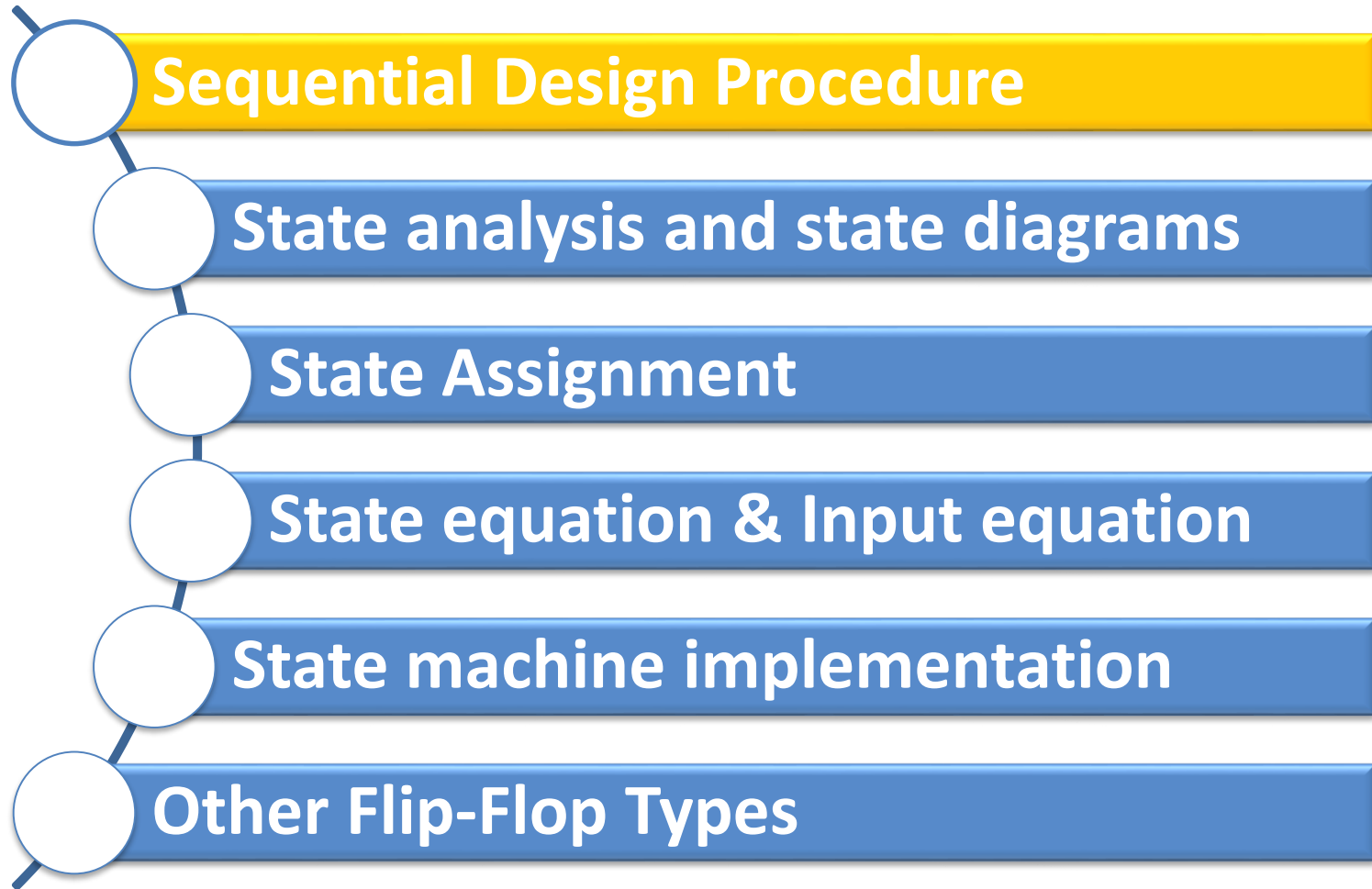



Sequential Circuit Design Procedure

- Event Description** → State diagram
- State table/compressed state
 - state allocation/Assignment
 - state equation
 - Output Equation
 - **choose Flip-Flop**
 - The Excitation/input equation
 - Optimization
 - Logic circuit/module mapping



Procedure

- ❑ **Specification**
- ❑ **Formulation - Obtain a state diagram or state table**
- ❑ **State Assignment - Assign binary codes to the states**
- ❑ **Flip-Flop Input Equation Determination - Select flip-flop types and derive flip-flop equations from next state entries in the table**
- ❑ **Output Equation Determination - Derive output equations from output entries in the table**
- ❑ **Optimization - Optimize the equations**
- ❑ **Technology Mapping - Find circuit from equations and map to flip-flops and gate technology**
- ❑ **Verification - Verify correctness of final design**



Specification

□ Component Forms of Specification

- Written description
- Mathematical description
- Hardware description language*
- Tabular description*
- Equation description*
- Diagram describing operation (not just structure)*

□ Relation to Formulation

- If a specification is rigorous at the binary level (marked with * above), then all or part of formulation may be completed

Formulation: Finding a State Diagram




- A **state** is an abstraction of the history of the past applied inputs to the circuit (including power-up reset or system reset).
 - The interpretation of “past inputs” is tied to the synchronous operation of the circuit. E. g., an input value (other than an asynchronous reset) is measured only during the setup-hold time interval for an edge-triggered flip-flop.
- **Examples:**
 - State A represents the fact that a 1 input has occurred among the past inputs.
 - State B represents the fact that a 0 followed by a 1 have occurred as the most recent past two inputs.



Instance: Finding a State Diagram

- ❑ In specifying a circuit, we use **states** to remember **meaningful properties** of **past input sequences** that are **essential** to **predicting future** output values.
- ❑ A **sequence recognizer** is a sequential circuit that produces a distinct output value whenever a prescribed pattern of input symbols occur in sequence, i.e, **recognizes** an input sequence occurrence.
- ❑ We will develop a procedure **specific to sequence recognizers** to convert a problem statement into a **state diagram**.
- ❑ Next, the **state diagram**, will be converted to a **state table** from which the circuit will be designed.

Course Outline

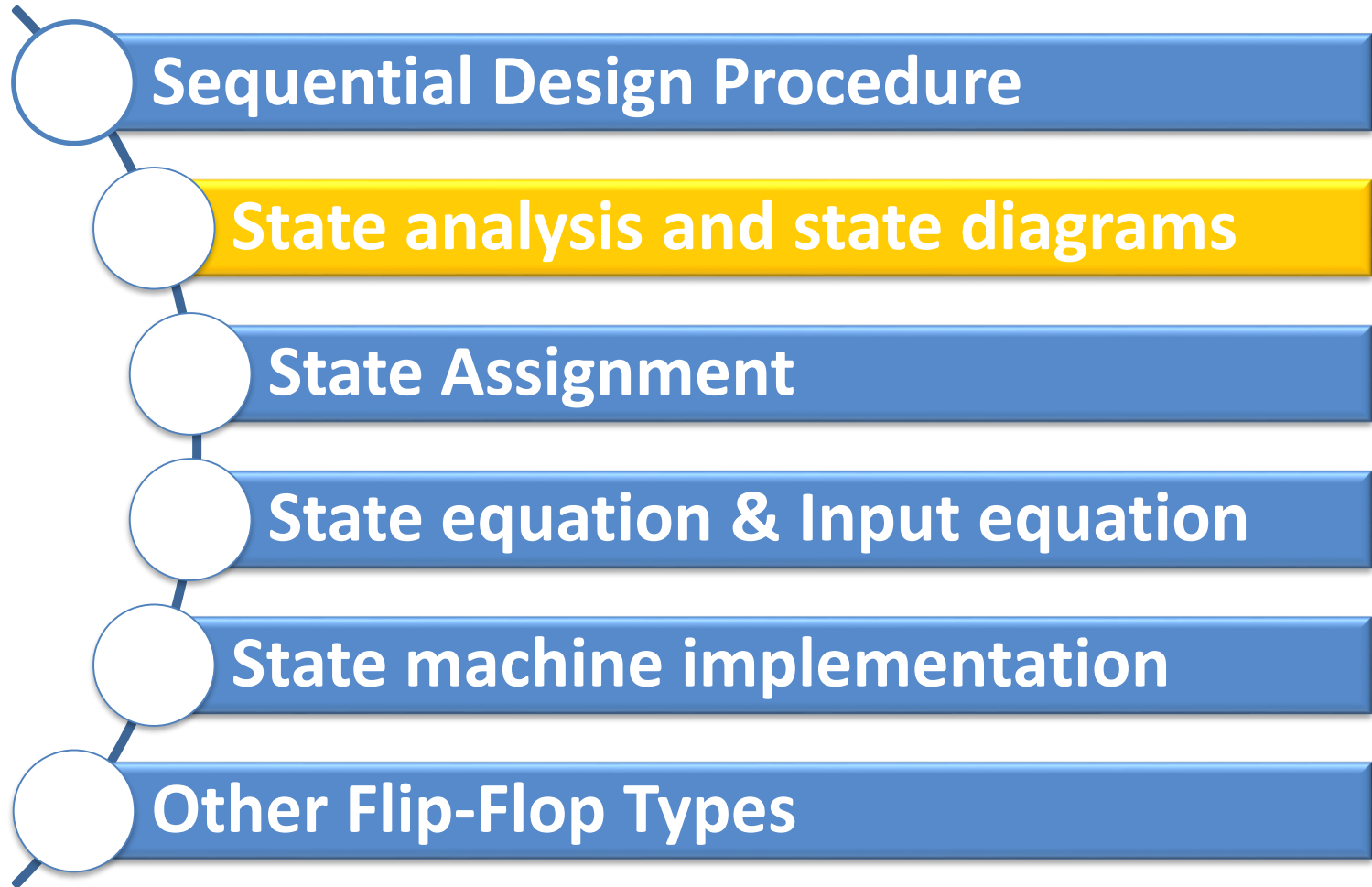



Sequence Recognizer Procedure

□ To develop a sequence recognizer state diagram:

- properly sequence*
- Begin in an initial state in which NONE of the initial portion of the sequence has occurred (typically “reset” state).
 - Add a state that recognizes that the first symbol has occurred.
 - Add states that recognize each successive symbol occurring.
 - The final state represents the input sequence (possibly less the final input value) occurrence.
- non-sequence*
- Add state transition arcs which specify what happens when a symbol *not* in the proper sequence has occurred.
 - Add other arcs on non-sequence inputs which transition to states that represent the input subsequence that has occurred.
- The last step is required because the circuit must recognize the input sequence *regardless of where it occurs within the overall sequence applied since “reset.”*



Sequence Recognizer Example

- Example: Recognize the sequence 1101
 - Note that the sequence 111101 contains 1101 and "11" is a proper sub-sequence of the sequence.
- Thus, the sequential machine must remember that the first two one's have occurred as it receives another symbol.
- Also, the sequence 1101101 contains 1101 as both an initial subsequence and a final subsequence with some overlap, i. e., 1101101 or 1101101.
- And, the 1 in the middle, 1101101, is in both subsequences.
- The sequence 1101 must be recognized each time it occurs in the input sequence.


Example: Recognize 1101

□ Define states for the sequence to be recognized:

- assuming it starts with first symbol,
- continues through each symbol in the sequence to be recognized, and
- uses output 1 to mean the full sequence has occurred,
- with output 0 otherwise.

□ Starting in the initial state (Arbitrarily named "A"):

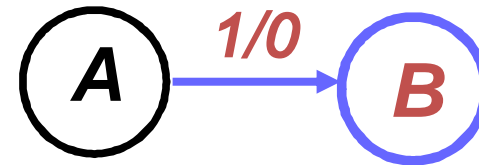- Add a state that recognizes the first "1."



- State "A" is the initial state, and state "B" is the state which represents the fact that the "first" one in the input subsequence has occurred. The output symbol "0" means that the full recognized sequence has not yet occurred.


Example: Recognize 1101:

Properly sequence




□ After one more 1, we have:

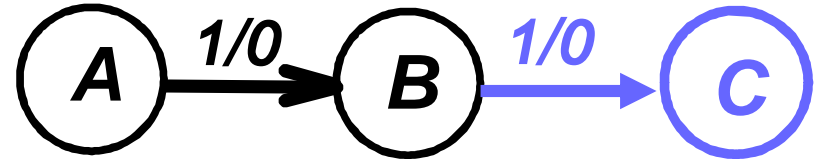- C is the state obtained when the input sequence has two "1"s.




□ Finally, after 110 and a 1, we have:

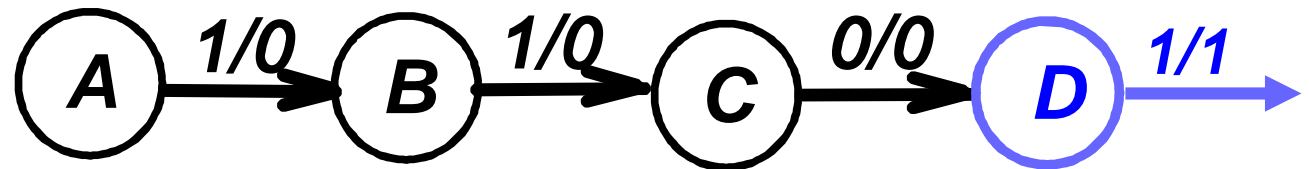


- Transition arcs are used to denote the output function (Mealy Model)
- Output 1 on the arc from D means the sequence has been recognized
- To what state should the arc from state D go? Remember: 1101101?
- Note that D is the last state but the output 1 occurs for the input applied in D. This is the case when a *Mealy model* is assumed.


Example: Recognize 1101 (continued)

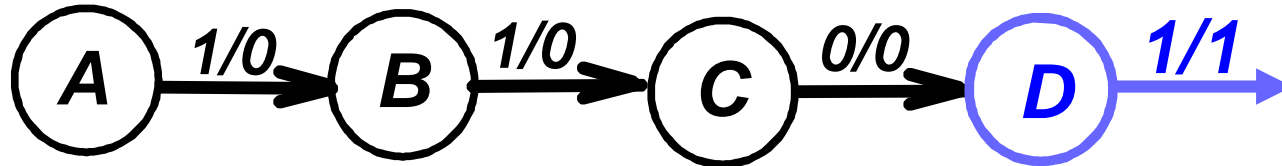

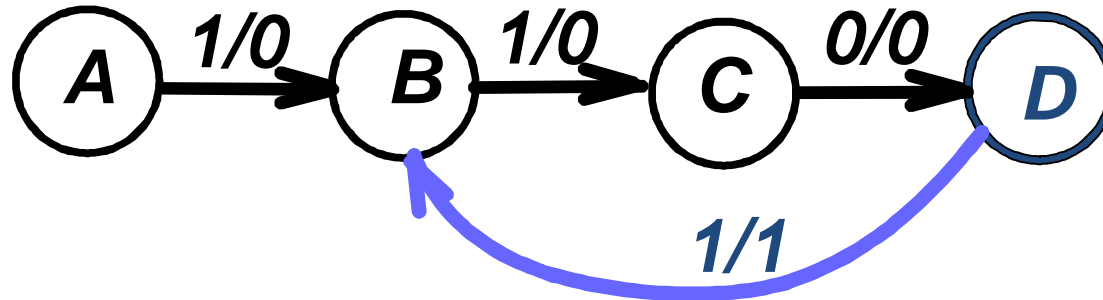- Clearly the final 1 in the recognized sequence 1101 is a sub-sequence of 1101. It follows a 0 which is not a sub-sequence of 1101. Thus it should represent *the same state reached from the initial state after a first 1 is observed*. We obtain:



Example: Recognize 1101 (continued)

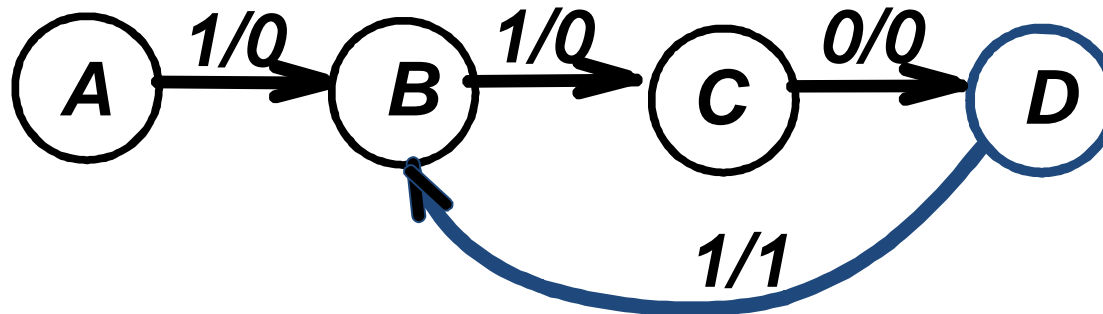


- The state have the following abstract meanings:
 - A: No proper sub-sequence of the sequence has occurred.
 - B: The sub-sequence 1 has occurred.
 - C: The sub-sequence 11 has occurred.
 - D: The sub-sequence 110 has occurred.
 - The 1/1 on the arc from D to B means that the last 1 has occurred and thus, the sequence is recognized.

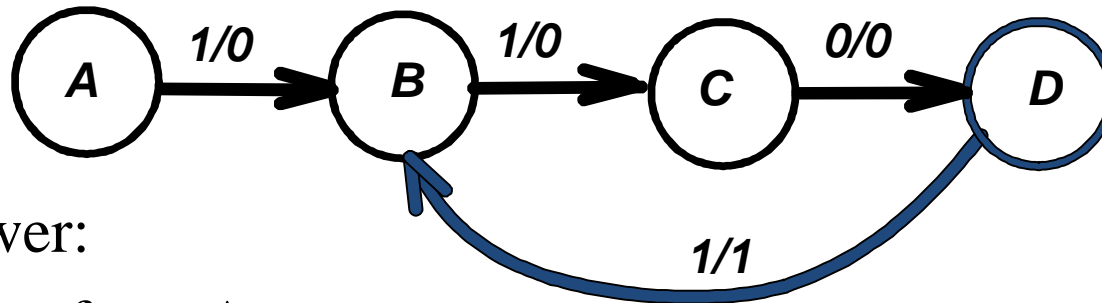Example: Recognize 1101 :

non-sequence



- The other arcs are added to each state for inputs not yet listed. Which arcs are missing?



- Answer:

"0" arc from A

"0" arc from B

"1" arc from C


"0" arc from D.

Recognize 1101 :

Complete state machine



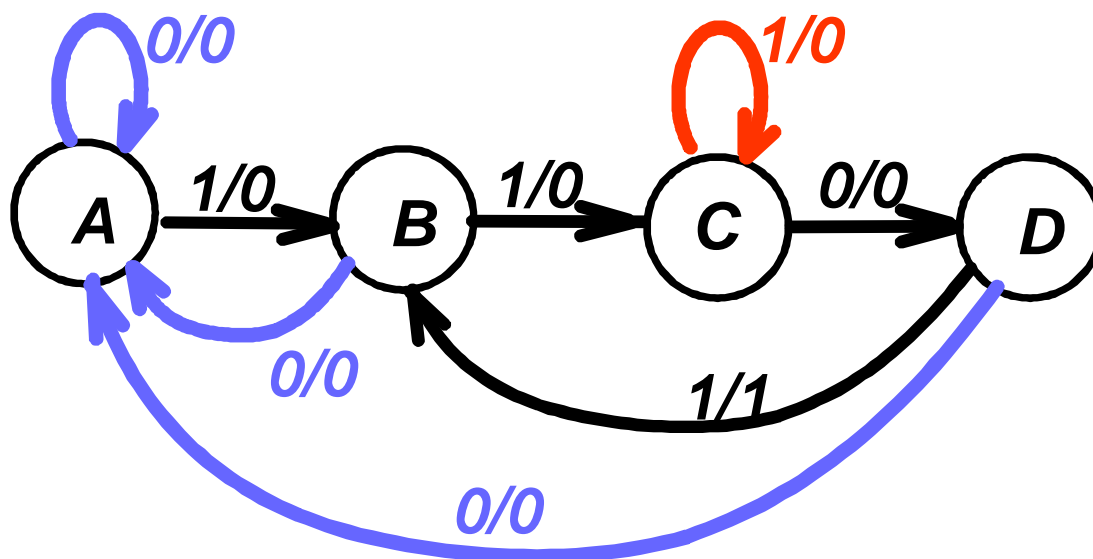
- State transition arcs must represent the fact that an input subsequence has occurred. Thus we get:



- Note that the 1 arc from state C to state C implies that State C means *two or more 1's have occurred*.

Formulation: Find State Table

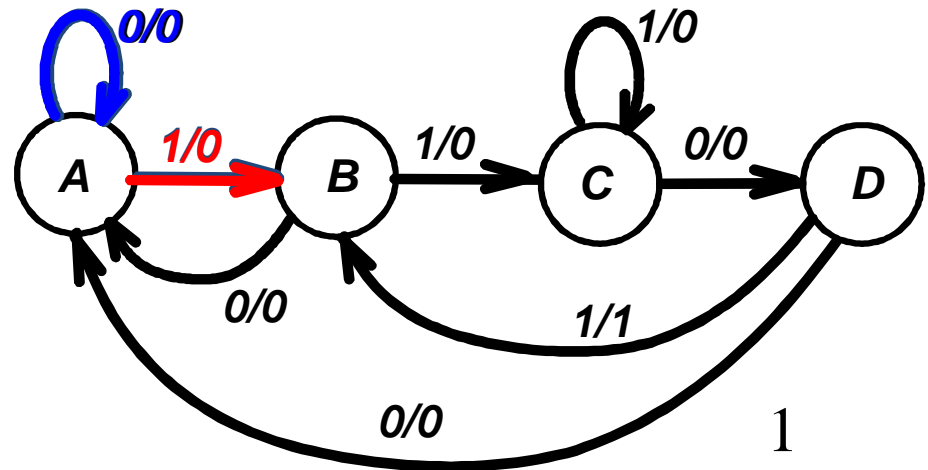
- From the **State Diagram**, we can fill in the **State Table**.
- There are 4 states, one input, and one output. We will choose the form with four rows, one for each current state.
- From State A, the 0 and 1 input transitions have been filled in along with outputs.



Present State	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B				
C				
D				

Formulation: Find State Table

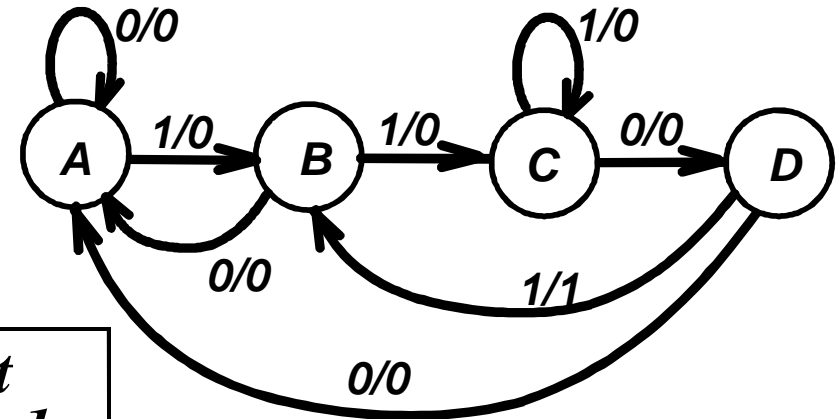□ From the *state diagram*, we complete the *state table*.



<i>Present State</i>	<i>Next State</i>		<i>Output</i>	
	<i>x=0</i>	<i>x=1</i>	<i>x=0</i>	<i>x=1</i>
<i>A</i>	<i>A</i>	<i>B</i>	<i>0</i>	<i>0</i>
<i>B</i>	<i>A</i>	<i>C</i>	<i>0</i>	<i>0</i>
<i>C</i>	<i>D</i>	<i>C</i>	<i>0</i>	<i>0</i>
<i>D</i>	<i>A</i>	<i>B</i>	<i>0</i>	<i>1</i>

□ What would the state diagram and state table look like for the **Moore** model?


Moore Model for Sequence 1101



- For the Moore Model, outputs are associated with states.
- We need to add a state "E" with output value 1 for the final 1 in the recognized input sequence.
 - This new state E, though similar to B, would generate an output of 1 and thus be different from B.
- The **Moore model** for a sequence recognizer usually has *more states* than the Mealy model.

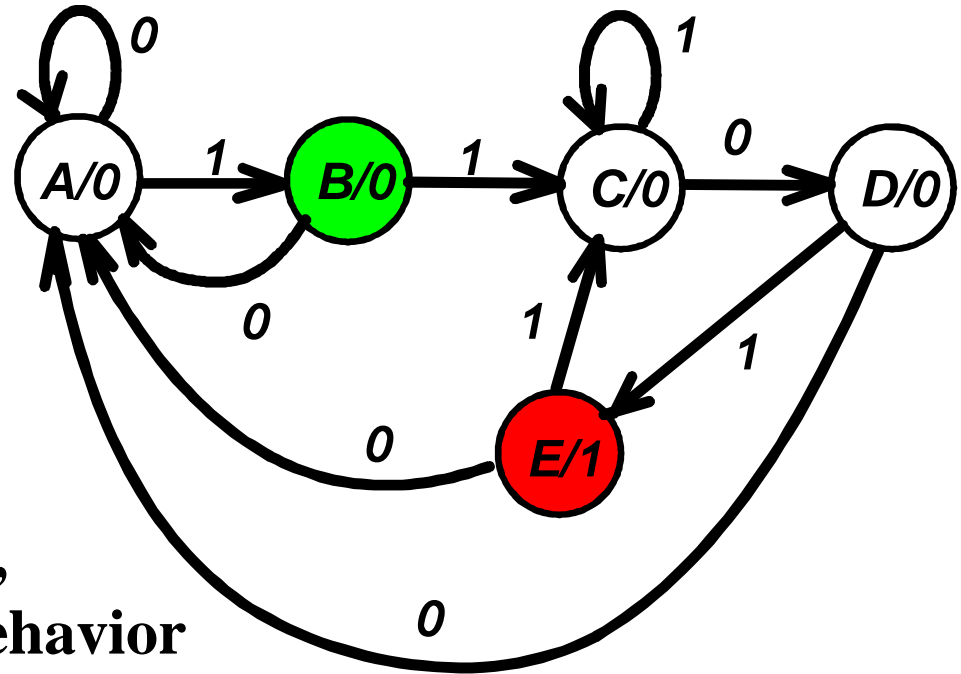
Example: Moore Model (continued)

- We mark outputs on states for Moore model
- Arcs now show only state transitions
- Add a new state **E** to produce the output 1
- Note that the new state, **E** produces the same behavior in the future as state **B**. But it gives a **different output** at the present time. Thus these states do represent a **different abstraction** of the input history.



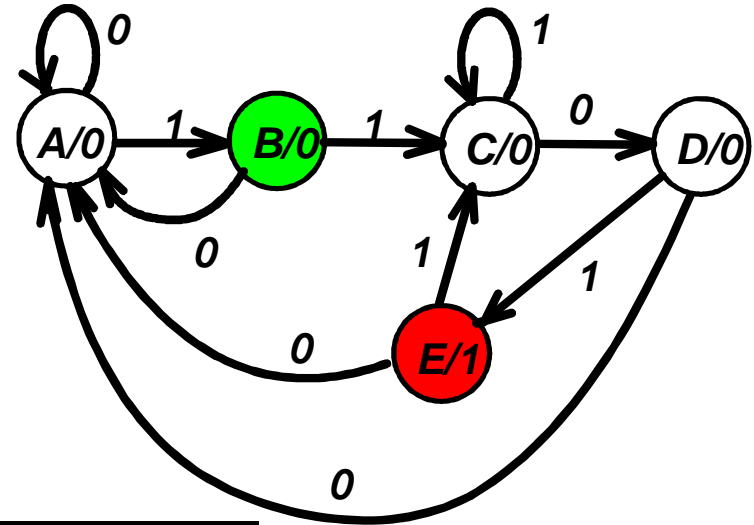Example: Moore Model (continued)


- The state table is shown below
- Memory aid re more state in the Moore model:
“Moore is More.”



<i>Present State</i>	<i>Next State</i>		<i>Output y</i>
	<i>x=0</i>	<i>x=1</i>	
<i>A</i>	<i>A</i>	<i>B</i>	<i>0</i>
<i>B</i>	<i>A</i>	<i>C</i>	<i>0</i>
<i>C</i>	<i>D</i>	<i>C</i>	<i>0</i>
<i>D</i>	<i>A</i>	<i>E</i>	<i>0</i>
<i>E</i>	<i>A</i>	<i>C</i>	<i>1</i>



Course Outline

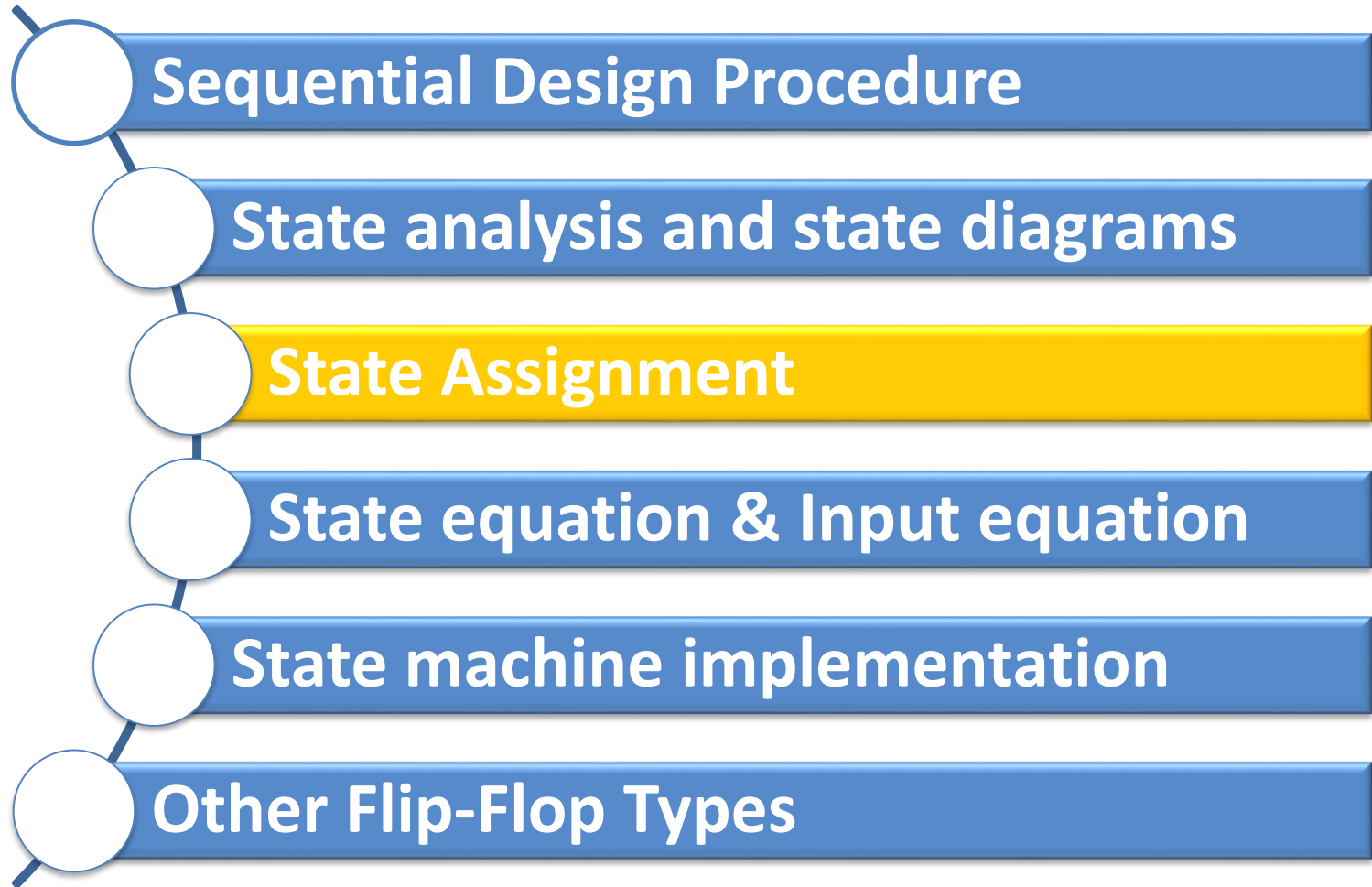



State Assignment

- Each of the m states must be assigned a unique code
- Minimum number of bits required is n such that
$$n \geq \lceil \log_2 m \rceil$$
where $\lceil x \rceil$ is the smallest integer $\geq x$
- There are useful state assignments that use more than the minimum number of bits
- There are $2^n - m$ unused states

State Assignment – Mealy

<i>Present State</i>	<i>Next State</i>		<i>Output</i>	
	<i>x=0</i>	<i>x=1</i>	<i>x=0</i>	<i>x=1</i>
<i>A</i>	<i>A</i>	<i>B</i>	<i>0</i>	<i>0</i>
<i>B</i>	<i>A</i>	<i>B</i>	<i>0</i>	<i>1</i>

- ❑ How many assignments of codes with a minimum number of bits?
 - Two : $A = 0, B = 1$ or $A = 1, B = 0$
- ❑ Does it make a difference?
 - Only in variable inversion, so small, if any.

State Assignment – Moore

<i>Present State</i>	<i>Next State</i>		<i>Output</i>	
	<i>x=0</i>	<i>x=1</i>	<i>x=0</i>	<i>x=1</i>
<i>A</i>	<i>A</i>	<i>B</i>	<i>0</i>	<i>0</i>
<i>B</i>	<i>A</i>	<i>C</i>	<i>0</i>	<i>0</i>
<i>C</i>	<i>D</i>	<i>C</i>	<i>0</i>	<i>0</i>
<i>D</i>	<i>A</i>	<i>B</i>	<i>0</i>	<i>1</i>

- How many assignments of codes with a minimum number of bits?
 - $4 \times 3 \times 2 \times 1 = 24$
- Does code assignment make a difference in cost?



Counting Order Assignment



State Assignment – Mealy

□ Counting Order Assignment:

$$A = 0\ 0, B = 0\ 1, C = 1\ 0, D = 1\ 1$$

□ The resulting coded state table:

Present State $Q_{1n}Q_{0n}$	Next State		Output(Z)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	1 1	1 0	0	0
1 1	0 0	0 1	0	1



Gray Code Assignment



State Assignment – Mealy

□ Gray Code Assignment:

$A = 0\ 0, B = 0\ 1, C = 1\ 1, D = 1\ 0$

□ The resulting coded state table:

Present State $Q_{1n}Q_{0n}$	Next State		Output(Z)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0 0	0 0	0 1	0	0
0 1	0 0	1 1	0	0
1 1	1 0	1 1	0	0
1 0	0 0	0 1	0	1



One-Hot Assignment

One Flip-flop per State : One-Hot Assignment



- Example codes for four states:

$(Y_3, Y_2, Y_1, Y_0) = 0001, 0010, 0100, \text{ and } 1000.$

- In equations, need to include **only** the variable **that** is **1** for the state.

- e. g., state with code 0001, is represented in equations by Y_0 instead of $\bar{Y}_3 \bar{Y}_2 \bar{Y}_1 Y_0$
- because all codes with 0 or two or more 1s have don't care next state values.

- Provides simplified analysis and design
- Combinational logic may be simpler, but flip-flop cost higher – may or may not be lower cost

State Assignment – Example 2

One-Hot



□ One-Hot Assignment :


A = 0001, B = 0010, C = 0100, D = 1000

The resulting coded state table:

Present State $Q_3Q_2Q_1Q_0$	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0001	0001	0010	0	0
0010	0001	0100	0	0
0100	1000	0100	0	0
1000	0001	0010	0	1



Course Outline

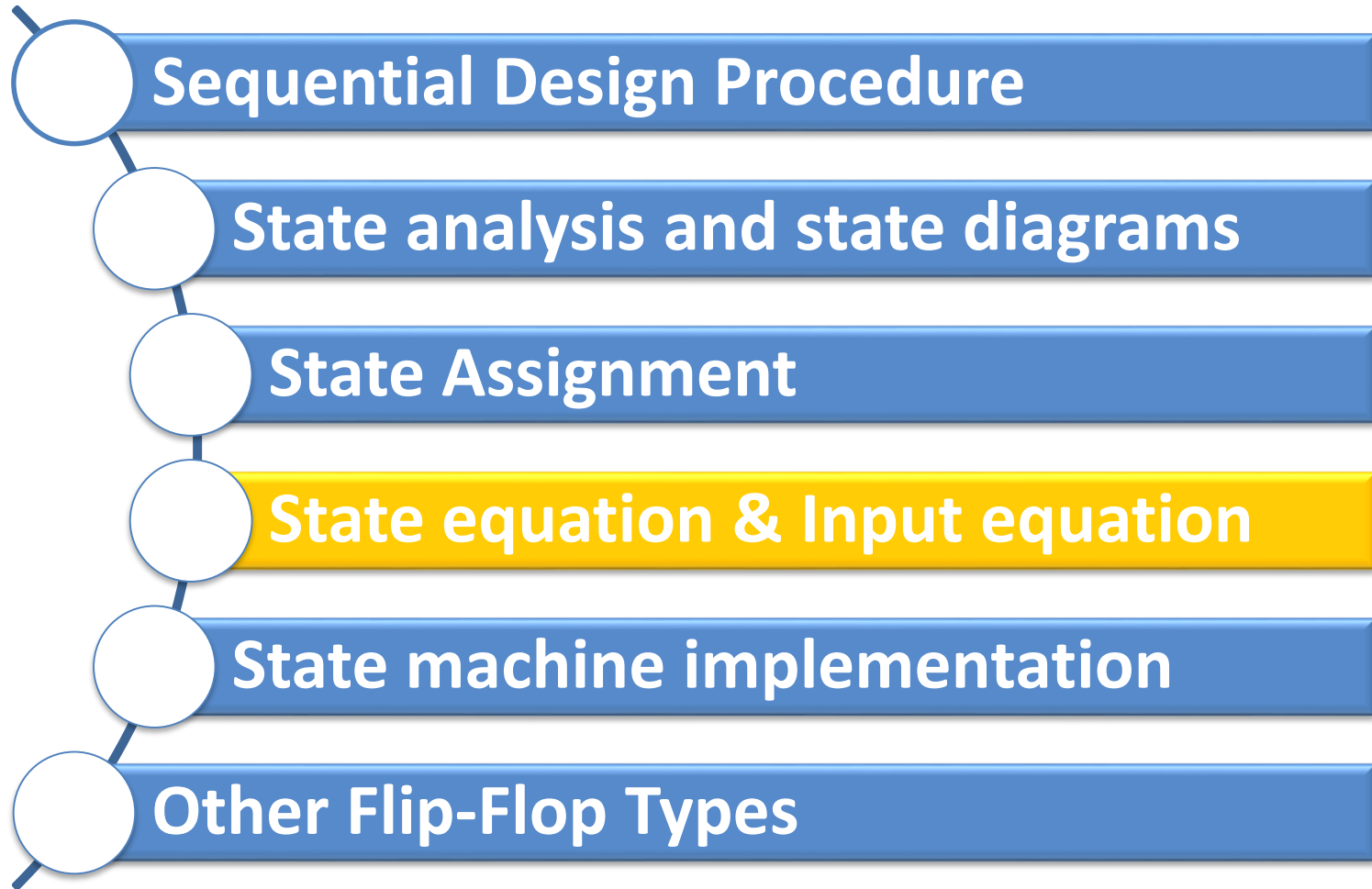



State Equation

For counting order

State & Input equation and Output Equations: –Counting Order Assignment



- Assume D flip-flops $Q^{(n+1)} = D$
- Interchange the bottom two rows of the state table, to obtain K-maps for $D_1(Q_1^{n+1})$, $D_2(Q_2^{n+1})$, and Z :

1. State equation
2. Choose Flip-Flop
3. Input equation

$D_1(Q_1^{n+1})$

	X	
	0	0
	0	1
Y_2	0	0
Y_1	1	1

$D_2(Q_2^{n+1})$

	X	
	0	1
	0	0
Y_2	0	1
Y_1	1	0

Z

	X	
	0	0
	0	0
Y_2	0	0
Y_1	0	1

□ Performing two-level optimization: $Q^{(n+1)} = D$

$$D_1(Q_1^{n+1})$$

	X	
	0	0
	0	1
Y_2	0	0
Y_1	1	1

$$D_2(Q_1^{n+1})$$

	X	
	0	1
	0	0
Y_2	0	1
Y_1	1	0

$$Z$$

	X	
	0	0
	0	0
Y_2	0	0
Y_1	0	1

$$D_1 = Y_1 \bar{Y}_2 + X \bar{Y}_1 Y_2$$

$$D_2 = \bar{X} Y_1 \bar{Y}_2 + X \bar{Y}_1 \bar{Y}_2 + X Y_1 Y_2$$

$$Z = X Y_1 \bar{Y}_2$$

Gate Input Cost = 22



State Equation for Gray Code order

State & Input Equation and Output Equations : –Gray Code Assignment



- Assume D flip-flops
- Obtain K-maps for $D_1(Q_1^{n+1})$, $D_2(Q_2^{n+1})$, and Z :

$D_1(Q_1^{n+1})$

		X	
	0	0	
	0	1	
Y_1	1	1	Y_2
	0	0	

$D_2(Q_2^{n+1})$

		X	
	0	1	
	0	1	
Y_1	0	1	Y_2
	0	1	

Z

		X	
	0	0	
	0	0	
Y_1	0	0	Y_2
	0	1	

Present State $Q_1 Q_0$	Next State		Output(Z)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0 0	0 0	0 1	0	0
0 1	0 0	1 1	0	0
1 1	1 0	1 1	0	0
1 0	0 0	0 1	0	1

□ Performing two-level optimization:

$D_1(Q_1^{n+1})$

	X
Y_2	0
Y_1	0
0	0
1	1
0	0
1	1

$D_2(Q_1^{n+1})$

	X
Y_2	0
Y_1	0
0	1
1	1
0	1
1	1

Z

	X
Y_2	0
Y_1	0
0	0
1	0
0	0
1	1

$$D_1 = Y_1 Y_2 + X Y_2$$

$$D_2 = X$$

$$Z = X Y_1 \bar{Y}_2$$

Gate Input Cost = 9


Map Technology Gray Code Assignment



Library:


- D Flip-flops with Reset (**not inverted**)
- NAND gates with up to 4 inputs and inverters

Initial Circuit:

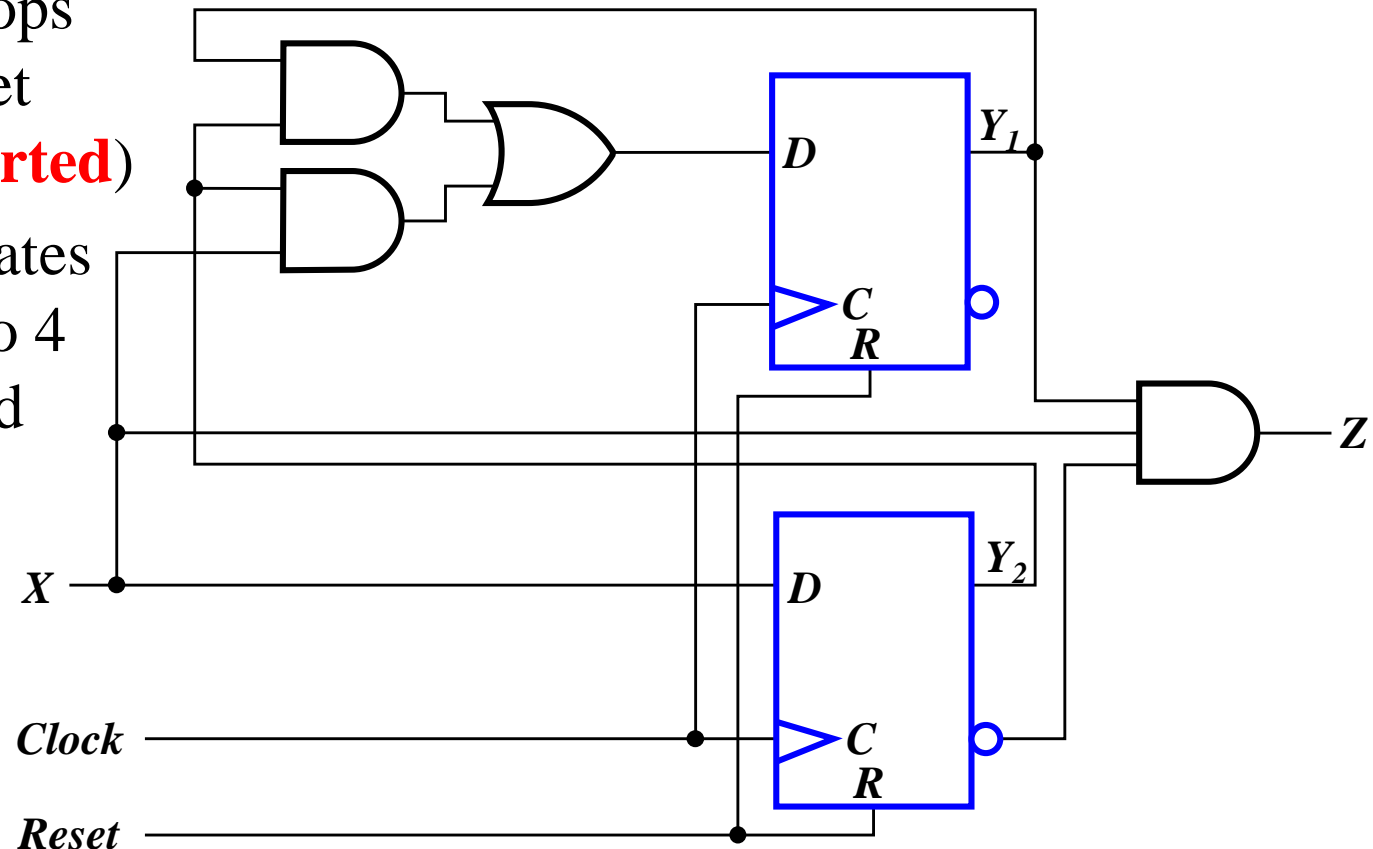

Mapped Circuit - Final Result

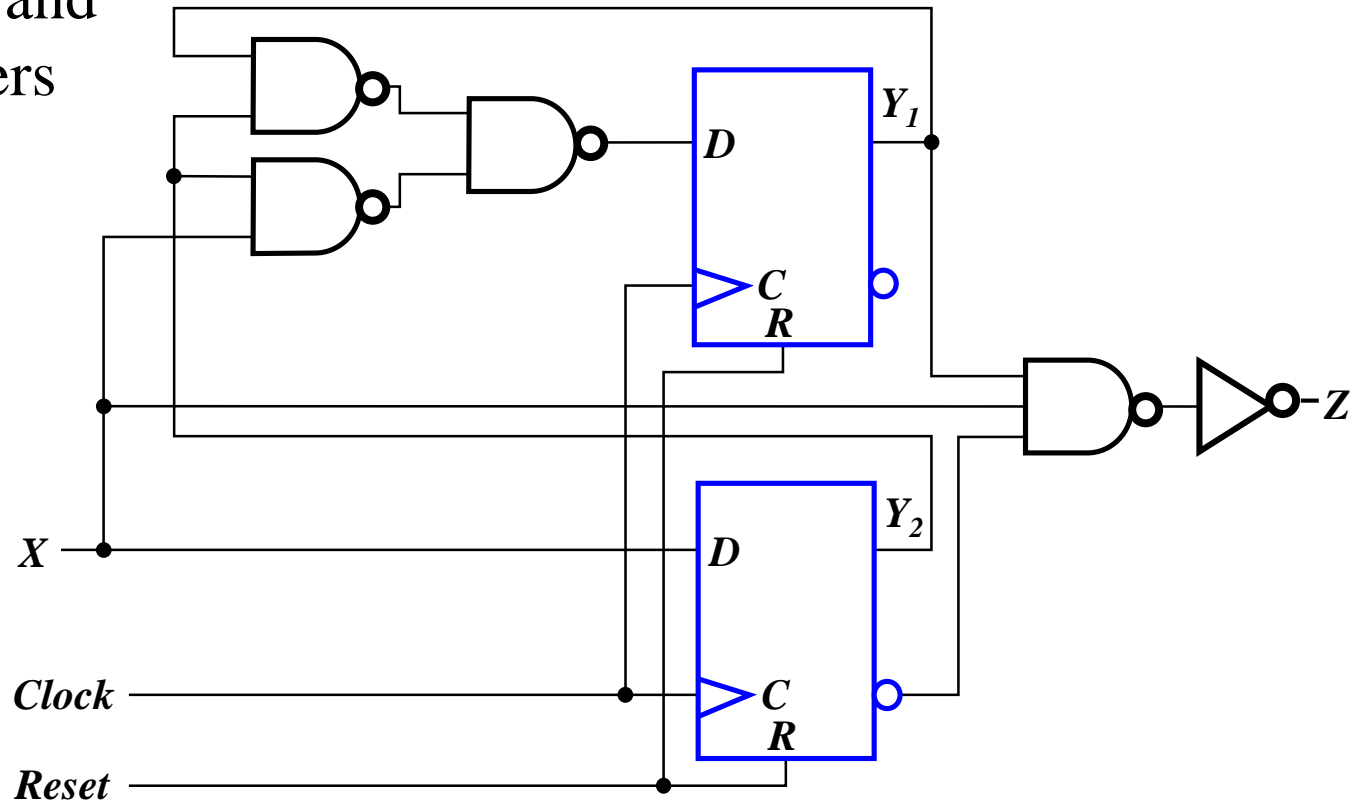- NAND gates with up to 4 inputs and inverters





State Equation

for One Hot assignment



- Equations read from 1 next state variable entries in table:

$$D_0 = X(Y_0 + Y_1 + Y_3) \text{ or } X \bar{Y}_2$$

$$D_1 = \bar{X}(Y_0 + Y_3)$$

$$D_2 = X(Y_1 + Y_2) \text{ or } X(\overline{Y_0 + Y_3})$$

$$D_3 = \bar{X} Y_2$$

$$Z = XY_3 \text{ Gate Input Cost} = 15$$

- Combinational cost intermediate plus cost of two more flip-flops needed.



Examples

Sequential Design


Sequential Design: Example 1

□ Design a sequential Counter

□ Definitions:

- 4-bit binary synchronous counter
- With a Counter Overflow signal: R_c
- Input: No
- Output: $Q_D Q_C Q_B Q_A$ and R_c

□ State diagrams

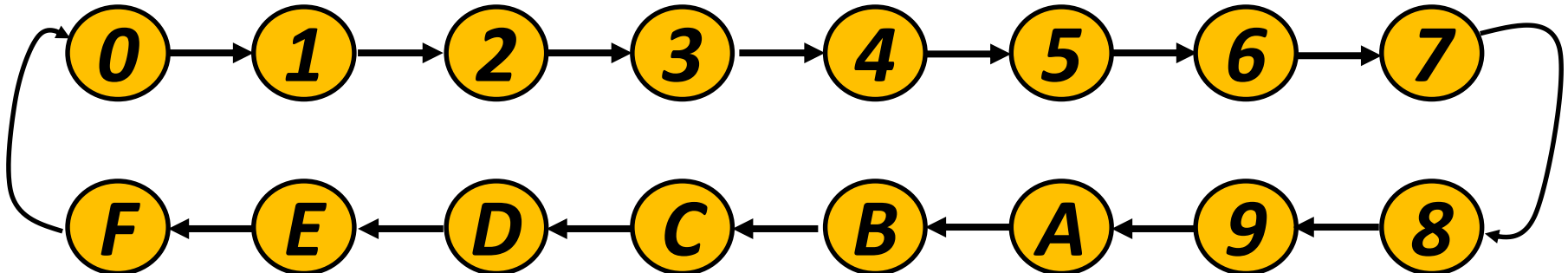




State Table and State Assignment

	Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
A	0	1	0	1	1	1	0	1
B	1	1	0	1	0	0	1	1
C	0	0	1	1	1	0	1	1
D	1	0	1	1	0	1	1	1
E	0	1	1	1	1	1	1	1
F	1	1	1	1	0	0	0	0

		D_A Q_B Q_A Gray Code				
		Q_D Q_C	00	01	11	10
Gray Code	00	1	2	4	3	
	01	5	6	8	7	
	11	D	E	0	F	
	10	9	A	C	B	

State and Output Equation : D_A


	Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
A	0	1	0	1	1	1	0	1
B	1	1	0	1	0	0	1	1
C	0	0	1	1	1	0	1	1
D	1	0	1	1	0	1	1	1
E	0	1	1	1	1	1	1	1
F	1	1	1	1	0	0	0	0

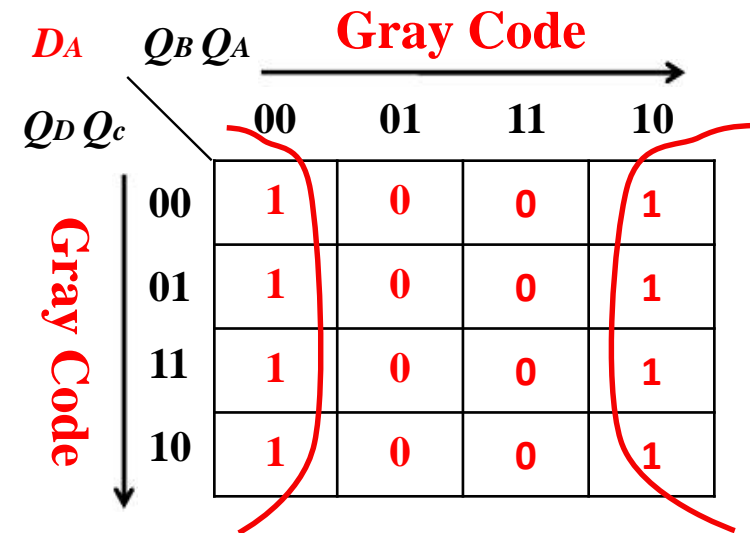



State and Output Equation : D_B


	Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
A	0	1	0	1	1	1	0	1
B	1	1	0	1	0	0	1	1
C	0	0	1	1	1	0	1	1
D	1	0	1	1	0	1	1	1
E	0	1	1	1	1	1	1	1
F	1	1	1	1	0	0	0	0

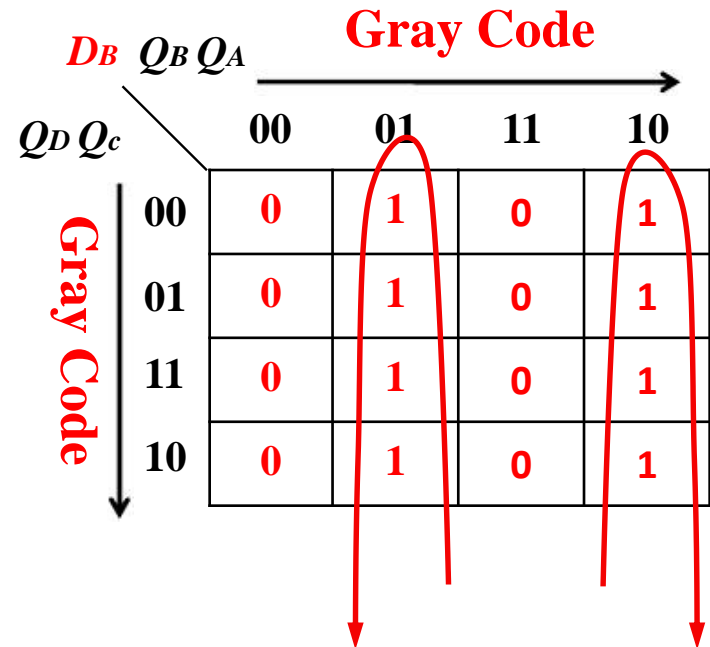

$$D_B = \overline{Q_B} Q_A + Q_B \overline{Q_A}$$
$$= \overline{\overline{Q_A} \oplus \overline{Q_B}}$$

State and Output Equation : D_C


	Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
A	0	1	0	1	1	1	0	1
B	1	1	0	1	0	0	1	1
C	0	0	1	1	1	0	1	1
D	1	0	1	1	0	1	1	1
E	0	1	1	1	1	1	1	1
F	1	1	1	1	0	0	0	0

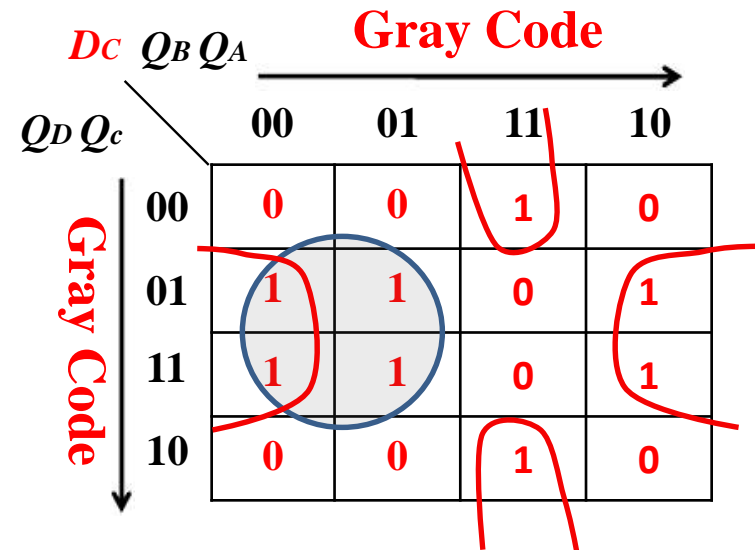

$$\begin{aligned}
 D_C &= \overline{Q_A}Q_C + \overline{Q_B}Q_C + Q_AQ_B\overline{Q_C} \\
 &= \overline{(\overline{Q_A} + \overline{Q_B})} \oplus \overline{Q_C}
 \end{aligned}$$

State and Output Equation: D_C

	Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0
2	0	1	0	0	1	1	0	0
3	1	1	0	0	0	0	1	0
4	0	0	1	0	1	0	1	0
5	1	0	1	0	0	1	1	0
6	0	1	1	0	1	1	1	0
7	1	1	1	0	0	0	0	1
8	0	0	0	1	1	0	0	1
9	1	0	0	1	0	1	0	1
A	0	1	0	1	1	1	0	1
B	1	1	0	1	0	0	1	1
C	0	0	1	1	1	0	1	1
D	1	0	1	1	0	1	1	1
E	0	1	1	1	1	1	1	1
F	1	1	1	1	0	0	0	0

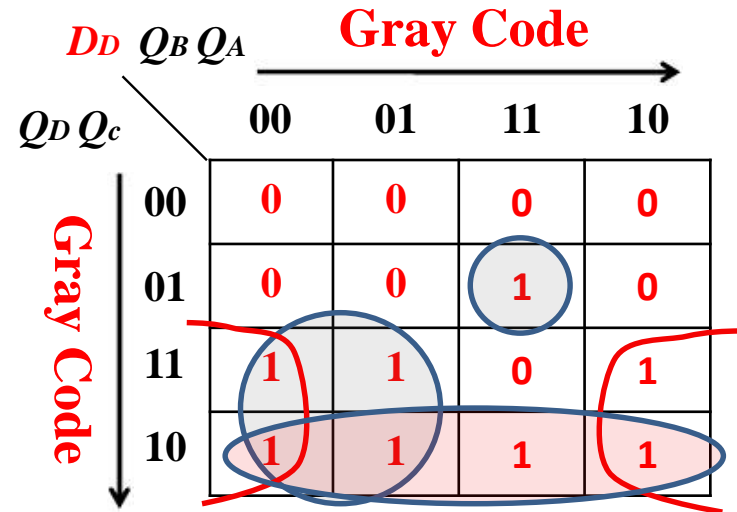

$$\begin{aligned}
 D_D &= \overline{Q_A}Q_D + \overline{Q_B}Q_D + \overline{Q_C}Q_D + Q_AQ_BQ_C\overline{Q_D} \\
 &= (\overline{\overline{Q_A} + \overline{Q_B} + \overline{Q_C}}) \oplus \overline{Q_D}
 \end{aligned}$$



Excitation function (Input Equation)

◎ Excitation function :

☞ According to D flip-flop characteristic equation: $Q_{n+1} = D_n$

$$D_A = \overline{Q_A}$$

$$D_B = \overline{Q_A}Q_B + Q_A\overline{Q_B} = \overline{\overline{Q_A} \oplus \overline{Q_B}}$$


$$D_C = \overline{Q_A}Q_C + \overline{Q_B}Q_C + Q_AQ_B\overline{Q_C} = \overline{(\overline{Q_A} + \overline{Q_B}) \oplus \overline{Q_C}}$$

$$D_D = \overline{Q_A}Q_D + \overline{Q_B}Q_D + \overline{Q_C}Q_D + Q_AQ_BQ_C\overline{Q_D} = \overline{(\overline{Q_A} + \overline{Q_B} + \overline{Q_C}) \oplus \overline{Q_D}}$$

$$R_C = \overline{\overline{Q_A} + \overline{Q_B} + \overline{Q_C} + \overline{Q_D}}$$

4-bit binary counter

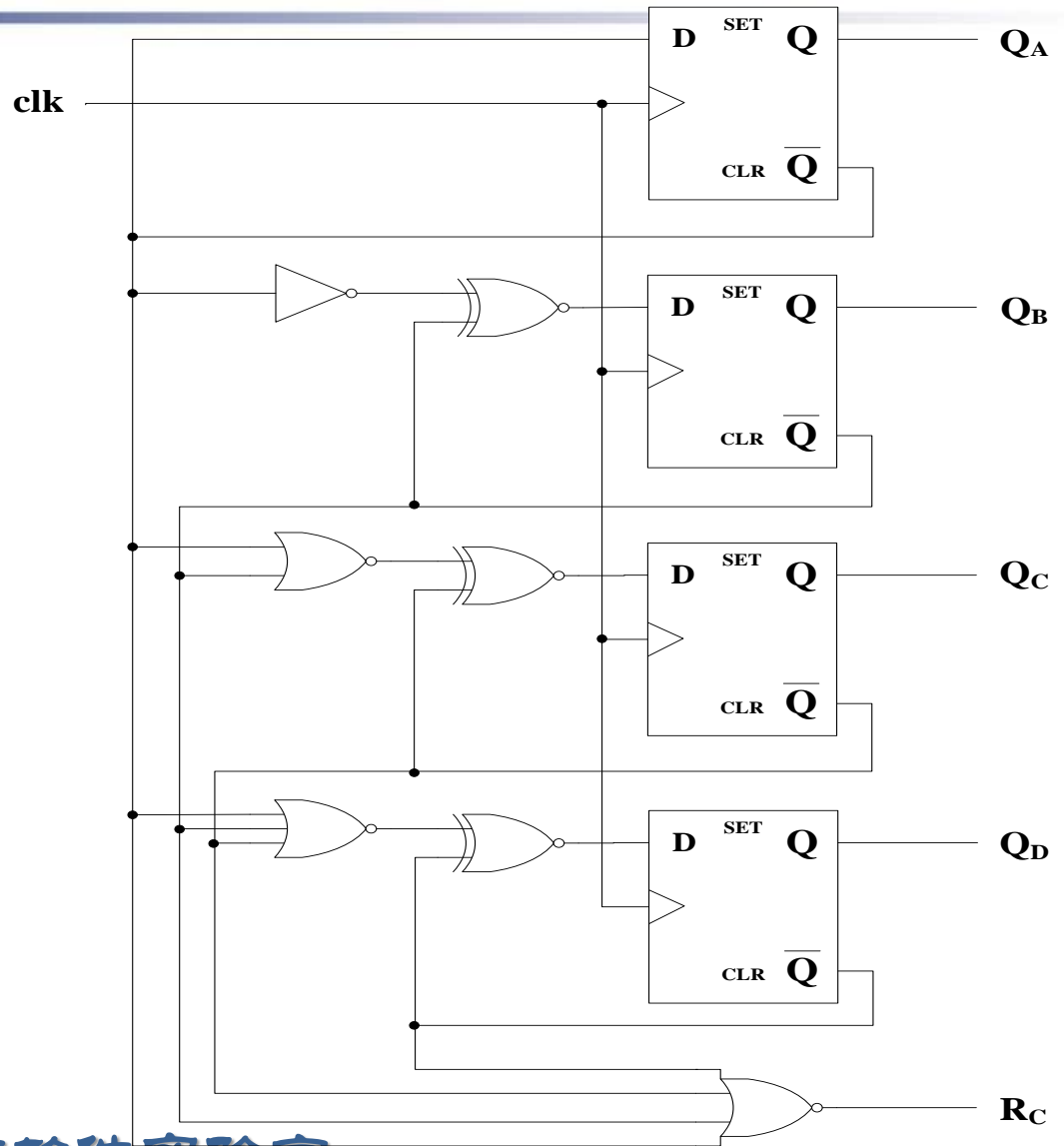4-bit binary synchronous counter logic diagram



4 synchronous counter structured instance description



```
module counter_4bit(clk, Qa, Qb, Qc, Qd, Rc);  
.....          //端口及变量定义  
FD              FD_A (.C(clk),.D(Da),.Q(Qa)),  
                  FD_B (.C(clk),.D(Db),.Q(Qb)),  
                  FD_C (.C(clk),.D(Dc),.Q(Qc)),  
                  FD_D (.C(clk),.D(Dd),.Q(Qd));  
  
defparam FD_A.INIT = 1'b0;          // define initial value of the D type Flip-Flop  
defparam FD_B.INIT = 1'b0;  
defparam FD_C.INIT = 1'b0;  
defparam FD_D.INIT = 1'b0;  
  
INV            nQa_L (.I(Qa), .O(nQa)),          //4个非门  
                  nQb_L (.I(Qb), .O(nQb)),  
                  nQc_L (.I(Qc), .O(nQc)),  
                  nQd_L (.I(Qd), .O(nQd));  
  
assign Da = nQa;  
  
XNOR2          Db_L (.I0(Qa), .I1(nQb), .O(Db)),          //2输入异或非  
                  Dc_L (.I0(Nor_nQa_nQb), .I1(nQc), .O(Dc)),  
                  Dd_L (.I0(Nor_nQa_nQb_nQc), .I1(nQd), .O(Dd));  
  
NOR4           Rc_L (.I0(nQa), .I1(nQb), .I2(nQc), .I3(nQd), .O(Rc));          //4输入或非门  
NOR2           Nor_nQa_nQb_L (.I0(nQa), .I1(nQb), .O(Nor_nQa_nQb));          //2输入或非门  
NOR3           Nor_nQa_nQb_nQc_L  
                  (.I0(nQa), .I1(nQb), .I2(nQc), .O(Nor_nQa_nQb_nQc));  
  
endmodule
```



Sequential Design: Example 2

□ Design a sequential modulo 3 accumulator for 2-bit operands


□ Definitions:

- Modulo n adder - an adder that gives the result of the addition as the remainder of the sum divided by n
 - Example: $2 + 2$ modulo 3 = remainder of $4/3 = 1$
- Accumulator - a circuit that “accumulates” the sum of its input operands over time - it adds each input operand to the stored sum, which is initially 0.

□ Stored sum: (Y_1, Y_0) , Input: (X_1, X_0) , Output:
 (Z_1, Z_0)

Example 3 (continued)

□ Complete the state diagram:

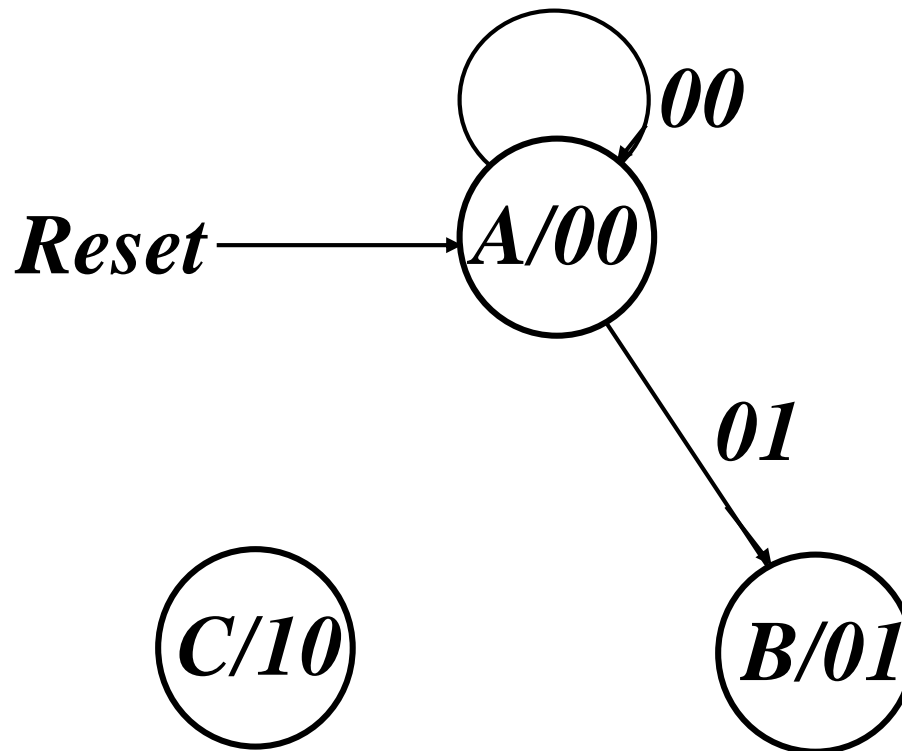

Example 3 (continued)

□ Complete the state table



X_1X_0 Y_1Y_0	00	01	11	10	Z_1Z_0
	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	$Y_1(t+1),$ $Y_0(t+1)$	
A (00)	00		X		00
B (01)			X		01
- (11)	X	X	X	X	11
C (10)			X		10

□ State Assignment: $(Y_1, Y_0) = (Z_1, Z_0)$

□ Codes are in gray code order to ease use of K-maps in the next step

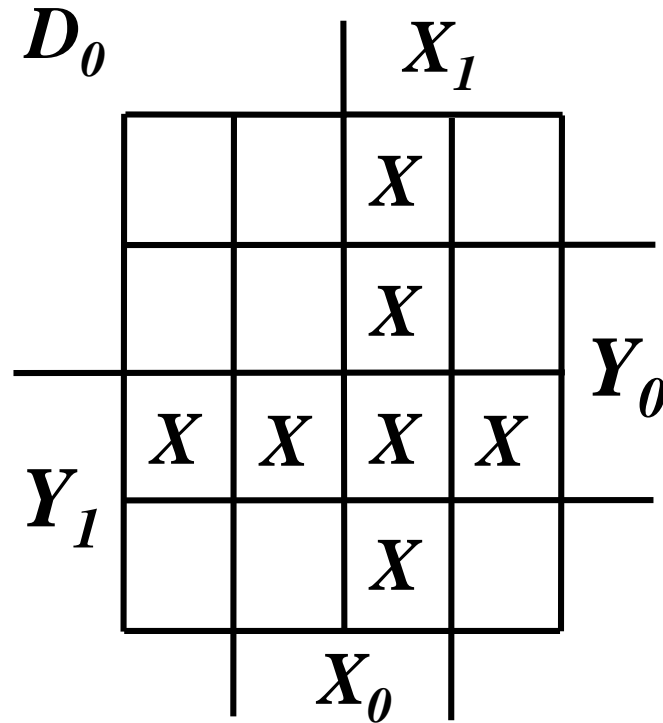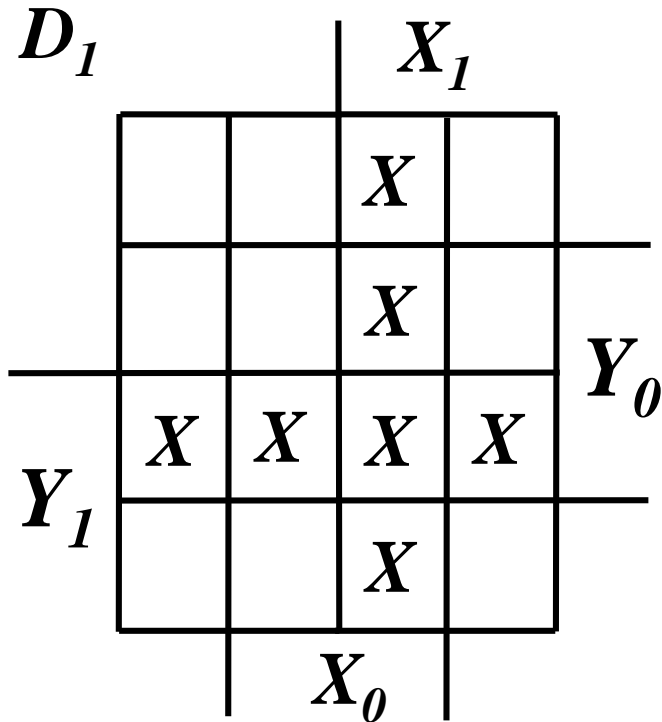Example 3 (continued)


- Find optimized flip-flop input equations for D flip-flops




- $D_1 =$

- $D_0 =$

Circuit - Final Result with AND, OR, NOT

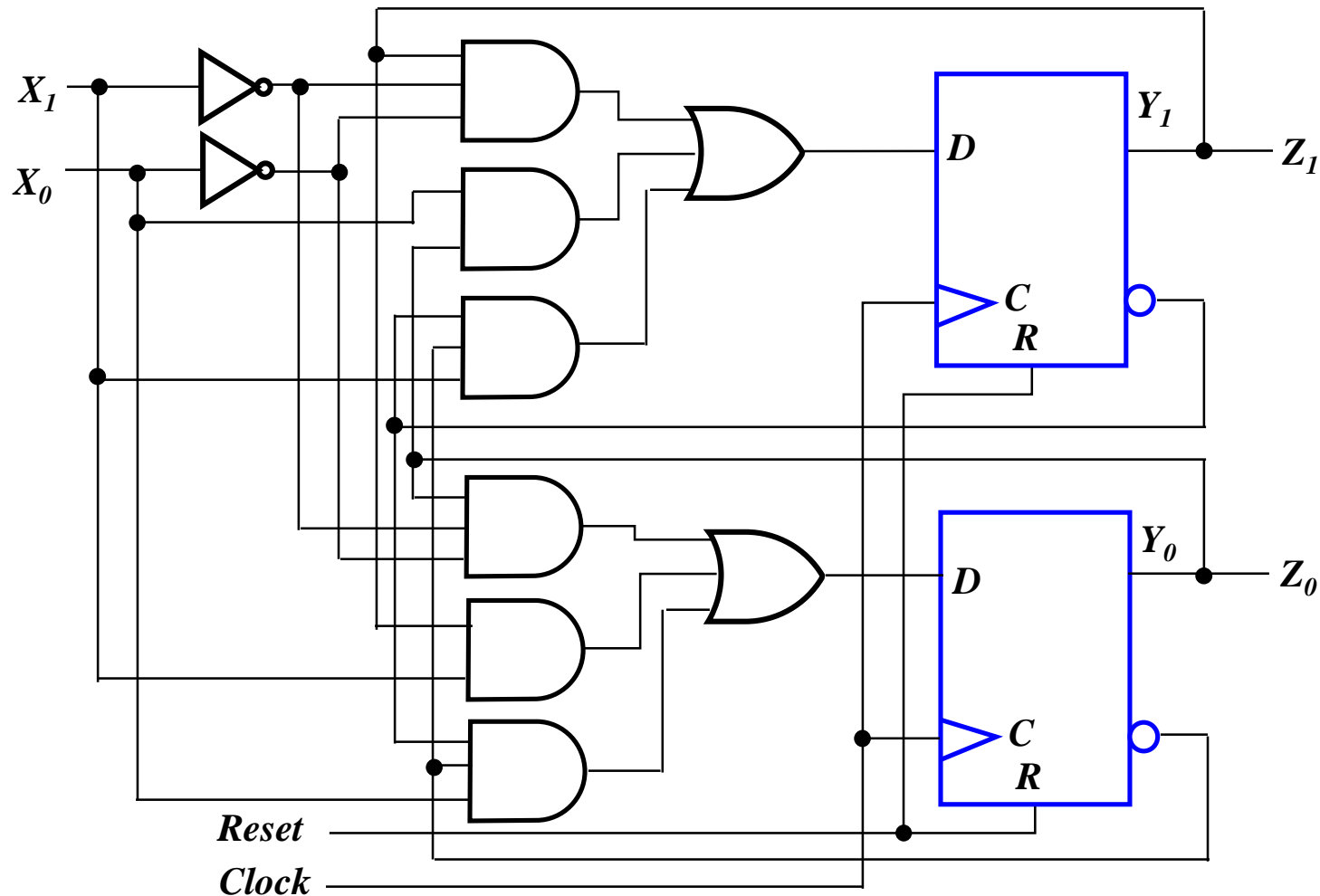


Course Outline

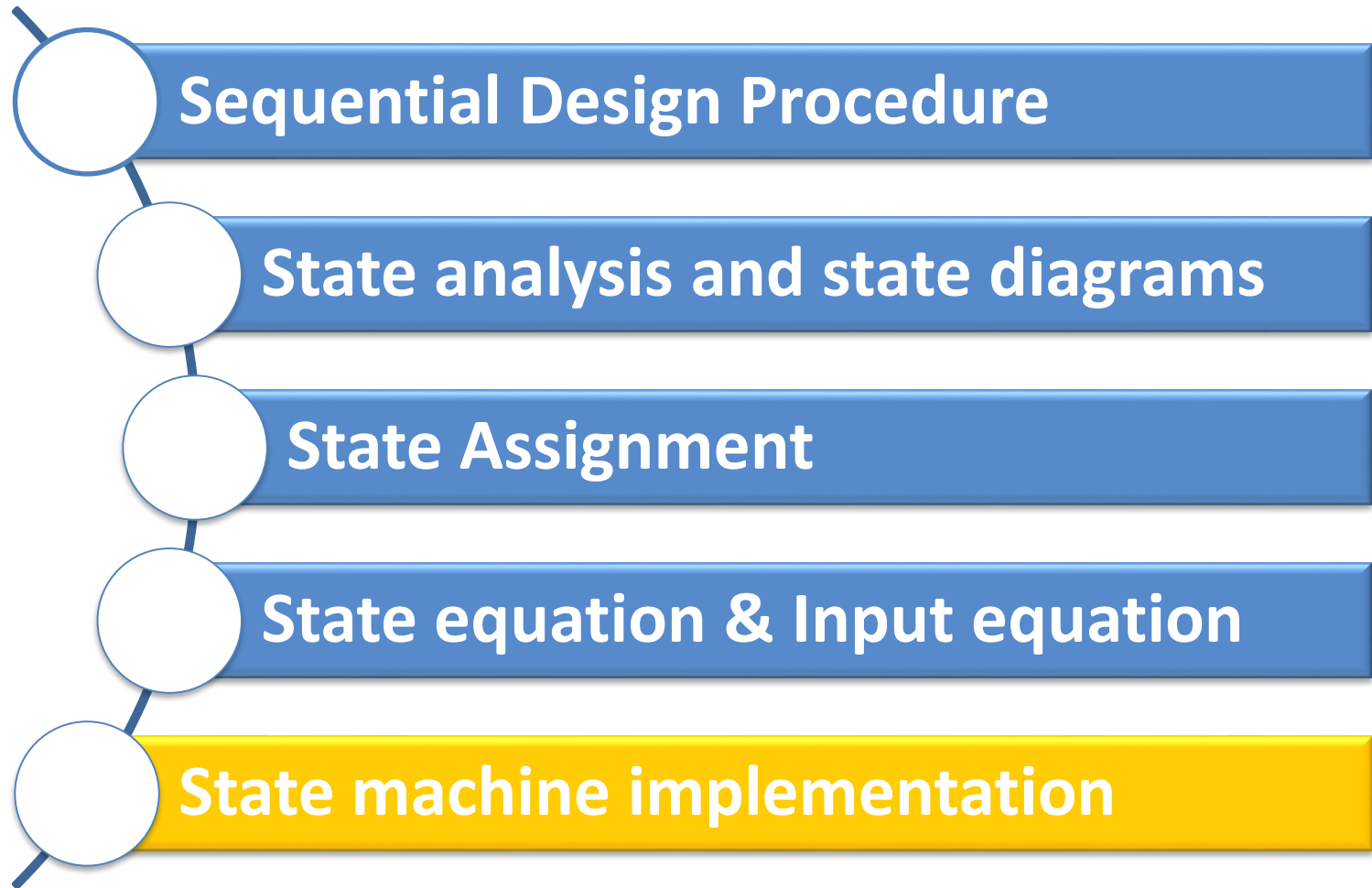


State machine description -1

□ The structure -- Mealy Model

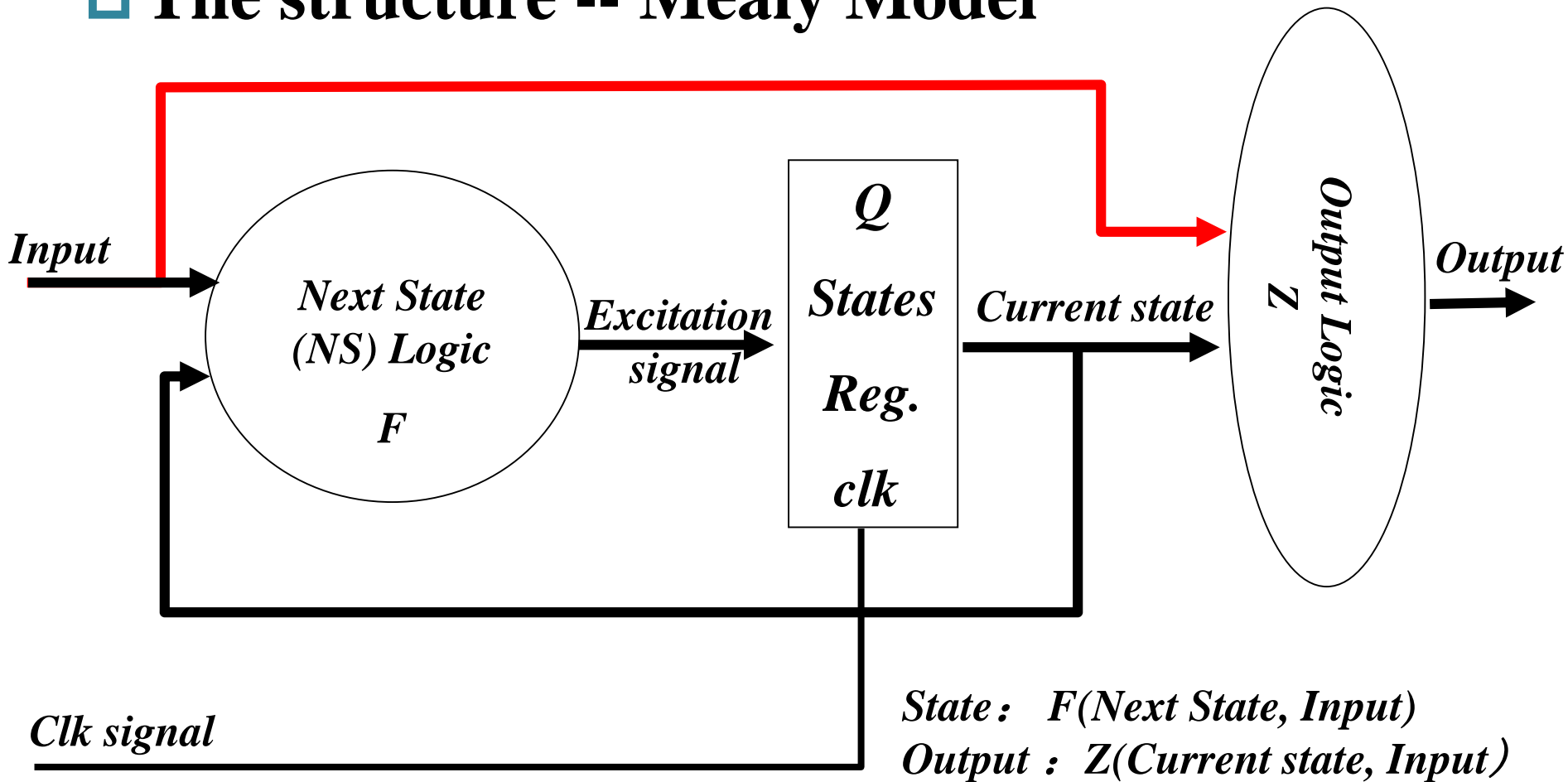

State machine description -2

□ The structure -- Moore Model

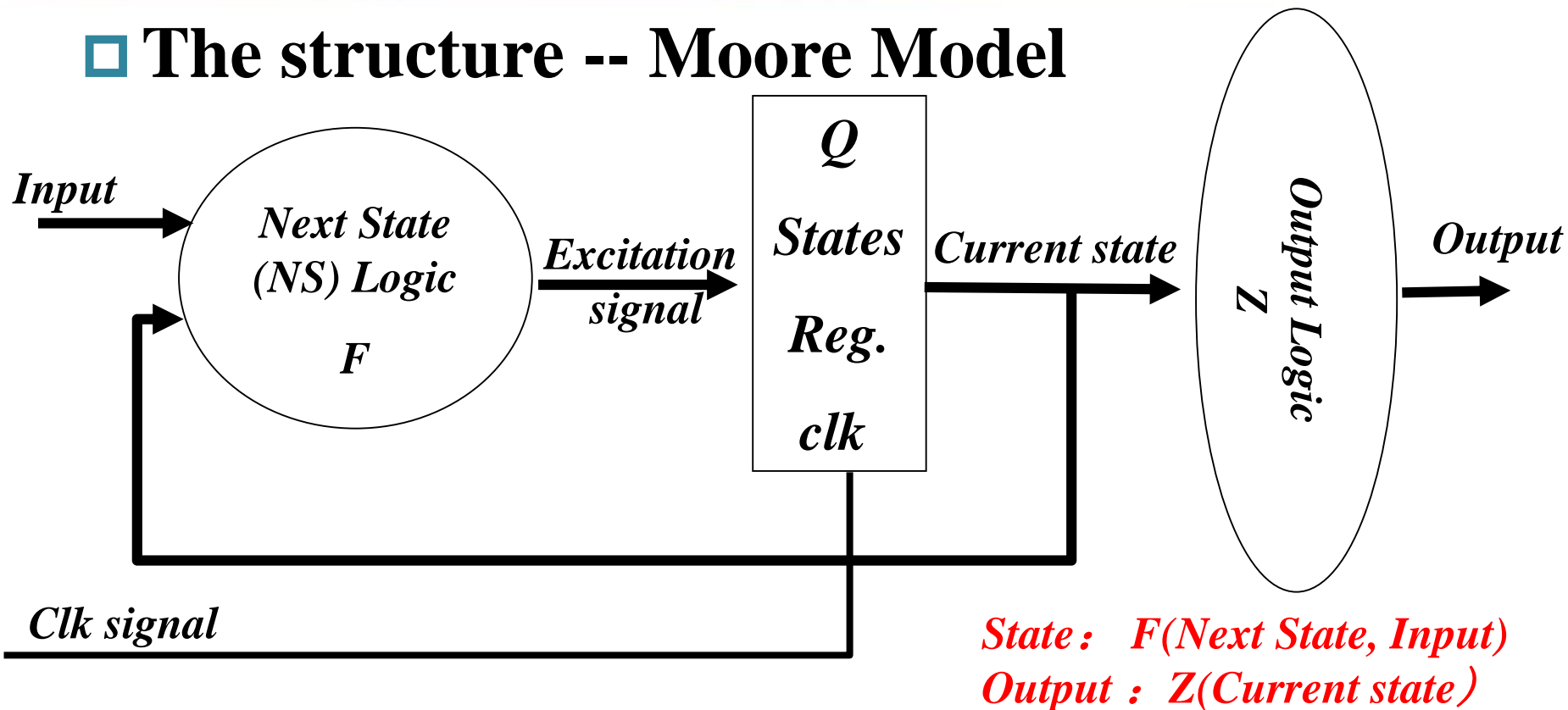


In the high-speed circuit design, the states are used directly as the output

- *the pipeline*
- *Output signal is fully synchronized with the clock*

State machine description -3


□ The Pipeline structure -- Mealy Model

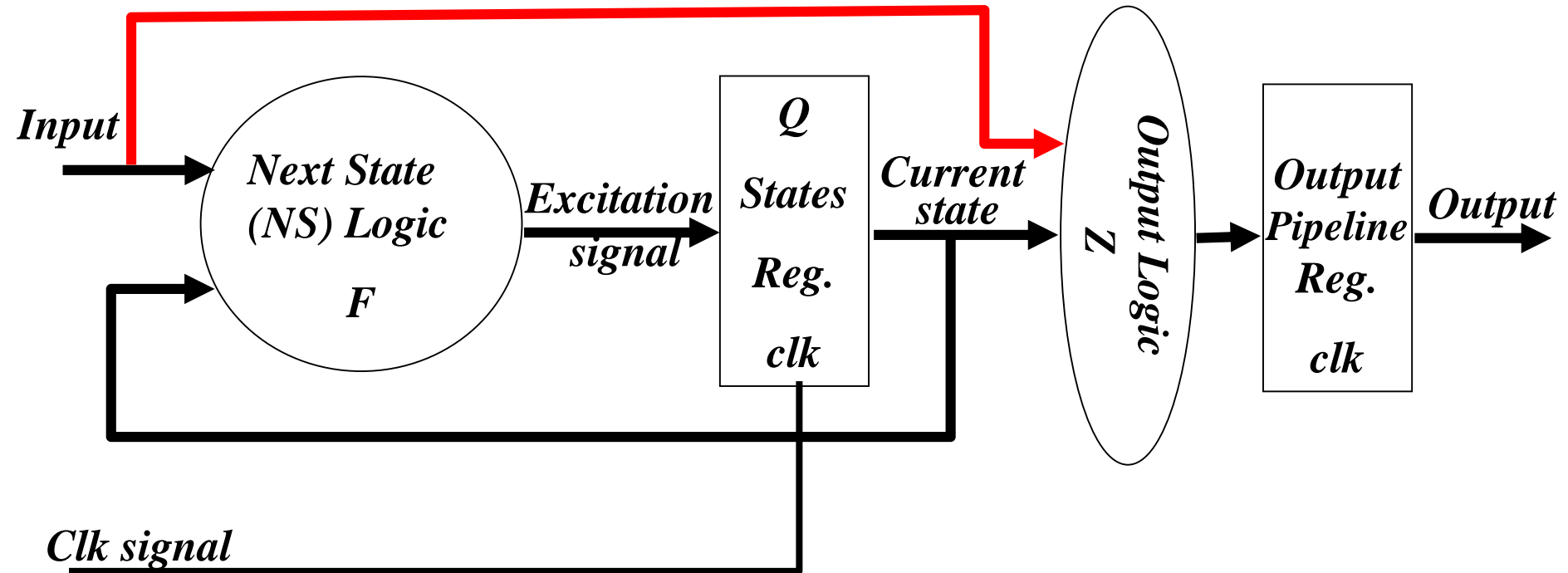

In the design of high-speed circuit, it is often necessary so that the state machine output almost completely synchronized with the clock. There is a way to be used directly as the output of the state variables.

Verilog HDL synthesis state machine

Assume a state machine:

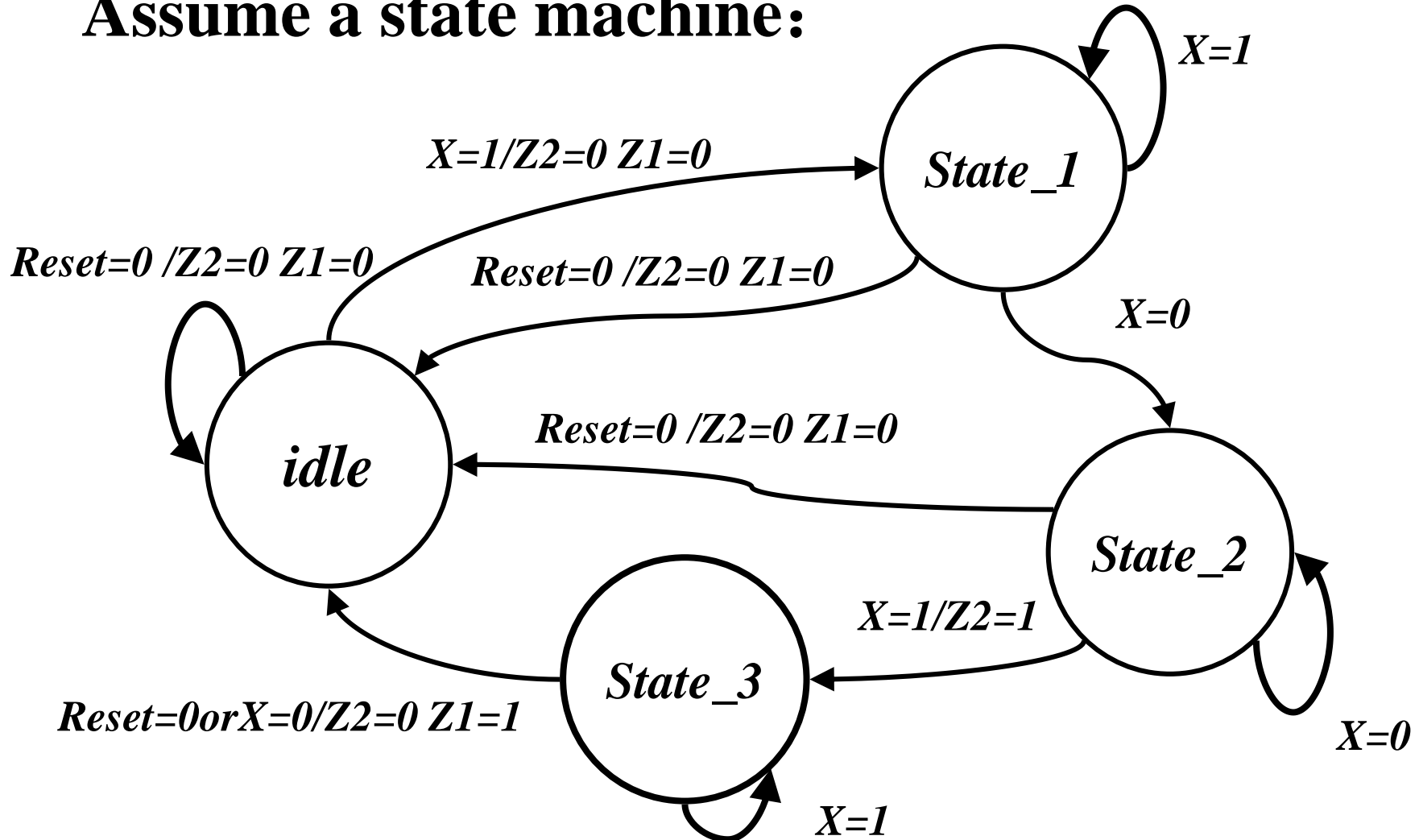

Verilog HDL synthesis state machine 1:

--Gray Code



```
module fsm (Clock, Reset, X, Z2, Z1);
  input Clock, Reset, X;
  output Z2, Z1;
  reg Z2, Z1;
  reg [1:0] state ;
  parameter Idle = 2'b00, State_1 = 2'b01,
    State_2 = 2'b10, State_3 = 2'b11;
  always @(posedge Clock)
    if (!Reset)
      begin
        state <= Idle; Z2<=0; Z1<=0;
      end
    else
      case (state)
        Idle: begin
          if (X) begin
            state <= State_1;
            Z1<=0;
          end
          else state <= Idle;
        end
      endcase
    end
```

```
    State_1: begin
      if (!X) state <= State_2;
      else state <= State_1;
    end
    State_2: begin
      if (X) begin
        state <= State_3;
        Z2<= 1;
      end
      else state <= State_2;
    end
    State_3: begin
      if (!X) begin
        state <=Idle;
        Z2<=0; Z1<=1;
      end
      else state <= State_3;
    end
  endcase
endmodule
```

Verilog HDL synthesis state machine 2:

--one-hot Code



```
module fsm (Clock, Reset, X, Z2, Z1);
  input Clock, Reset, X;
  output Z2, Z1;
  reg Z2, Z1;
  reg [3:0] state ;
  parameter Idle = 4'b1000, State_1 = 4'b0100,
            State_2 = 4'b0010, State_3 = 4'b0001;
  always @(posedge clock)
    if (!Reset)
      begin
        state <= Idle; Z2<=0; Z1<=0;
      end
    else
      case (state)
        Idle: begin
          if (X) begin
            state <= State_1;
            Z1<=0;
          end
          else state <= Idle;
        end
      endcase
end
```

```
State_1: begin
  if (!X) state <= State_2;
  else state <= State_1;
end
State_2: begin
  if (X) begin
    state <= State_3;
    Z2<= 1;
  end
  else state <= State_2;
end
State_3: begin
  if (!X) begin
    state <=Idle;
    Z2<=0; Z1<=1;
  end
  else state <= State_3;
end
default: state <=Idle;
endcase
```

endmodule

Verilog HDL synthesis state machine 3:



----State Code as Output

```
module fsm (Clock, Reset, X, Z2, Z1);  
input Clock, Reset, X;  
output Z2, Z1;  
reg [3:0] state ;  
    assign Z2= state[3];  
    // 把状态变量的最高位用作输出Z2  
    assign Z1= state[0];  
    // 把状态变量的最低位用作输出Z1  
parameter // Z2_S2_S1_Z1  
    zero    = 4'b0000,  
    Idle    = 4'b0001,  
    State_1 = 4'b0100,  
    State_2 = 4'b0010,  
    State_3 = 4'b1000;  
always @(posedge Clock)  
    if (!Reset)  
        begin  
            state <= Zero;  
        end  
    else  
        case (state)  
            Idle,Zero: begin
```

```
                if (X) begin  
                    state <= State_1;  
                end  
                else state <= Idle;  
            end  
        State_1: begin  
            if (!X) state <= State_2;  
            else state <= State_1;  
        end  
        State_2: begin if (X) begin  
                        state <= State_3;  
                    end  
            else state <= State_2;  
        end  
        State_3: begin if (!X) begin  
                        state <= Idle;  
                    end  
            else state <= State_3;  
        end  
        default: state <= Zero;  
    endcase  
endmodule
```

Verilog HDL synthesis state machine 4:



----Multi-output complex state machine

```
module fsm (Clock, Reset, X, Z2, Z1);  
  input Clock, Reset, X;  
  output Z2, Z1;  
  reg Z2, Z1;  
  reg [1:0] state ;  
  parameter  
    Idle = 2'b00, State_1 = 2'b01,  
    State_2 = 2'b10, State_3 = 2'b11;  
  always @(posedge Clock)  
    if (!Reset)  
      state <= Idle;  
    else  
      case (state)  
        Idle: begin if (X) begin  
                      state <= State_1;  
                    end  
                else state <= Idle;  
              end  
        State_1: begin  
                    if (!X) state <= State_2;  
                    else state <= State_1;  
                  end  
        State_2: begin  
                    if (X) state <= State_3;  
                    else state <= State_2;  
                  end  
        State_3: begin  
                    if (!X) state <= Idle;  
                    else state <= State_3;  
                  end  
        default: state <= 2'bxx;  
      endcase  
  always @(state or Reset) //产生输出Z2模块  
    if (!Reset) Z2=0;  
    else  
      if (state == State_3) Z2=1;  
      else Z2= 0;  
  always @(state or Reset) //产生输出Z1模块  
    if (!Reset) Z1=0;  
    else  
      if (state == Idle) Z1=1;  
      else Z1=0;  
endmodule
```


```
State_2: begin  
  if (X) state <= State_3;  
  else state <= State_2;  
end  
State_3: begin  
  if (!X) state <= Idle;  
  else state <= State_3;  
end  
default: state <= 2'bxx;  
endcase
```

```
always @(state or Reset) //产生输出Z2模块  
  if (!Reset) Z2=0;  
  else  
    if (state == State_3) Z2=1;  
    else Z2= 0;  
always @(state or Reset) //产生输出Z1模块  
  if (!Reset) Z1=0;  
  else  
    if (state == Idle) Z1=1;  
    else Z1=0;
```

endmodule



Course Outline

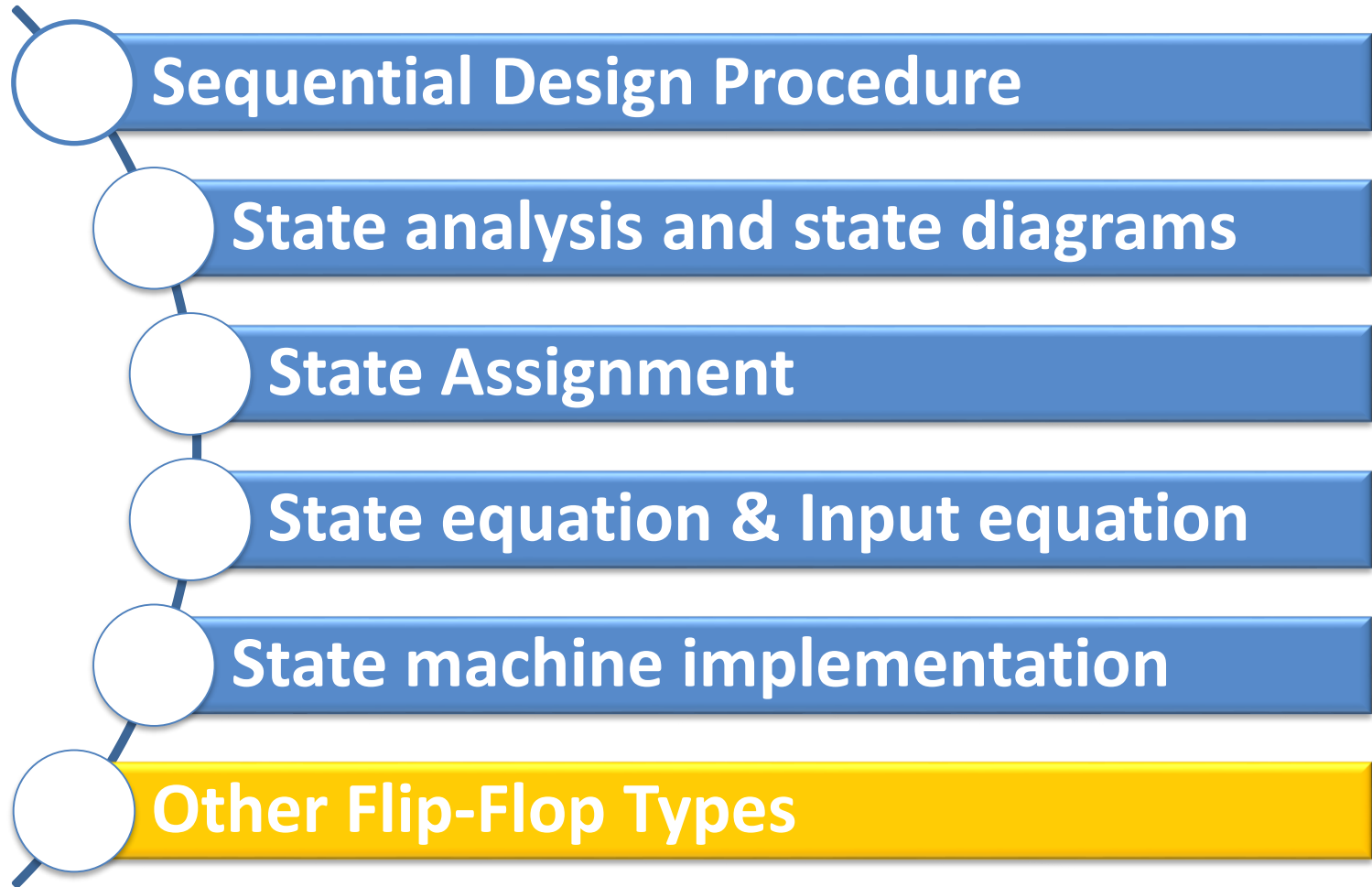



Other Flip-Flop Types

- **J-K and T flip-flops**
 - Behavior
 - Implementation
- **Basic descriptors for understanding and using different flip-flop types**
 - Characteristic tables
 - Characteristic equations
 - Excitation tables
- **For actual use, see Reading Supplement - Design and Analysis Using J-K and T Flip-Flops**



J-K Flip-flop


□ Behavior

- Same as S-R flip-flop with J analogous to S and K analogous to R
- **Except** that $J = K = 1$ is allowed, and
- For $J = K = 1$, the flip-flop changes to the *opposite state*
- As a master-slave, has same “**1s catching**” behavior as S-R flip-flop
- If the master changes to the **wrong state**, that state will be passed to the slave
 - E.g., if master falsely set by $J = 1, K = 1$ cannot reset it during the current clock cycle


J-K Flip-flop (continued)

□ Implementation

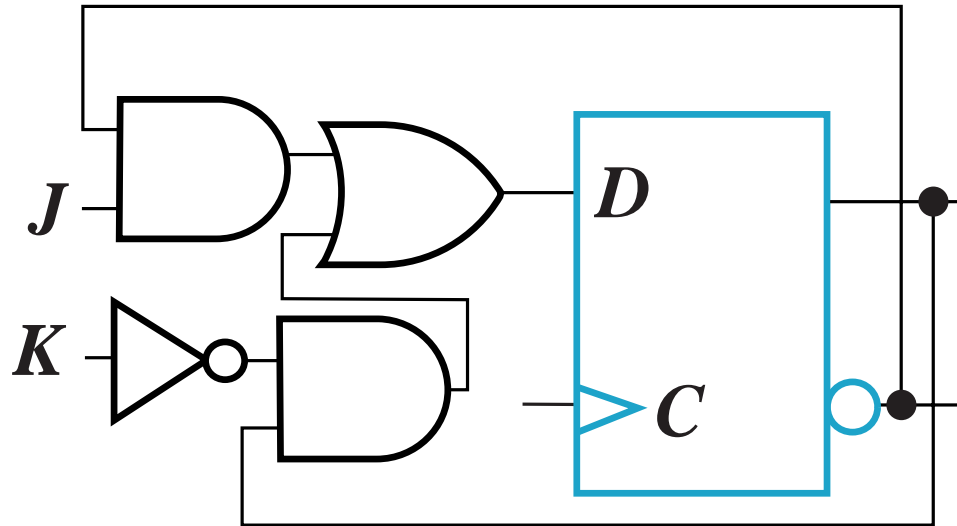- To avoid 1s catching behavior, one solution used is to use an edge-triggered D as the core of the flip-flop



■ Symbol

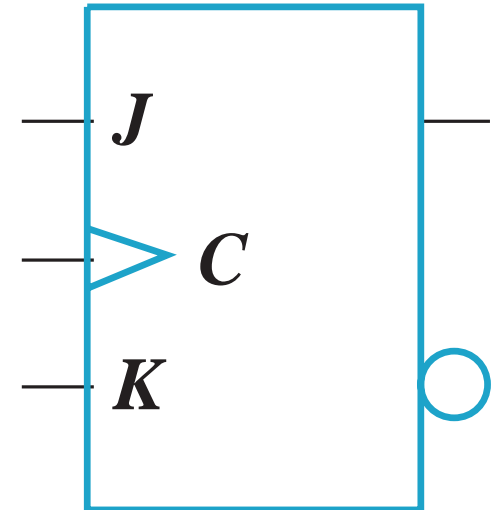



T Flip-flop


□ Behavior

- Has a single input T
 - For $T = 0$, no change to state
 - For $T = 1$, changes to opposite state
- Same as a J-K flip-flop with $J = K = T$
- As a master-slave, has same “**1s catching**” behavior as J-K flip-flop
- Cannot be initialized to a known state using the T input
 - Reset (asynchronous or synchronous) essential


T Flip-flop (continued)

□ Implementation

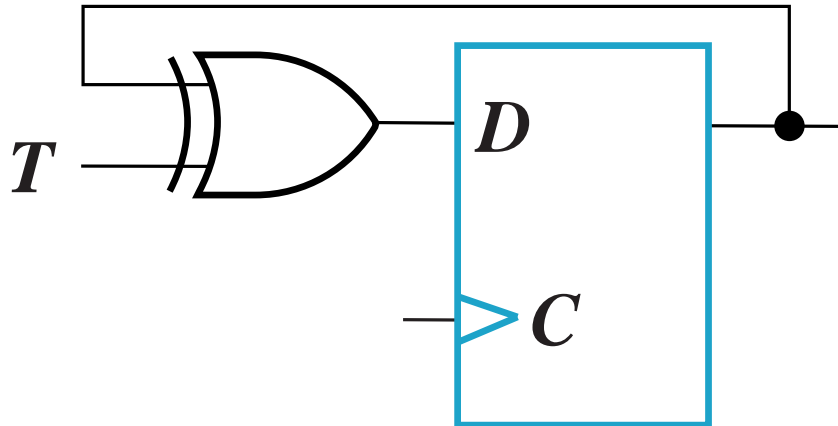- To avoid 1s catching behavior, one solution used is to use an edge-triggered D as the core of the flip-flop



■ Symbol

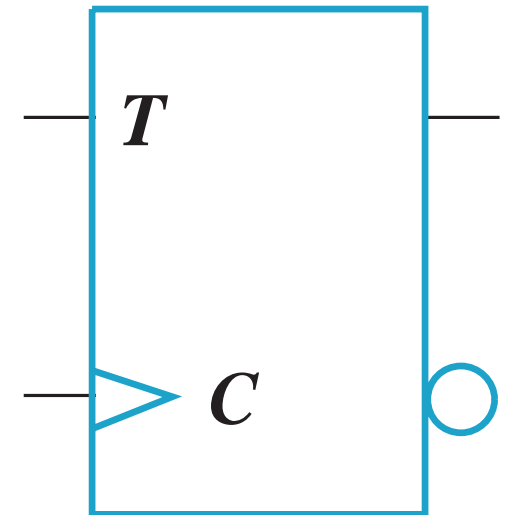



Basic Flip-Flop Descriptors

□ Used in analysis

- *Characteristic table* - defines the next state of the flip-flop in terms of flip-flop inputs and current state
- *Characteristic equation* - defines the next state of the flip-flop as a Boolean function of the flip-flop inputs and the current state

□ Used in design

- *Excitation table* - defines the flip-flop input variable values as function of the current state and next state



D Flip-Flop Descriptors

□ Characteristic Table

<i>D</i>	<i>Q(t + 1)</i>	<i>Operation</i>
<i>0</i>	<i>0</i>	<i>Reset</i>
<i>1</i>	<i>1</i>	<i>Set</i>

□ Characteristic Equation

$$Q(t+1) = D$$

□ Excitation Table

<i>Q(t + 1)</i>	<i>D</i>	<i>Operation</i>
<i>0</i>	<i>0</i>	<i>Reset</i>
<i>1</i>	<i>1</i>	<i>Set</i>



T Flip-Flop Descriptors

□ Characteristic Table

T	$Q(t+1)$	<i>Operation</i>
0	$Q(t)$	<i>No change</i>
1	$\bar{Q}(t)$	<i>Complement</i>

□ Characteristic Equation

$$Q(t+1) = T \oplus Q$$

□ Excitation Table

$Q(t+1)$	T	<i>Operation</i>
$Q(t)$	0	<i>No change</i>
$\bar{Q}(t)$	1	<i>Complement</i>

S-R Flip-Flop Descriptors

□ Characteristic Table

<i>S</i>	<i>R</i>	<i>Q(t + 1)</i>	<i>Operation</i>
0	0	<i>Q(t)</i>	<i>No change</i>
0	1	0	<i>Reset</i>
1	0	1	<i>Set</i>
1	1	?	<i>Undefined</i>

□ Characteristic Equation

$$Q(t+1) = S + \bar{R} Q, S \cdot R = 0$$

□ Excitation Table

<i>Q(t)</i>	<i>Q(t + 1)</i>	<i>S</i>	<i>R</i>	<i>Operation</i>
0	0	0	X	<i>No change</i>
0	1	1	0	<i>Set</i>
1	0	0	1	<i>Reset</i>
1	1	X	0	<i>No change</i>



J-K Flip-Flop Descriptors

□ Characteristic Table

<i>J</i>	<i>K</i>	$Q(t+1)$	<i>Operation</i>
0	0	$Q(t)$	<i>No change</i>
0	1	0	<i>Reset</i>
1	0	1	<i>Set</i>
1	1	$\bar{Q}(t)$	<i>Complement</i>

□ Characteristic Equation


$$Q(t+1) = J \bar{Q} + \bar{K} Q$$

□ Excitation Table

$Q(t)$	$Q(t+1)$	<i>J</i>	<i>K</i>	<i>Operation</i>
0	0	0	X	<i>No change</i>
0	1	1	X	<i>Set</i>
1	0	X	1	<i>Reset</i>
1	1	X	0	<i>No Change</i>

Flip-flop Behavior Example

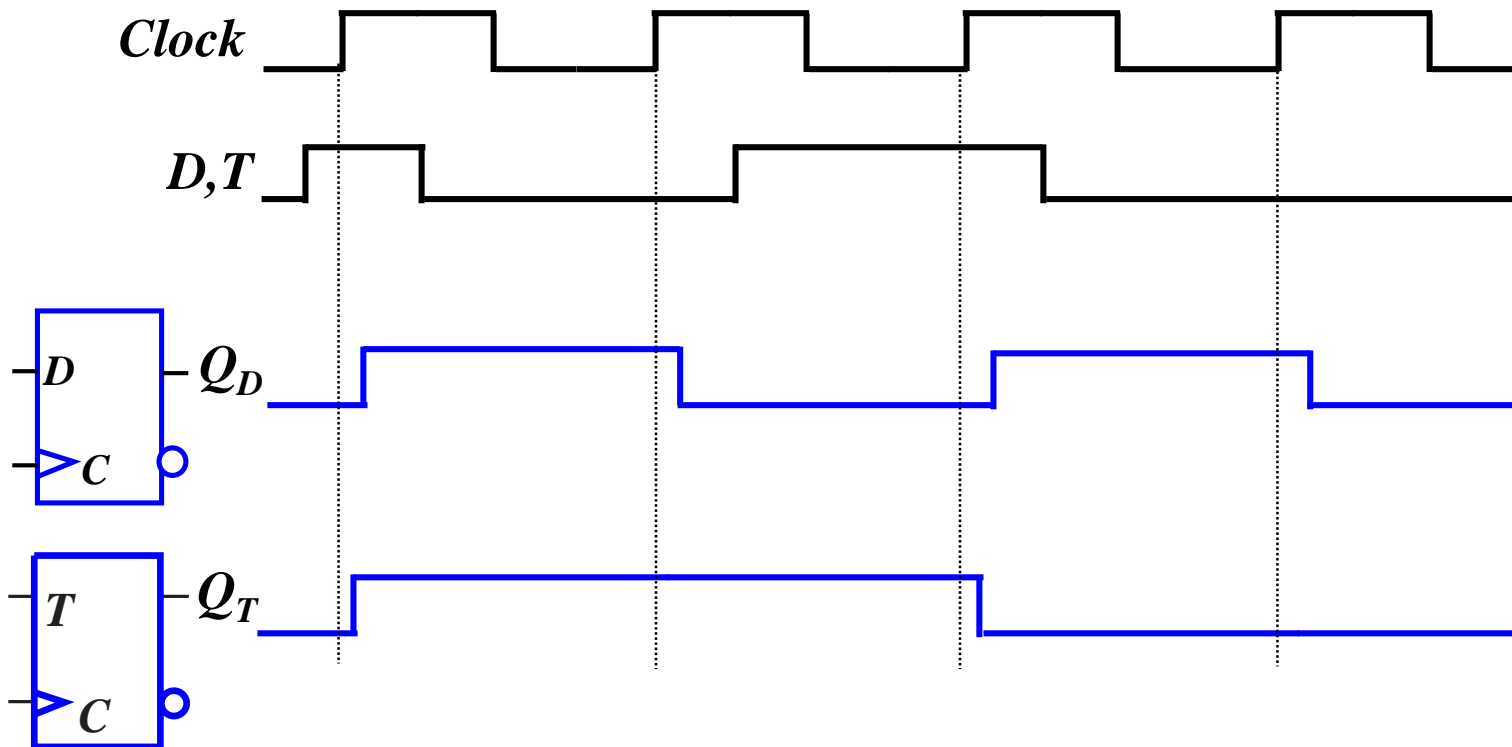
- Use the characteristic tables to find the output waveforms for the flip-flops shown:



Flip-Flop Behavior Example (continued)



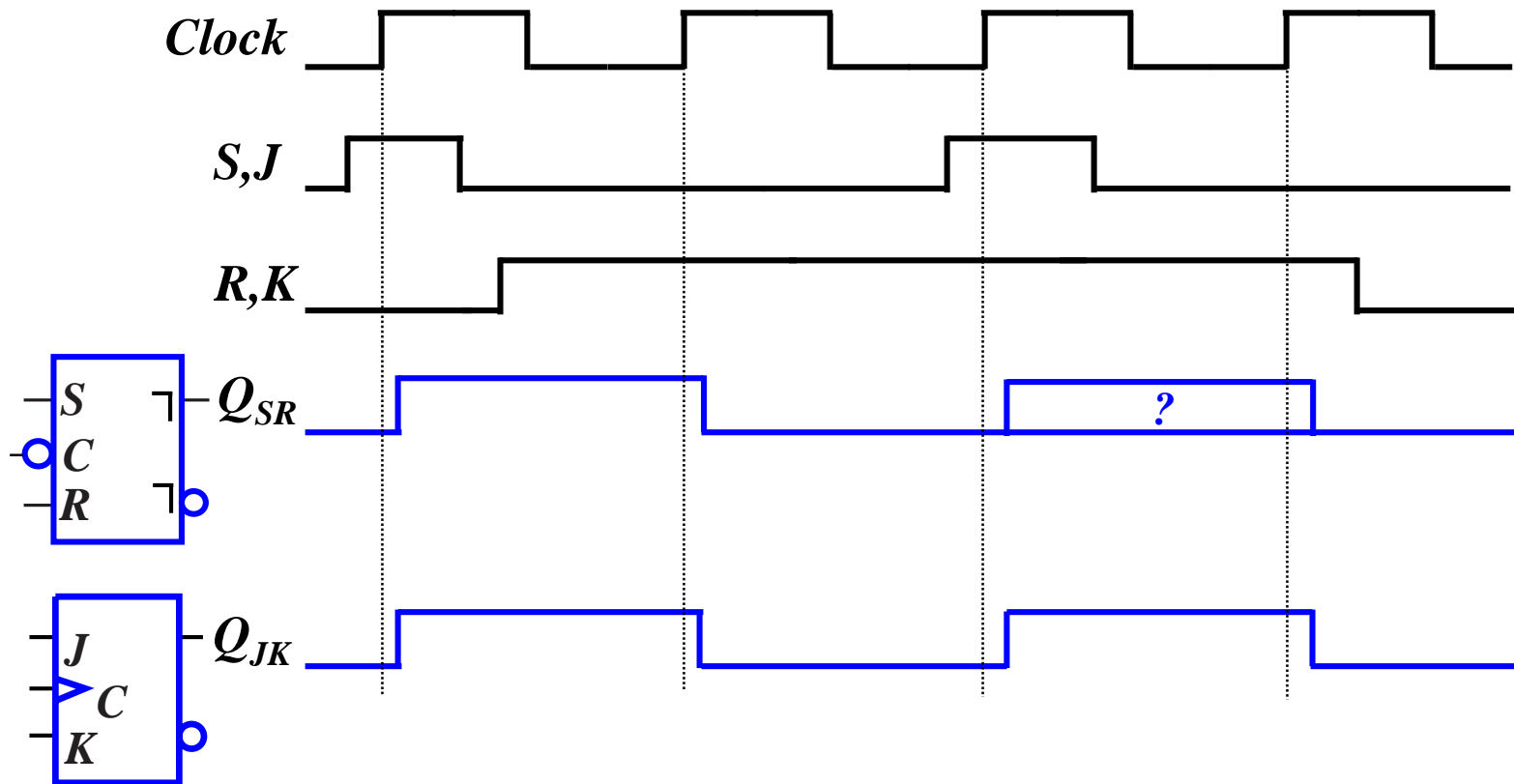- Use the characteristic tables to find the output waveforms for the flip-flops shown:





第五章作业 二

Ch4-2

page280-293:

4-13, 4-21, 4-22, 4-25, 4-29, 4-58, 4-59

*Sequential Circuit ,
It is only the states, nothing more!*

Thank you!

